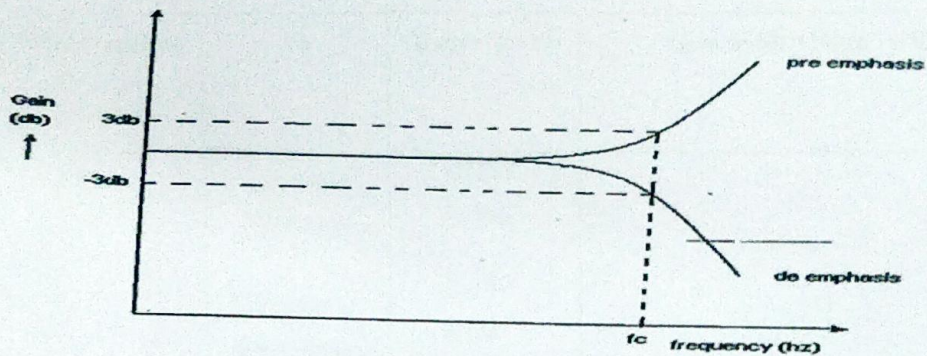


MODEL GRAPH



OBSERVATION FOR PRE-EMPHASIS:

$$V_i = 2V$$

Frequency(Hz)	V_o	Gain= V_o/V_i	Gain in dB= $20\log(V_o/V_i)$
500 Hz	0.60 mV	0.48	-6.375
600 Hz	1.16 V	0.58	-4.731
700 Hz	1.40 V	0.7	-3.098
800 Hz	1.60 V	0.8	-1.938
900 Hz	1.80 V	0.9	-0.915
1 k Hz	2.08 V	1.04	0.340
1.1 k Hz	2.36 V	1.18	1.437
1.2 k Hz	2.68 V	1.31	2.734
1.3 k Hz	2.96 V	1.48	3.405
1.4 k Hz	3.24 V	1.62	4.190
1.5 k Hz	3.56 V	1.78	5.008
1.6 k Hz	3.88 V	1.94	5.786
1.7 k Hz	4.2 V	2.1	6.444
1.8 k Hz	4.48 V	2.24	7.004
1.9 k Hz	4.76 V	2.38	7.531
2 k Hz	5.6 V	2.8	8.943

OBSERVATION FOR DE-EMPHASIS

$V_i = 1V$

Frequency(Hz)	V_o	Gain= V_o / V_i	Gain in dB = $20\log(V_o/V_i)$
500	920mV	0.920	- 0.124
600	880mV	0.880	- 1.11
700	880mV	0.880	- 1.11
800	880 840mV	0.840	- 1.514
900	760mV	0.760	- 2.383
1K	720mV	0.720	- 2.853
1.1K	720mV	0.720	- 2.853
1.2K	640mV	0.640	- 3.876
1.3K	640mV	0.640	- 3.876
1.4K	600mV	0.6	- 4.436
1.5K	600mV	0.6	- 4.436
1.6K	600mV	0.6	- 4.436
1.7K	560mV	0.56	- 5.03
1.8K	560mV	0.56	- 5.03
1.9K	480mV	0.48	- 6.375
2.0K	480mV	0.48	- 6.375

Analog and Digital Communication Lab

Experiment 4: Pre-Emphasis and De-Emphasis Circuits Using FM

I Pre-Lab Questions:

1. What is meant by threshold effect?

Soln. The loss of message signal in the output of the envelope detector due to low carrier-to-noise ratio is called as threshold effect.

2. What is pre-emphasis?

Soln. Pre-emphasis is employed in frequency modulation or phase modulation transmitters to equalize the modulating signal drive power in terms of deviation ratio.

3. How the threshold effect can be avoided?

Soln. The threshold effect can be improved by applying feedback in demodulators. Circuits such as phase-locked loops and frequency-locked loops so that the output SNR value does not fall rapidly.

4. What is fidelity?

Soln. Fidelity refers to the ability of the receiver to produce an exact replica of transmitted signal. It is provided at the output stage of the receiver.

5. What is sensitivity and selectivity?

Soln. Selectivity of radio receiver is the ability of a receiver to accept the wanted signal and to reject the unwanted.

Sensitivity of radio receiver is its ability to amplify the desired weak signal.

II Post-Lab Questions:

1. What is de-emphasis?

Soln. De-emphasis is the process of reducing the relative amplitudes of certain frequencies in a signal that have been exaggerated by pre-emphasis.

2 How to reduce noise during transmission in FM?

Soln Limiter circuit is used in FM receiver to remove the noise present in the peaks of the received signal and to remove any amplitude variation in the received signal, the output of the limiter has constant amplitude.

3 What should be the time constant in de-emphasis circuit?

Soln A time constant of $75 \mu s$, where $t = RC$. Any combination of resistor and capacitor giving this time constant will be satisfactory.

4 Why pre-emphasis is done after modulation?

Soln Pre-emphasis is employed in frequency modulation or phase modulation transmitters to equalize the modulating signal drive power in terms of variation portion.

5 List some applications of pre-emphasis circuit.

Soln In high speed digital transmission, pre-emphasis is used to improve signal quality at the output of a data transmission.

