

## UNIT-V


### DATA CONVERSION DEVICES

for processing, transmission & storage, it is often convenient to express analog values in digital form because it gives better accuracy and reduces noise

#### DAC Types

- (i) weighted resistor DAC
- (ii) R-2R ladder
- (iii) Inverted R-2R ladder.

#### WEIGHTED RESISTOR DAC

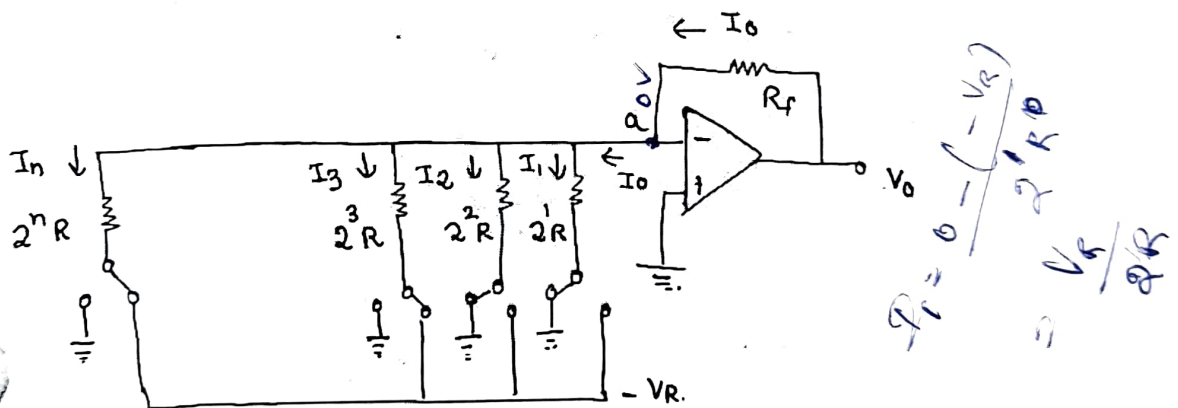

Summing amplifier with binary weighted resistor network. It has  $n$ -electronic switches  $d_1, d_2, \dots, d_n$  connected by binary input word. They are single pole double throw (SPDT) type. If binary i/p is 1, it connects resistance to reference voltage  $(-V_R)$ . And if input bit is 0, switch connects resistor to ground.

$$I_0 = I_1 + I_2 + \dots + I_n$$

$$= \frac{V_R}{2R} d_1 + \frac{V_R}{2^2 R} d_2 + \dots + \frac{V_R}{2^n R} d_n$$

$d_1 d_2 \dots d_n$  -  $n$  bit binary word.

$$\therefore = \frac{V_R}{R} [d_1 2^{-1} + d_2 2^{-2} + \dots + d_n 2^{-n}]$$

output voltage

$$V_o = I_o R_f$$


$$= V_R \frac{R_f}{R} [d_1 2^{-1} + d_2 2^{-2} + \dots + d_n 2^{-n}]$$

$$d_1 = 0 \quad d_2 = 0 \quad d_3 = 1$$

reference voltage is  $-V_R$

$\therefore$  positive staircase is obtained
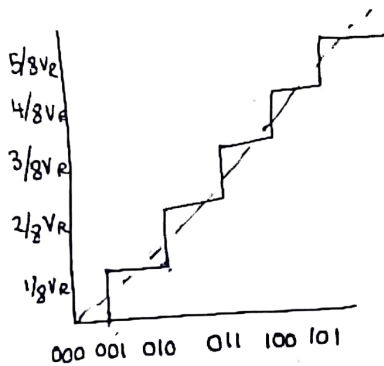
$$\begin{aligned} 001 &= V_R \left[ \frac{0}{2} + \frac{0}{4} + \frac{1}{8} \right] \\ &= \frac{V_R}{8} \end{aligned}$$



circuit shown is connected in inverting mode.

It can also be connected in non inverting mode.

op- am acts as  $I$  to  $V$  converter.


Accuracy & Stability of DAC depends of accuracy of resistors

disadv (i) wide range of resistors used.

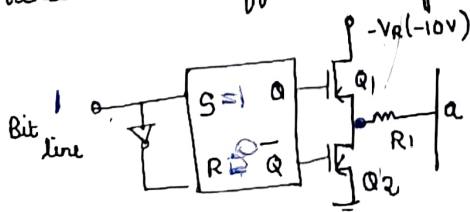(ii) for better resolution binary word length should be large.


Bipolar transistors donot perform well as voltage switches

hence by using totem pole MOSFET SWITCH low ON resistance & zero offset voltage can be achieved



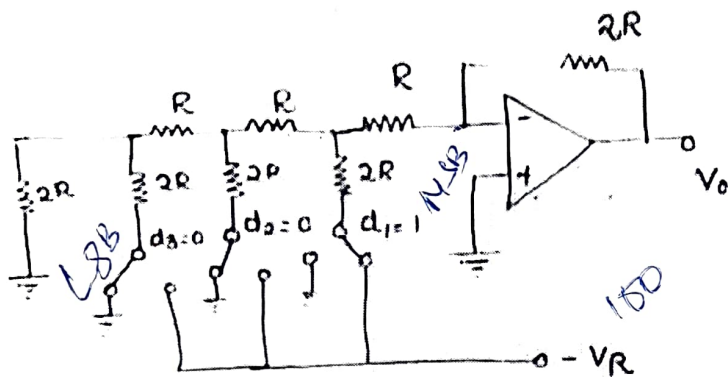
## R-2R Ladder DAC

wide range of resistors are required in binary weighted resistor type DAC. This is avoided by using R-2R ladder type DAC where only two values of resistors are required. Consider 3 bit DAC as shown below



Switch position,  $d_1, d_2, d_3$  corresponds to binary word 100

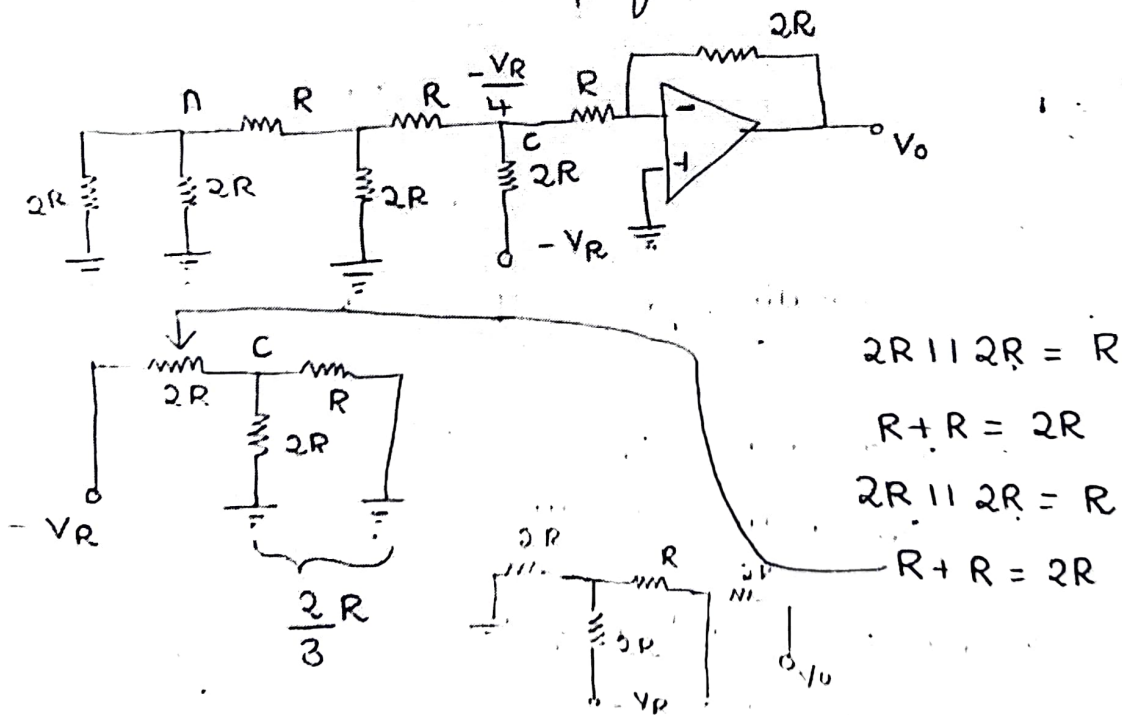
The circuit can be simplified as shown below



voltage at node C can be calculated as

$$= \frac{-V_R \left( \frac{2R}{3} \right)}{2R + \frac{2R}{3}} = -\frac{V_R}{4}$$

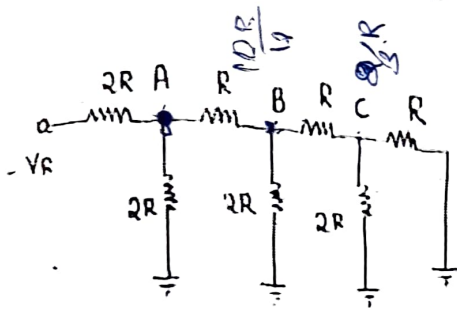the output voltage:  $V_0 = \frac{-2R}{L} \left( -V_R \right) = V_R = V_{FS}$




At A  $(R \parallel 2R) = \frac{2R^2}{3R} = \frac{2R}{3}$ ; series with R

$$\frac{2R}{3} + R = \frac{5R}{3}; \parallel \text{ with } 2R$$

$$\frac{\left(\frac{5R}{3}\right) 2R}{\frac{5R}{3} + 2R} = \frac{10R}{11}$$

series with R;  $\frac{10R}{11} + R = \frac{21R}{11}$

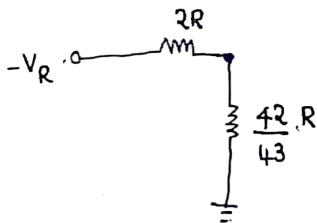
$\parallel$  to  $2R$ ;  $\frac{\left(\frac{21R}{11}\right) 2R}{\frac{21R}{11} + 2R} = \frac{42R}{43}$




voltage at A =  $-V_R \times \frac{42R}{43} \times \frac{21}{43}$

$$= -V_R \times \frac{42 \times 21}{43 \times 43}$$

$$V_A = -\frac{21}{64} V_R$$


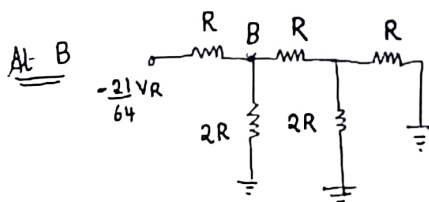


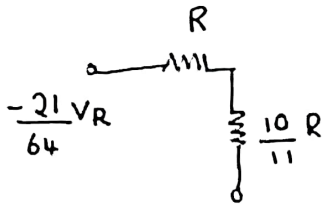

$$V_B = \frac{-\frac{21}{64} V_R \times \frac{10R}{11}}{\frac{10R}{11} + R}$$

$$= \frac{-\cancel{\frac{21}{64}} V_R \times \frac{10R}{\cancel{11}}}{\frac{\cancel{21}R}{\cancel{11}}}$$
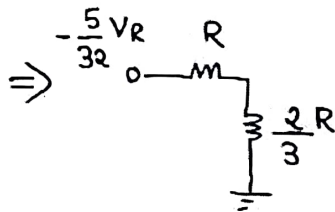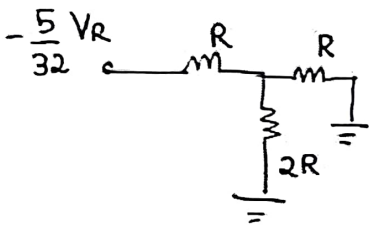
$$= -\frac{10V_R}{64} = -\frac{5}{32} V_R$$




$$\Rightarrow V_C = \frac{-\frac{5}{32} \times \frac{2R}{3}}{\frac{2R}{3} + R} = \frac{-\cancel{\frac{5}{32}} \times \cancel{\frac{2R}{3}}}{\frac{\cancel{2}R}{\cancel{3}}}$$

$$V_C = -\frac{1}{16} V_R$$


output voltage:  $V_0 = -\frac{2R}{R} \left( -\frac{V_R}{4} \right) = \frac{V_R}{2} = \frac{V_{FS}}{2}$

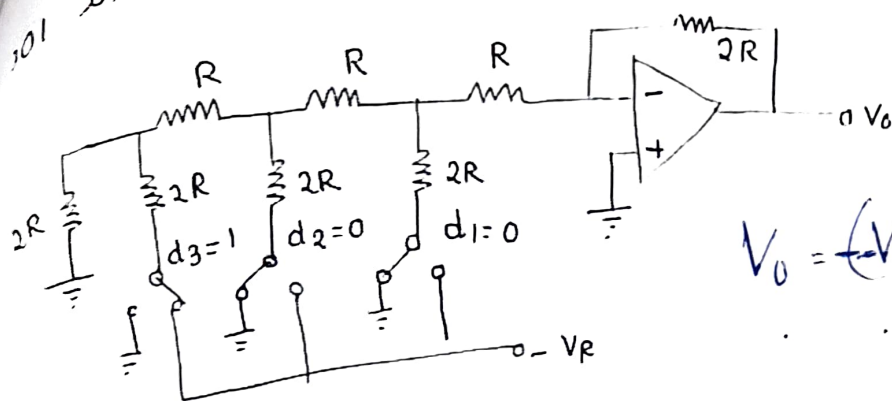switch position corresponding to binary word in 3 bit DAC is shown in circuit below



$$V_0 = -\left( \frac{V_R}{2} \right) \cdot \frac{R_f}{2R} \left[ \frac{d_1}{2} + \frac{d_2}{2^2} + \frac{d_3}{2^3} \right]$$

equivalent circuit is

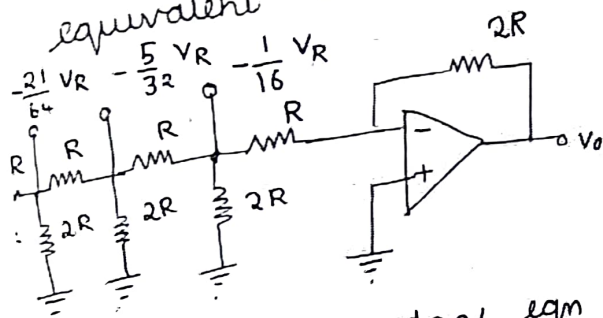

The output voltage eqn for this circuit is given

by

$$V_0 = -\frac{2R}{R} \left( -\frac{V_R}{16} \right) = \frac{V_R}{8} = \frac{V_{FS}}{8}$$

In similar fashion, output voltage for R-2R ladder type DAC corresponding to other 3 bit binary words can be calculated.