

Test: CLAT- 2

Course Code & Title: 18ECC201J – Analog Electronic Circuits

Year & Sem: II / IV

Date: 24-05-2022

Duration: 2 periods

Max. Marks: 50


Course Articulation Matrix :


Course Articulation Matrix :		Program Outcomes (POs)														
18ECC201J - Analog Electronic Circuits		Graduate Attributes												PSO		
COs	Course Outcomes (COs)	1	2	3	4	5	6	7	8	9	10	11	12	1	2	3
CO-1 :	Analyze bipolar amplifier circuits and their frequency response.	1	2	3	-	-	-	-	-	-	-	-	-	-	-	-
CO-2 :	Develop MOSFET amplifier circuits and their frequency response.	1	2	3	-	-	-	-	-	-	-	-	-	-	-	-
CO-3 :	Compile various negative feedback amplifier and oscillator circuits.	1	-	3	-	-	-	-	-	-	-	-	-	-	-	-
CO-4 :	Demonstrate the different classes of power amplifiers according to their performance characteristics.	1	2	3	-	-	-	-	-	-	-	-	-	-	-	-
CO-5 :	Construct the basic circuit building blocks that are used in the design of IC amplifiers, namely current mirrors and sources.	1	2	3	-	-	-	-	-	-	-	-	-	-	-	-
CO-6 :	Organize analog electronic circuits using discrete components to measure various analog circuits' performance.	-	-	3	-	-	-	-	-	2	-	-	-	3	1	-



Part - A


(10 x 1 = 10 Marks)

Instructions: Answer ANY 5 Questions

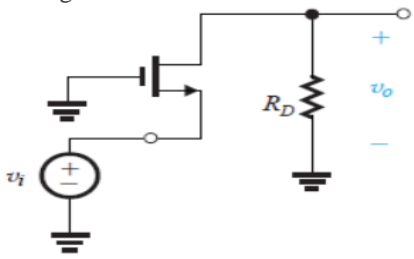
Q. No	Question	Marks	BL	CO	PO
1.	When a gate to source voltage of common source amplifier is at positive peak, drain to source voltage will be a. at positive peak b. at negative peak c. infinite d. zero	1	1	CO2	1
2.	What is the reason for connecting a capacitor in parallel with R_s ? a. It blocks the noise b. For ac signal it acts a short circuit resulting in grounding source terminal c. It blocks the noise & for ac signal it acts a short circuit resulting in grounding source terminal d. To increase impedance	1	2	CO2	1
3.	The MOSFET in the following circuit is in _____ configuration. 	1	2	CO2	1
4.	The lower and upper cut off frequency of MOSFET amplifier is 35KHz and 45MHz respectively. The calculated Bandwidth is _____. a. 10MHz	1	2	CO2	2

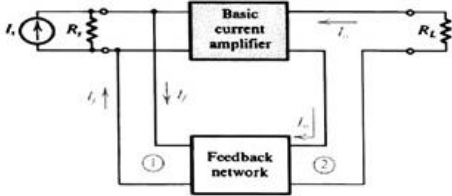	b. 80MHz c. 45MHz d. 5MHz				
5.	The _____ region produces the maximum voltage gain in a single-stage FET amplifier. a. low-frequency b. high-frequency c. mid-frequency d. corner frequency	1	2	CO2	1
6.	Name the feedback topology given below.  a. Series-Series b. Shunt-Series c. Shunt-Shunt d. Series-Shunt	1	2	CO3	2
7.	_____ connection increases both input and output impedance. a. Series-Series b. Shunt-Series c. Shunt-Shunt d. Series-Shunt	1	2	CO3	1
8.	The trans-resistance amplifier uses _____ feedback a. Series-Series b. Shunt-Series c. Shunt-Shunt d. Series-Shunt	1	2	CO3	1
9.	The phase shift network will produce a phase shift of 180 degrees at a. three different frequencies b. one frequency c. two different frequencies d. infinitely many frequencies	1	2	CO3	1
10	In clapp oscillator voltage is divided by using _____. a. resistors b. capacitors c. inductors d. voltage dividing circuits are not used	1	2	CO3	1
Part – B (4 x 10 = 40 Marks)					
SECTION B1 Instructions: Answer ANY 2 Questions					
11	Calculate the small signal voltage gain of the source follower circuit shown in Fig A.	10	3	CO2	2

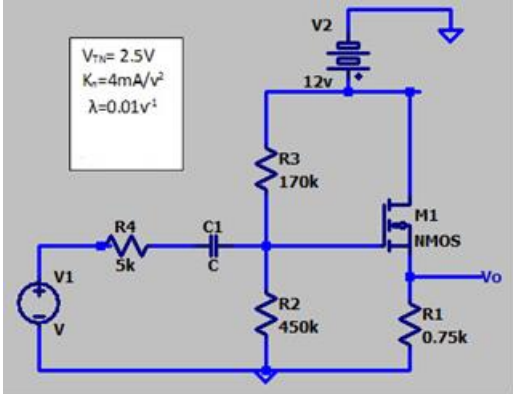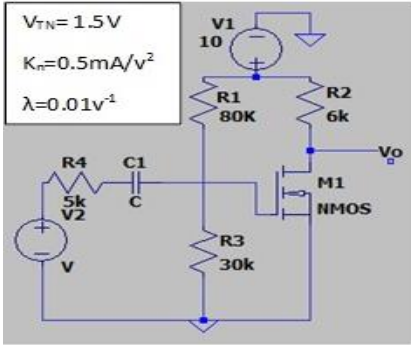					
	Fig A				
12	Draw the circuit of the n-channel common source amplifier and derive the expression for the input resistance , output resistance and voltage gain.	10	3	CO2	2
13	<p>a. Explain the impact of output coupling capacitor in frequency response of an amplifier with necessary diagram.</p> <p>b. Determine the input and output resistance of CS amplifier shown below.</p> 	5	2	CO2	2
		5	3	CO2	3
SECTION B2 Instructions: Answer ANY 2 Questions					
14	<p>a. Draw the current series feedback topology and derive the expression for the transfer gain, input resistance , output resistance with feedback.</p> <p>b. Explain the Barkhausen Criterion for an oscillator.</p>	8	3	CO3	2
		2	2	CO3	2
15	a. For a given circuit, identify the type of feedback topology and derive the expression for the transfer gain, input resistance and output resistance with feedback.	8	3	CO3	3

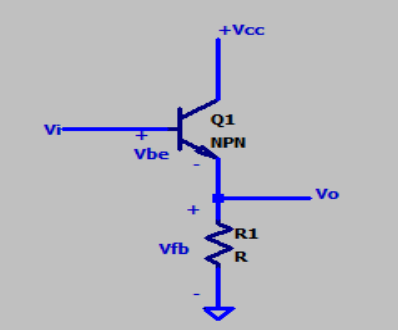					
	b. Compare Colpitts and Hartley oscillator.	2	2	CO3	1
16	a. A tank circuit contains an inductance of 1mH. Compute the range of tuning capacitor value if the resonant frequency ranges from 540Khz – 1650 KHz.	4	3	CO3	3
	b. Explain the working of Wein bridge oscillator with neat diagram, write the expression for frequency of oscillation and the condition for oscillation.	6	2	CO3	2

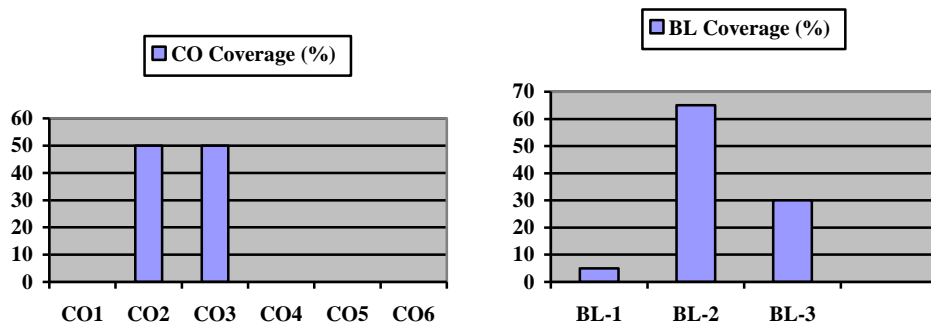Course Outcome (CO) and Bloom's level (BL) Coverage in Questions



Approved by the Course Coordinator

Signature of the Question paper setter

Evaluation Sheet

Name of the Student:

Register No.:

Part- A (10 x 1= 10 Marks)					
Q. No	CO	PO	Maximum Marks	Marks Obtained	Total
1	CO4	1	1		
2	CO4	1	1		
3	CO4	1	1		
4	CO4	2	1		
5	CO4	1	1		
6	CO5	2	1		
7	CO5	1	1		
8	CO5	1	1		
9	CO5	1	1		
10	CO5	1	1		
Part- B (4 x 10= 40 Marks)					
11	CO4	3	10		
12	CO4	2	10		
13.a	CO4	2	5		
13.b	CO4	3	5		
14.a	CO5	2	8		
14.b	CO5	2	2		
15.a	CO5	3	8		
15.b	CO5	1	2		
16.a	CO5	3	4		
16.b	CO5	2	6		

Consolidated Marks:

CO	Maximum Marks	Marks Obtained
2		
3		
Total		

PO	Maximum Marks	Marks Obtained
1		
2		
3		
Total		

Signature of Course Teacher

Signature of the Course Coordinator

Signature of the Academic Advisor