

# **LINEAR INTEGRATED CIRCUITS**

## Unit-1

# Table of Content

- Op-amp symbol, terminals, packages
- Op-amp-Specifications
- Block diagram Representation of op-amp
- Ideal op-amp & practical op-amp - Open loop & closed loop configurations
- Basic op-amp internal schematic
- Review of data sheet of an op-amp
- DC Characteristics of op-amp
- AC Characteristics of op-amp

# The Operational Amplifier

- An operational amplifier (op-amp) is a direct coupled high-gain amplifier usually consisting of one or more differential amplifier and followed by a level translator and an output stage.
- A direct-coupled amplifier is a type of amplifier in which the output of one stage of the amplifier is coupled to the input of the next stage in such a way to permit signals with zero frequency, also referred to as direct current to pass from input to output.
- Operational amplifier is abbreviated as op-amp.

# Application of op-amp

- The operational amplifier was originally designed for performing mathematical operations such as addition, subtraction, multiplication, integration.
- It can also be used for amplification of dc as well as ac input signal, active filters, oscillators, comparators, regulator and other by addition of external suitable feedback components.

# Op-amp symbol

- The circuit schematic of an op-amp is a triangle as shown in Fig.1.
- It has 2 input terminals and 1 output terminal.
- The terminal with a (-) sign is called inverting input terminal.
- The terminal with (+) sign is called non-inverting input terminal

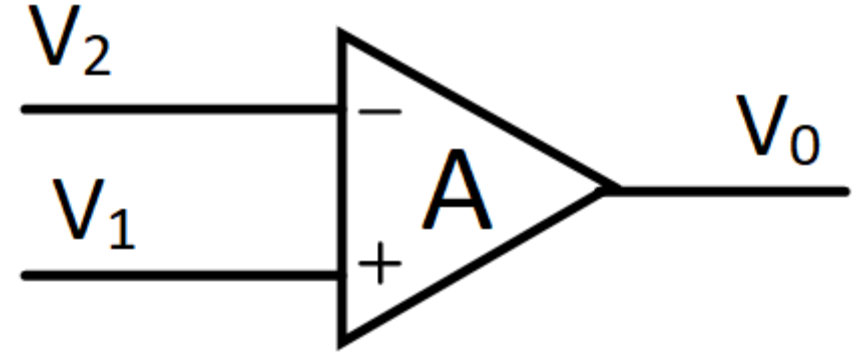


Fig.1. Schematic symbol for the op-amp

From the Fig.1.

$V_1$  = Voltage at the non-inverting input terminal (Volts).

$V_2$  = Voltage at the inverting input terminal (Volts).

$V_0$  = Output voltage (Volts).

All these voltages are measured with respect to ground.

A= Large signal voltage gain

# Op-amp Packages

Basic op-amp diagram with supply voltage is shown in Fig.2.

- Op-amps have 5 basic terminals

- 2 input terminals

- 1 output terminal

- 2 power supply

- Positive power supply (  $V+$  )
- Negative power supply (  $V-$  )
- Power supply may range  $\pm 5\text{ V}$  to  $\pm 22\text{ V}$

Generally,  $\pm 15\text{ V}$  is used as power supply.

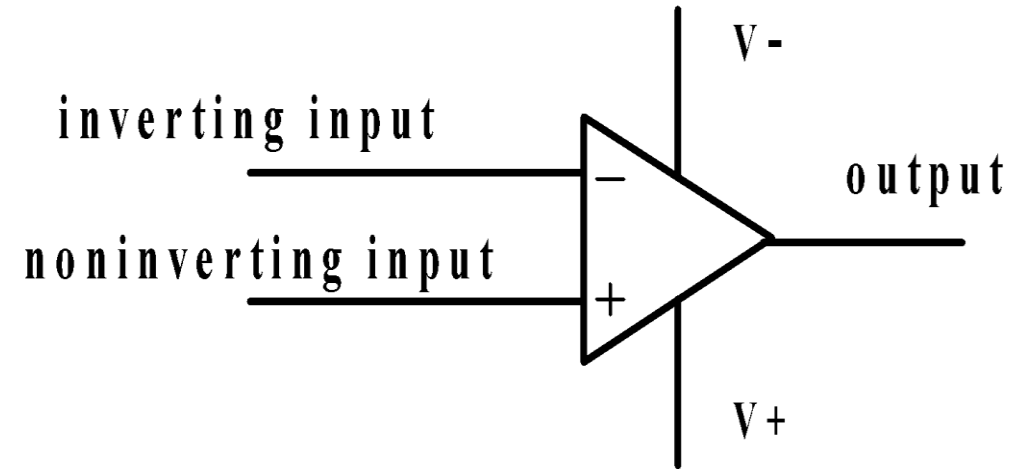


Fig. 2: Basic op-amp diagram with supply voltage

# Op-amp packages

- There are 3 popular packages available:
  - (i) The flat package
  - (ii) The metal can or transistor (TO) package
  - (iii) The dual-in-line package (DIP) (8,12,14,16, 20 pins)

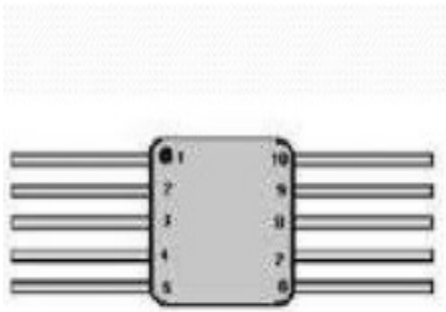


Fig. 3.a. Flat pack



Fig. 3.b. metal can package

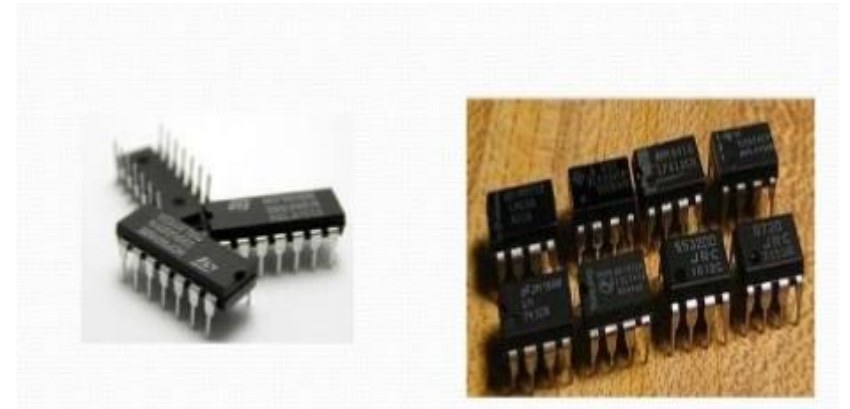


Fig. 3.c. Dual-in-line package (741)

# Operational Amplifiers Pin configuration

The pin configuration of 8 pin mini DIP is shown as follows:

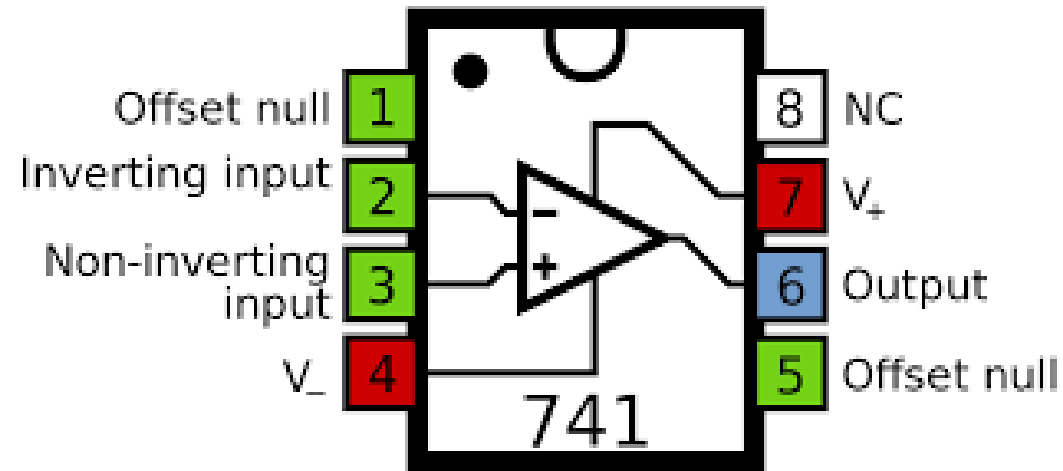


Fig. 4: Pin connection, LM741



# Op-amp specifications

## Temperature Ranges:

- All Ics are manufactured fall into one of 3 basic temperature grades:
  - (i) Military temperature range:  $-55^{\circ}\text{C}$  to  $+125^{\circ}\text{C}$  (or  $-55^{\circ}\text{C}$  to  $+85^{\circ}\text{C}$  )
  - (ii) Industrial temperature range:  $-20^{\circ}\text{C}$  to  $+85^{\circ}\text{C}$  (or  $-40^{\circ}\text{C}$  to  $+85^{\circ}\text{C}$  )
  - (iii) Commercial temperature range:  $0^{\circ}\text{C}$  to  $+70^{\circ}\text{C}$  (or  $0^{\circ}\text{C}$  to  $+75^{\circ}\text{C}$  )

# Op-amp specifications (Cont.)

- 741 an internally compensated op-amp originally manufactured by Fairchild.
- Some of the well-known manufacturers of linear Ics are:
  1. Fairchild-----  $\mu A$ ,  $\mu AF$
  2. National semiconductor----- LM, LH, LF, TBA
  3. Motorola----- MC, FC
  4. RCA -----CA, CD
  5. Texas Instruments----- SN
  6. Signetics-----N/S, NE/SE
  7. Burn-Brown-----BB

## Op-amp specifications (Cont.)

- $\mu$ A741 is also manufactured by other manufactures as follows:

1. National semiconductor-----LM741
2. Motorola-----MC1741
3. RCA-----CA3741
4. Texas Instruments-----SN52741
5. Signetics-----N/S741

Some linear Ics are available in different classes such as A, C, E, S, and SC.

## Op-amp specifications (Cont.)

- 741-----Military graded op-amp
- 741C-----Commercial grade op-amp
- 741A-----Improved version of 741
- 741E-----Improved version of 741C
- 741S-----Military graded op-amp with higher slew rate
- 741SC-----Commercial grade op-amp with higher slew rate

# Block diagram representation of op-amp

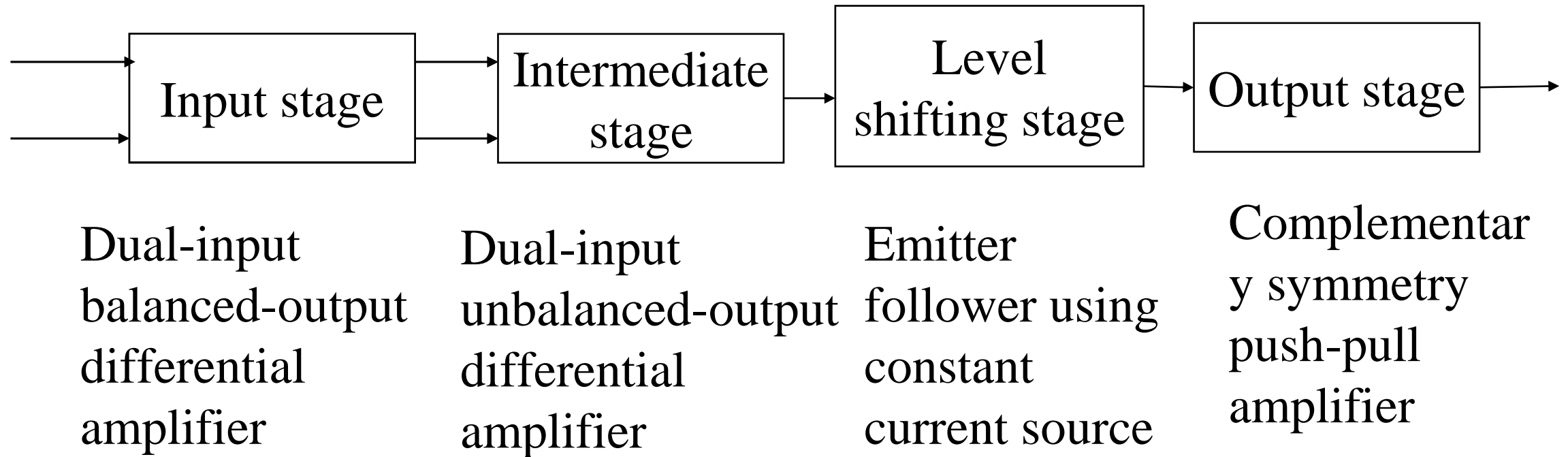


Fig. 5. Block diagram of an op-amp

- The op-amp consists of 4 stages namely input stage, intermediate stage, level shifting stage, output stage.

## Block diagram representation of op-amp (Cont.)

- The input stage is the dual-input balanced output differential amplifier. The main purpose of the differential amplifier is to **provide high gain to the difference mode signal and cancel the common mode signal**. The input stage provides **most of the voltage gain** of the amplifier and also establishes **the input resistance** of the op-amp.
- The intermediate stage is driven by input stage. In most amplifiers the intermediate stage is dual input, unbalanced (single ended) output. Because, **direct coupling** is used, the dc voltage at the output of the intermediate stage is well **above ground potential**.
- Generally, the level translator (shifting) circuit is used after intermediate stage to **shift the dc level** at the output of the intermediate stage downward to **zero volt with respect to ground**. Here emitter follower using constant current source is used.

## Block diagram representation of op-amp (Cont.)

- The final stage of op-amp is output stage, it consists of **complementary symmetry push-pull amplifier**. Due to the use of push-pull complementary amplifier, the output voltage swing increases, and current supplying capability of the op-amp raises. A well designed output stage **also provides low output resistance**.

# Basic op-amp internal schematic

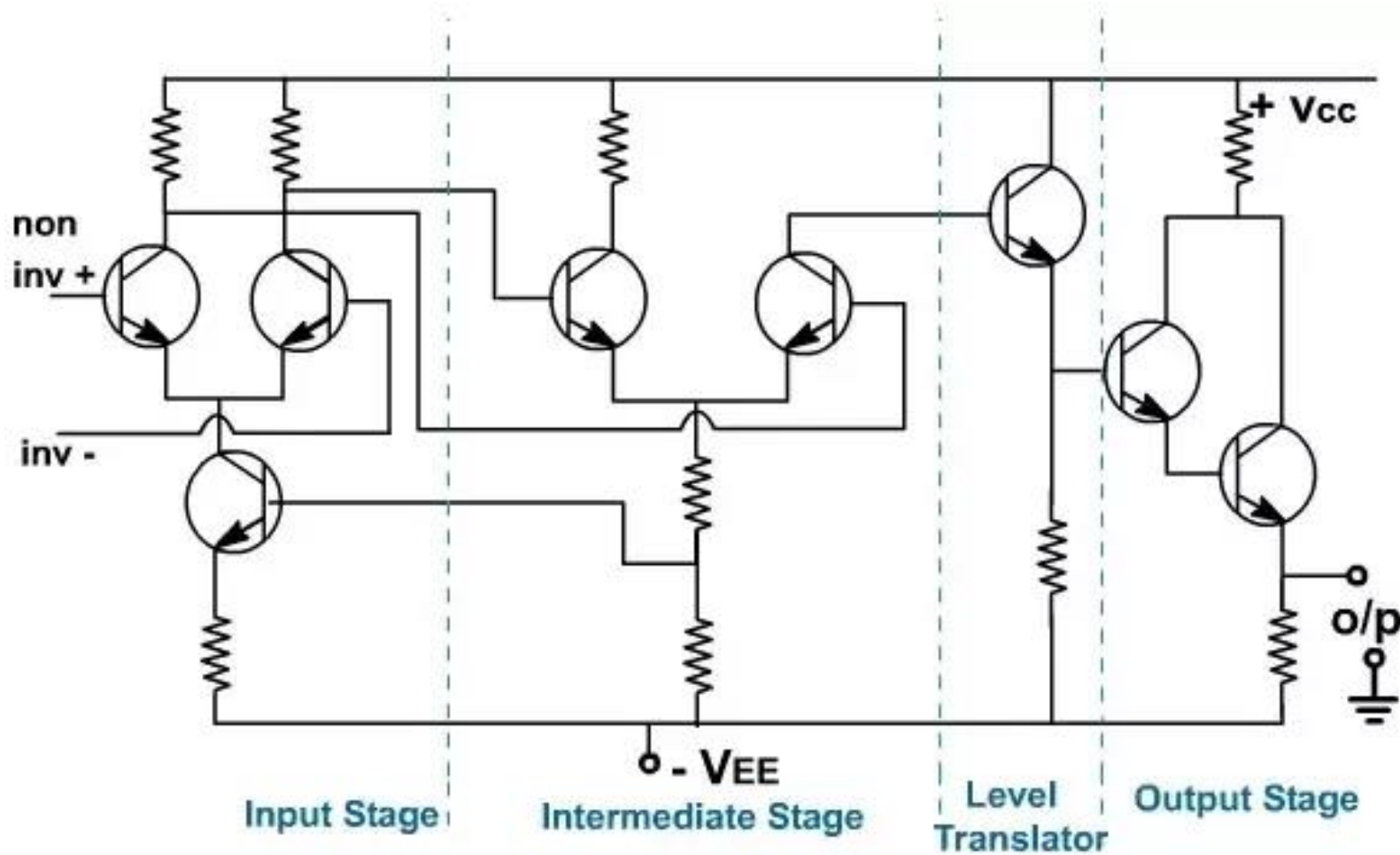


Fig. 6. Internal schematic of op-amp (MC 1435 op-amp)



# The ideal op-amp

- An ideal op-amp would show the following characteristics:
  1. Infinite voltage gain  $A$ 
    - ✓ for finite output voltage.
  2. Infinite input resistance  $R_i$ 
    - ✓ so that almost any signal source can drive it and there is no loading of preceding stage.
  3. Zero output resistance  $R_o$ 
    - ✓ so that output can drive infinite number of other devices.
  4. Zero output voltage when input voltage is zero.
  5. Infinite bandwidth
    - ✓ so that any frequency from 0 to  $\infty$  Hz can be amplified without attenuation.

## The ideal op-amp (Cont.)

### 6. Infinite common-mode rejection ratio (CMRR)

✓ so that output common-mode noise voltage is zero

✓ CMRR is ratio of differential voltage gain to the common mode voltage gain.

### 7. Infinite slew rate (SR)

✓ so that output voltage changes occur simultaneously with input voltage changes.

✓ Slew rate (SR) is defined as the maximum rate of change of output voltage per unit time and is expressed in volt per microsecond.

# Equivalent circuit of an op-amp

- The equivalent circuit of an op-amp includes voltage gain (open loop voltage gain) ( $A$ ), differential voltage ( $V_d$ ), output resistance ( $R_o$ ), input resistance ( $R_i$ ).
- The equivalent circuit of an op-amp is shown in Fig. 7.

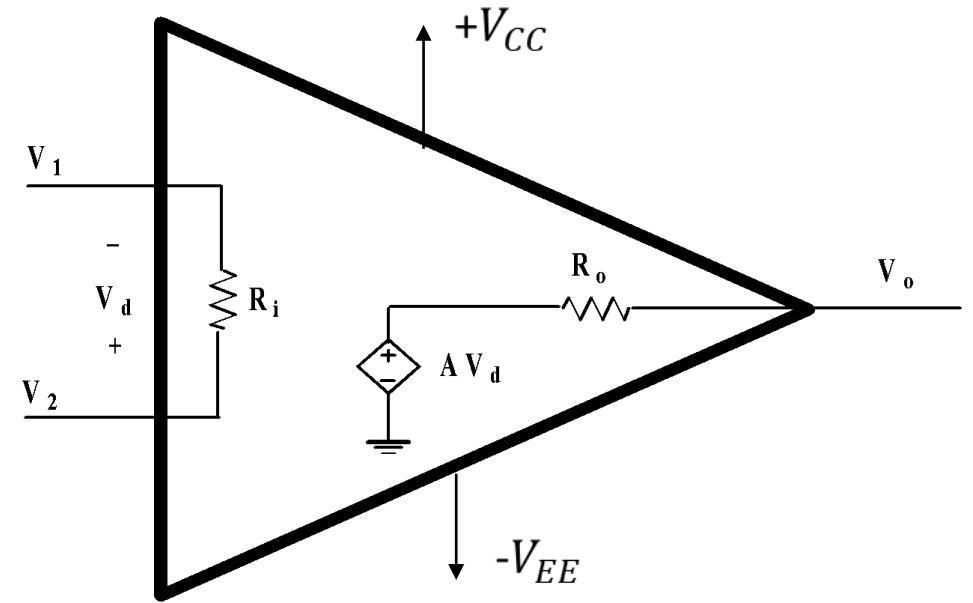


Fig.7. Equivalent circuit of an op-amp

Here,  $V_1$  = input at inverting terminal

$V_2$  = input at non-inverting terminal

Output voltage =  $V_o = A V_d = A (V_2 - V_1)$  ----- Equation—(1)

Equation (1) indicates that op-amp amplifies the difference between 2 input voltages.

## Equivalent circuit of an op-amp (Cont.)

- The output can not exceed positive and negative saturation voltage.
- positive saturation voltage  $(+V_{sat}) < +V_{CC}$  (positive power supply)
- negative saturation voltage  $(-V_{sat}) < -V_{EE}$  (negative power supply) .
- The ideal voltage transfer curve (assuming output offset voltage is zero) is shown in Fig. 8.

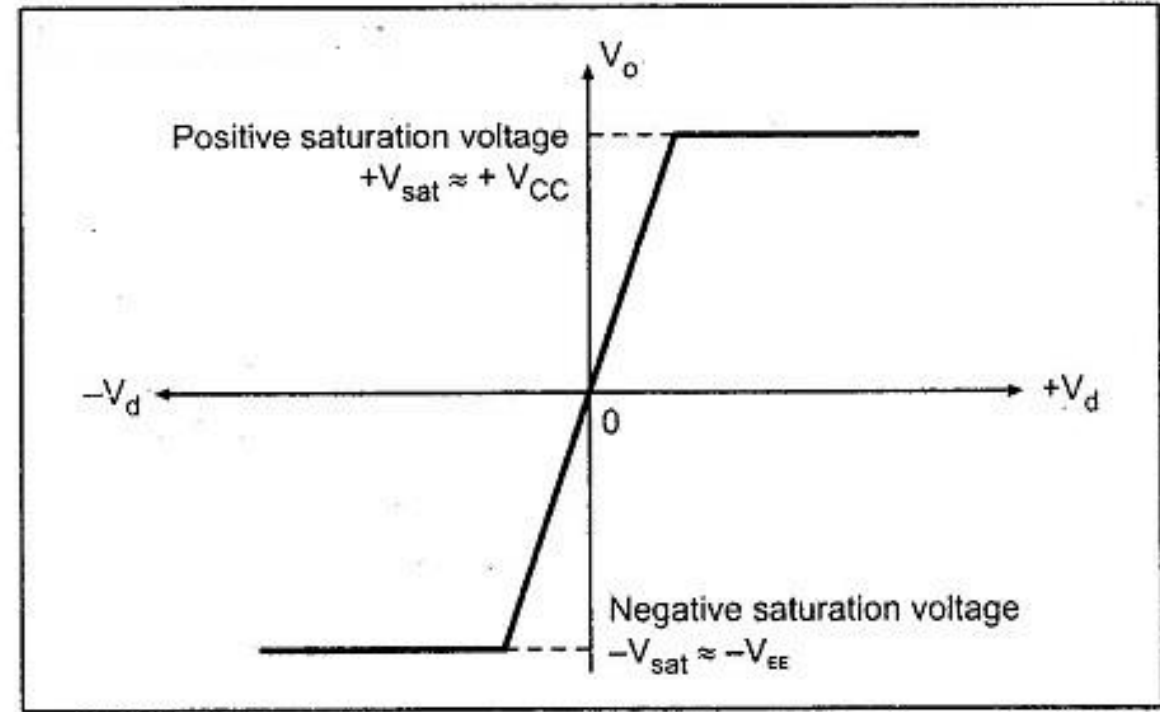


Fig. 8. Ideal voltage transfer curve

# Open-loop configuration

- In open loop op-amp configuration, no connection either direct or via another network exists between the output and input terminals.  
(Output signal is not feedback to input).

There are 3 open-loop op-amp configurations:

1. Differential amplifier
2. Inverting amplifier
3. Non-inverting amplifier

# Open-loop differential amplifier

- Op-amp amplifies both dc as well as ac input.
- The source resistance  $R_{i1}$  and  $R_{i2}$  are normally negligible compared to input resistance  $R_i$ .
- So the voltage drop across resistor assumed to be zero
- So,  $V_1 = V_{i1}$ ,  $V_2 = V_{i2}$
- Output voltage =  $V_0 = AV_{id} = A(V_1 - V_2)$   
 $\Rightarrow V_0 = A(V_{in1} - V_{in2})$
- Here, gain  $A$  is referred as open-loop gain.

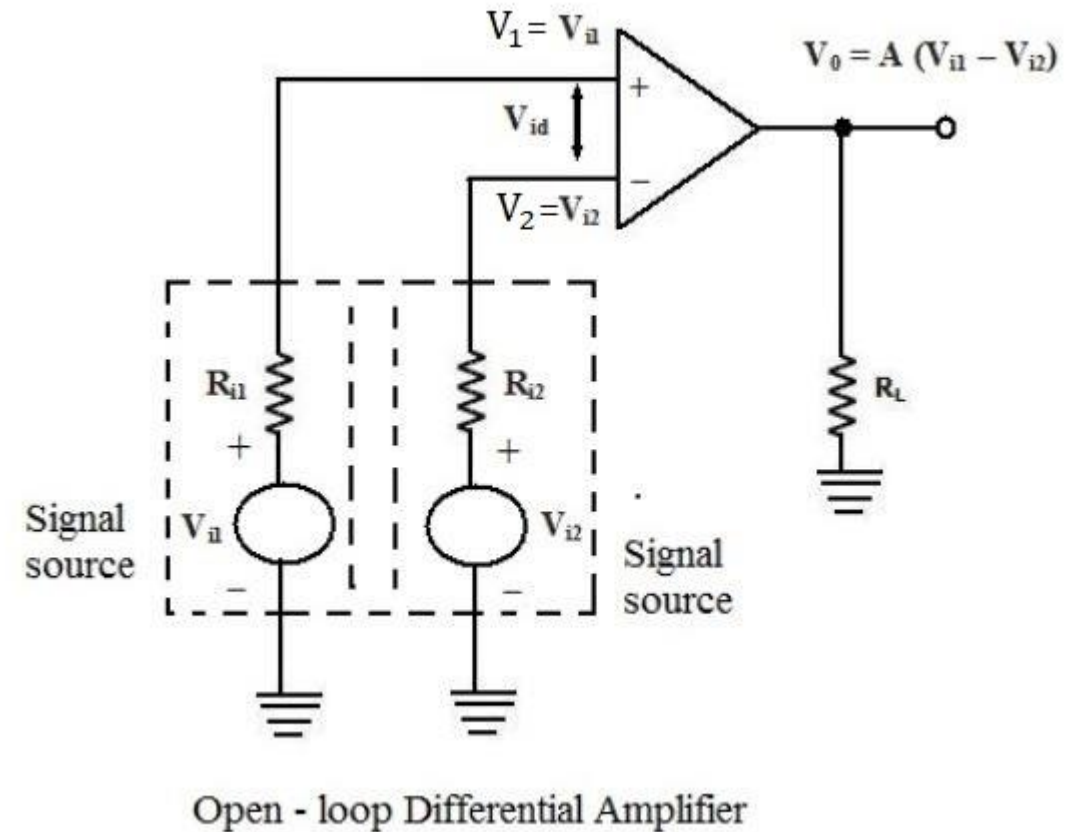


Fig. 9. Open-loop differential amplifier

# Open-loop inverting amplifier

- Open-loop noninverting amplifier is shown in Fig. 10.
- From Fig. 10,
- $V_1 = 0, V_2 = V_i$
- Output voltage =  $V_0 = AV_{id} =$   
$$A(V_1 - V_2)$$
  
$$\Rightarrow V_0 = A(0 - V_i) = -A V_i$$
- The negative sign indicates that the output of phase with respect to input by  $180^\circ$  or is of opposite polarity.
- Thus in inverting amplifier, the input signal is amplified by gain  $A$  and also inverted at output

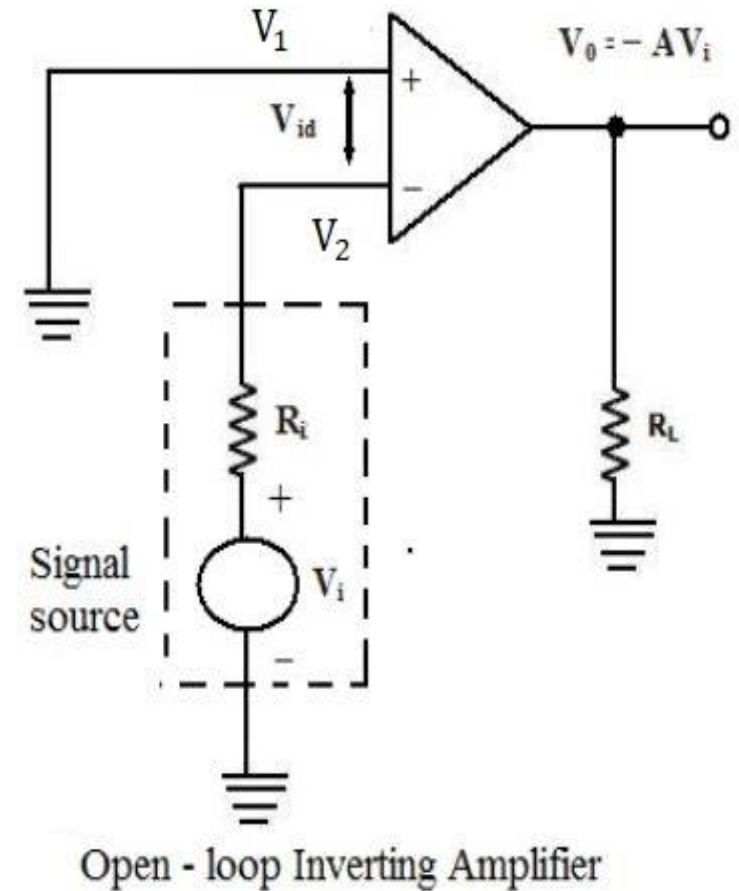


Fig. 10. Open-loop inverting amplifier

# Open-loop non inverting amplifier

- Open-loop noninverting amplifier is shown in Fig. 11.
- From Fig. 11,
- $V_1 = V_i, V_2 = 0$
- Output voltage=  $V_0 = AV_{id} =$   
 $A(V_1 - V_2)$   
 $\Rightarrow V_0 = A(V_i - 0) = A V_i$

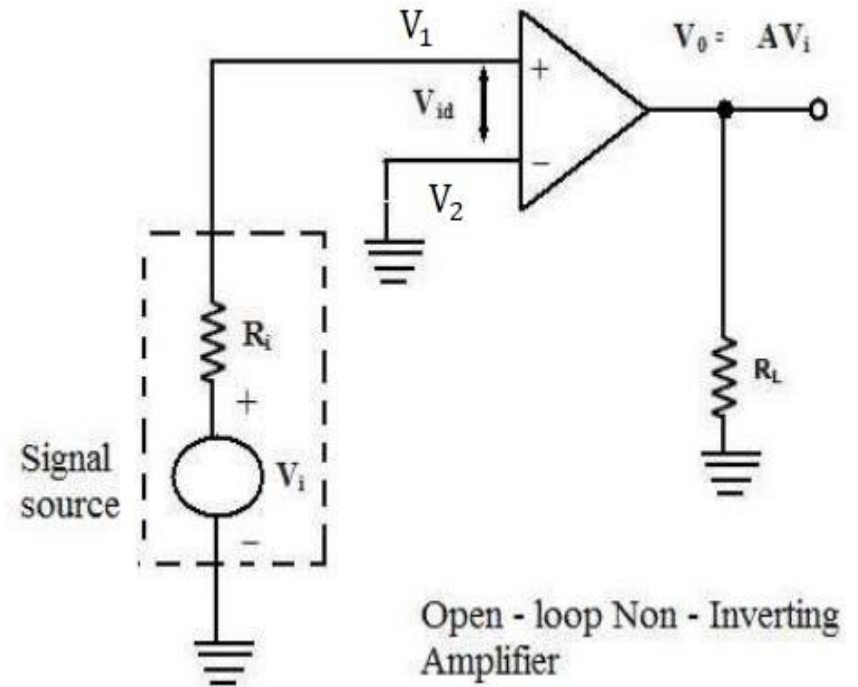


Fig. 11. Open-loop non-inverting amplifier



# Problems

1. Q. Determine the output voltage for the open-loop inverting amplifier, if:
  - a. Input voltage=20 mV dc.
  - b. Input voltage=-50  $\mu$ V peak sine wave

Assume op-amp is 741 (saturation voltage  $\pm 14$  V,  $A=2,00,000$ ).

Ans:-

a.  $V_0 = -A V_i = -2,00,000 \times 20 \times 10^{-3} = -400$  V

So, output voltage is -14V.

b.  $V_0 = -A V_i = -2,00,000 \times (-50) \times 10^{-6} = 10$  V

So, output voltage is 10 V.

# Closed loop configurations (feedback in ideal op-amp)

- Open loop gain of an op-amp can be very high.
- This very high gain is no real use to us as it makes the amplifier both unstable and hard to control.
- The utility of an op-amp can be greatly increased by providing negative feedback. (Connecting output to the inverting terminal).
- The output in this case is not driven into saturation and circuit behaves in linear manner.
- For the feedback circuit for simplification, 2 assumptions considered.
  - (i) The current drawn by either of input terminals (non-inverting and inverting) is negligible.
  - (ii) The differential input voltage ( $V_d$ ) between non-inverting and inverting input terminal is essentially zero ( $V_d=0$ )

# Closed loop configurations (feedback in ideal op-amp) (Cont.)

There are 4 closed loop op-amp configurations are available.

1. Inverting amplifier
2. Non-inverting amplifier
3. Voltage follower
4. Differential amplifier

# Inverting amplifier

The inverting amplifier is shown in Fig. 12.

Here,  $R_1 = \text{input resistance}$ ,

$R_f = \text{feedback resistance}$

As we have considered 2 assumption for closed loop configuration

(i)  $V_d = 0 \Rightarrow V_1 - V_2 = 0$ ,

As  $V_1 = 0$ , So,  $V_2 = 0$ . This is known as virtual ground.

(ii) The current drawn by either of input terminals (non-inverting and inverting) is negligible.

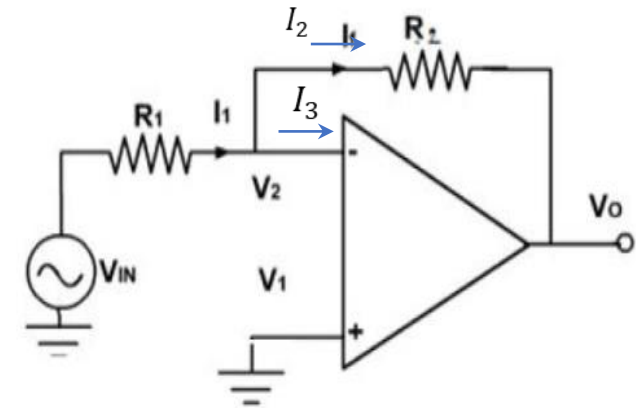


Fig.12. Inverting amplifier

## Inverting amplifier (Cont.)

Applying KCL at point  $V_2$

$$I_1 = I_2 + I_3 \quad \text{As } I_3 = 0$$

$$\Rightarrow \frac{V_{in} - V_2}{R_1} = \frac{V_2 - V_0}{R_f} \quad \text{As } V_2 = 0$$

$$\Rightarrow \frac{V_{in}}{R_1} = \frac{-V_0}{R_f} \Rightarrow V_0 = \frac{-R_f}{R_1} V_{in}$$

$$\Rightarrow \text{So, Output voltage} = V_0 = \frac{-R_f}{R_1} V_{in}$$

- Closed loop gain of inverting amplifier

$$= A_{CL} = \frac{V_0}{V_{in}} = \frac{-R_f}{R_1}$$

- The negative sign indicate phase shift of  $180^\circ$ .
- To avoid loading effect,  $R_1$  should be large.

## Non-inverting amplifier

The noninverting amplifier is shown in Fig. 13.

Here,  $R_1 = \text{input resistance}$ ,  
 $R_f = \text{feedback resistance}$

As we have considered 2 assumption for closed loop configuration

(i)  $V_d = 0 \Rightarrow V_1 - V_2 = 0$ ,

As  $V_1 = V_{in}$ , So,  $V_2 = V_{in}$ .

(ii) The current drawn by either of input terminals (non-inverting and inverting) is negligible. So,  $I_3 = 0$ .

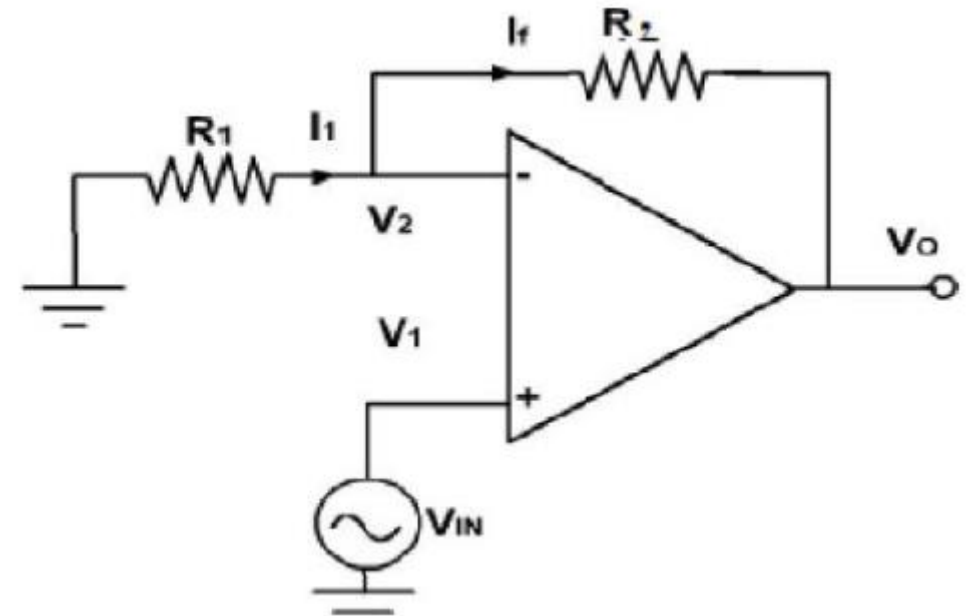


Fig.13. Non-inverting amplifier

## Non-inverting amplifier (Cont.)

Applying KCL at point  $V_2$

$$I_2 = I_1 + I_3 \quad \text{As } I_3 = 0$$

$$\Rightarrow \frac{V_0 - V_2}{R_f} = \frac{V_2 - 0}{R_1} \quad \text{As } V_2 = V_{in}$$

$$\Rightarrow \frac{V_0 - V_{in}}{R_f} = \frac{V_{in}}{R_1} \Rightarrow V_0 = \left(1 + \frac{R_f}{R_1}\right) V_{in}$$

$$\Rightarrow \text{So, Output voltage} = V_0 = \left(1 + \frac{R_f}{R_1}\right) V_{in}$$

- Closed loop gain of noninverting amplifier

$$= A_{CL} = \frac{V_0}{V_{in}} = \left(1 + \frac{R_f}{R_1}\right)$$

# Voltage follower

The voltage follower circuit is shown in Fig. 14.

In this circuit,  $R_f = 0$ ,  $R_i = \infty$ .

Voltage across A is  $V_2$  and B is  $V_1$

As  $V_d = 0 \Rightarrow V_1 - V_2 = 0$ ,

As  $V_1 = V_{in}$ , So,  $V_2 = V_{in}$ .

So,  $V_0 = V_2 = V_{in}$

$\Rightarrow$  So, Output voltage =  $V_0 = V_{in}$

Closed loop gain of voltage follower

$$= A_{CL} = \frac{V_0}{V_{in}} = 1$$

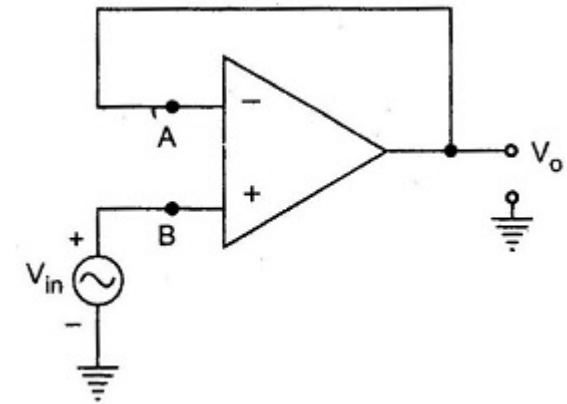


Fig.14. Voltage follower



# Review of data sheet of an op-amp

- The various electrical parameters supplied in the data sheets are as follows:

## 1. Input offset voltage:

- It is the voltage that must be applied between the input terminals of an op-amp to nullify the output.
- Since this voltage could be positive or negative, its absolute value is listed on the data sheet.
- For 741C, maximum value of input offset voltage is 6 mV.

## 2. Input offset current:

- The algebraic difference between current in negative input and positive input is referred to as input offset current.
- It is 200 nA maximum for 741C.

# Review of data sheet of an op-amp (Cont.)

## 3. Input bias current:

- The average of the currents entering into the negative input and positive input terminal of op-amp is called input bias current.
- Its value is 500 nA for 741C.

## 4. Input resistance:

- This is the differential input resistance as seen at either of the input terminals with the other terminal connected to ground.
- For 741C, the input resistance is 2 M $\Omega$ .

# Review of data sheet of an op-amp (Cont.)

## 5. Input capacitance:

- It is the equivalent capacitance that can be measured at either of the input terminal with the other terminal connected to ground.

## 6. Offset voltage adjust range:

- For 741C offset voltage adjustment range is  $\pm 15$  mV.

## 7. Input voltage range:

- This is the common-mode voltage that can be applied to both input terminals without disturbing the performance of an op-amp.
- For 741C is the range of  $\pm 13$  mV.

# Review of data sheet of an op-amp (Cont.)

## 8. Common-mode rejection ratio (CMRR):

- For 741C, CMRR is typically 90 dB.  $R_S \leq 10\text{ K}\Omega$ .
- The higher the value of CMRR, better is the matching between 2 input terminals and smaller the output common-mode voltage.

## 9. Supply Voltage rejection ratio:

- The change in op-amp's input offset voltage due to variations in supply voltage is called supply voltage rejection ratio.
- Some manufacturer use the term like power supply rejection ratio (PSRR) or power supply sensitivity (PSS).
- For 741C,  $\text{SVRR} = 150\text{ }\mu\text{V}/\text{V}$

# Review of data sheet of an op-amp (Cont.)

## 10. Large signal voltage gain:

- Voltage gain =  $\frac{\text{Output voltage}}{\text{differential input voltage}}$
- Since amplitude of output of voltage is much larger than differential input voltage.
- The voltage gain is large signal voltage gain.
- For 741C, typical value is 2,00,000. under the test condition  $R_L \geq 2\text{ K}\Omega$

## 11. Output voltage swing:

- The output voltage swing indicates the value of positive and negative saturation voltage of an op-amp, and never exceeds the supply voltage  $V^+$  and  $V^-$ .
- For 741C, the output voltage swing is guaranteed to be between +13 V and -13 V for  $R_L \geq 2\text{ K}\Omega$

# Review of data sheet of an op-amp (Cont.)

## 12. Output resistance:

- Output resistance  $R_o$  is the resistance measured between the output terminal of the op-amp and the ground.
- It is  $75\ \Omega$  for the 741C op-amp.

## 13. Output short circuit current:

- This is the current that may flow if an op-amp gets shorted accidentally.
- The short circuit current  $I_{SC}$  for 741C is 25 mA.
- This means that the built in short circuit protection is guaranteed to withstand 25 mA of current.

## 14. Supply current:

- Supply current  $I_S$  is the current drawn by op-amp from the power supply.
- It is 2.8 mA for 741C.

# Review of data sheet of an op-amp (Cont.)

## 15. Power consumption:

- This gives the amount of quiescent power ( $v_i = 0\text{ V}$ ) that must be consumed by the op-amp so as to operate properly.
- It is 85 mW for 741C.

## 16. Transient response:

- Rise time overshoot (go past can intended stopping or turning point) are 2 characteristic of the transient response of any circuit.
- For 741C, rise time is 0.3  $\mu\text{sec}$ , and overshoot is 5%.

## 17. Slew rate:

- Op-amp 741C has a low slew rate ( $0.5\text{ V}/\mu\text{s}$ ) and therefore can not be used for high frequency application

# **DC Characteristics of Op-amp**



# DC Characteristics of op-amp:


An ideal op-amp draws no current from the source and Its response is also independent of temperature.

- But a real op-amp does not work this way.
- Current is taken from the input source into the op-amp inputs.
- Two inputs responds differently to current and voltage due to mismatch in transistor
- A real op-amp also shifts its operation with temperature
- The non –ideal dc characteristics that add error components to the dc output voltage are:
  1. Input bias current
  2. Input offset current
  3. Input offset voltage
  4. Thermal drift

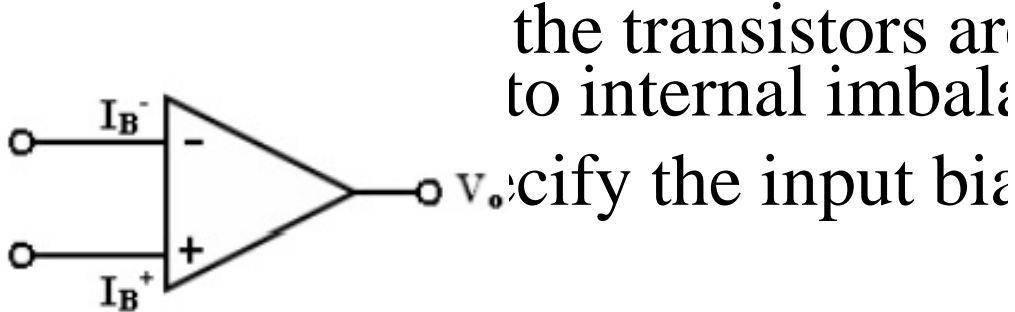
# Input bias current

The op-amp's input is differential amplifier, which may be made of BJT or FET.

- In an ideal op-amp, we assumed that no current is drawn from the input terminals.
- The base currents entering into the inverting and non-inverting terminals ( $I_B^-$  &  $I_B^+$  respectively).



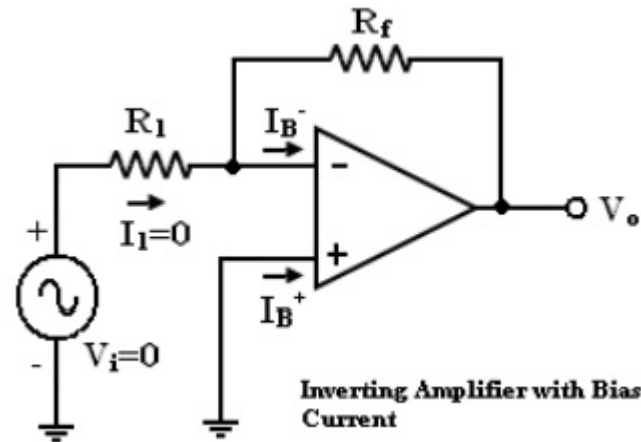the transistors are  
to internal imbalance  
specify the input bias



are not  
outputs.


# Input offset current

Bias current compensation will work if both bias currents  $I_{B^+}$  and  $I_{B^-}$  are equal.

Since the input transistor cannot be made identical. There will always be some small difference between  $I_{B^+}$  and  $I_{B^-}$ . This difference is called the offset current

$$|I_{os}| = I_{B^+} - I_{B^-}$$

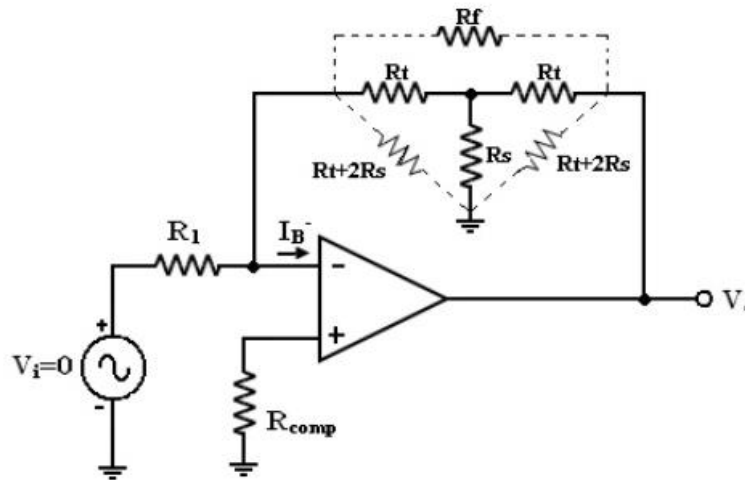Offset current  $I_{os}$  for BJT op-amp is 200nA and for FET op-amp is 10pA. Even with bias current compensation, offset current will produce an output voltage when  $V_i = 0$ .



$$V_1 = I_B^+ R_{comp}$$

And  $I_1 = V_1/R_1$

KCL at node 'a' gives,

Again

$$V_o = I_2 R_f - V_1$$

$$V_o = I_2 R_f - I_B^+ R_{comp}$$

$$V_o = 1M \Omega \times 200nA$$

$$V_o = 200mV \text{ with } V_i = 0$$

$R_1$  large, the feedback resistor  $R_f$  must also be high. So as to obtain reasonable gain.

The T-feedback network is a good solution. This will allow large feedback resistance, while keeping the resistance to ground low (in dotted line).



The T-network provides a feedback signal as if the network were a single feedback resistor.

# Input offset voltage

In Spite of the use of the above compensating techniques, it is found that the output voltage may still not be zero with zero input voltage [ $V_o \neq 0$  with  $V_i = 0$ ].

This is due to unavoidable imbalances inside the op-amp and one may have to apply a small voltage at the input terminal to make output ( $V_o$ ) = 0.

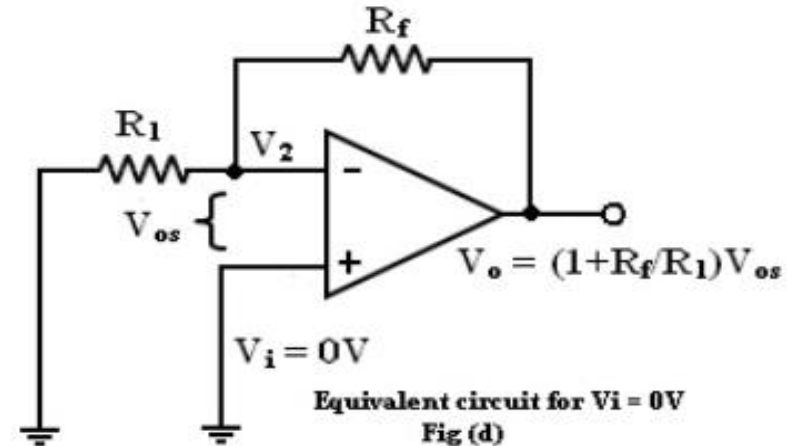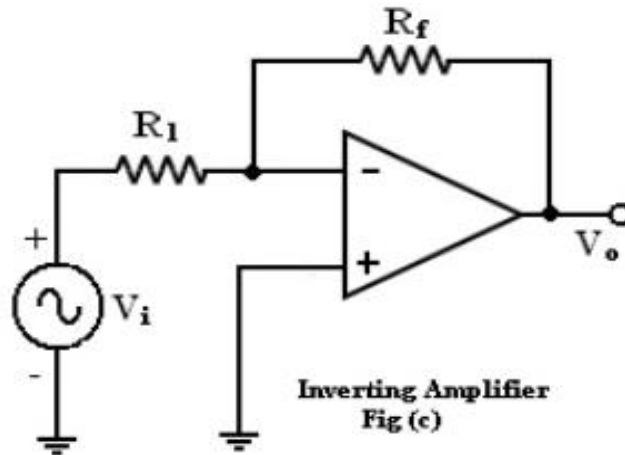This voltage is called input offset voltage  $V_{os}$ . This is the voltage required to be applied at the input for making output voltage to zero ( $V_o = 0$ ).






# Total output offset voltage

The total output offset voltage VOT could be either more or less than the offset voltage produced at the output due to input bias current ( $I_B$ ) or input offset voltage alone ( $V_{os}$ ).

This is because  $I_B$  and  $V_{os}$  could be either positive or negative with respect to ground. Therefore the maximum offset voltage at the output of an inverting and non-inverting amplifier (figure b, c) without any compensation technique used is given by many op-amp provide offset compensation pins to nullify the offset voltage.

10K potentiometer is placed across offset null pins 1&5. The wiper is connected to the negative supply at pin 4.

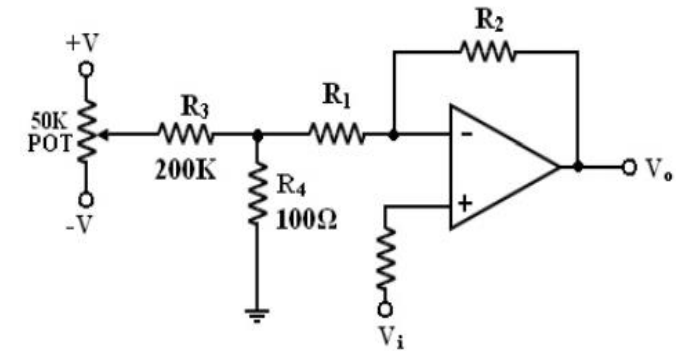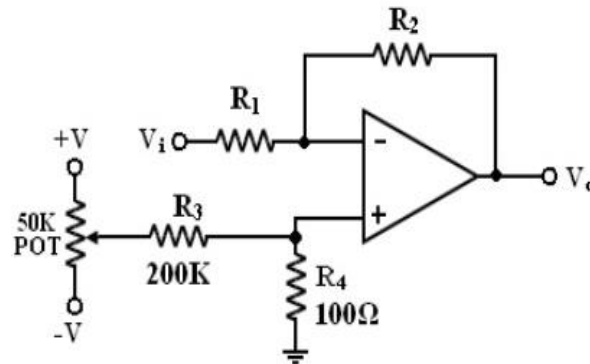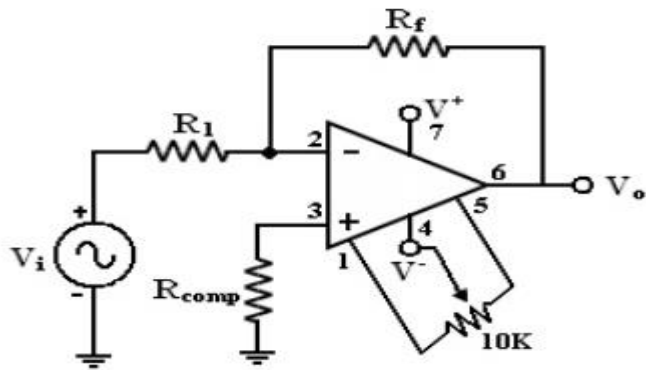The position of the wiper is adjusted to nullify the offset voltage



# Thermal drift

Bias current, offset current, and offset voltage change with temperature

A circuit carefully nulled at 25°C may not remain. So when the temperature rises to 35°C. This is called drift.

Offset current drift is expressed in nA/°C.

These indicate the change in offset for each degree Celsius change in temperature.

# AC Characteristics of Op-amp



# AC Characteristics

- For small signal sinusoidal applications, ac characteristics of op-amp should be known:
  1. Frequency response
  2. Slew rate

# I. Frequency response

- Ideally, an op-amp should have infinite bandwidth i.e., gain of op-amp remains same for frequencies.
- The practical op-amp gain decreases at higher frequencies.
- The reason for gain roll-off is due to the capacitive component in the equivalent circuit of op-amp.
- The capacitance is due to the physical characteristics of the device (BJT or FET) used and internal construction of op-amp.
- For an op-amp with only one break frequency, all the capacitors effect can be represented by single capacitor  $C$  as shown in figure.
- There is one pole  $R_o C$  and one -20dB/decade roll-off comes into effect.

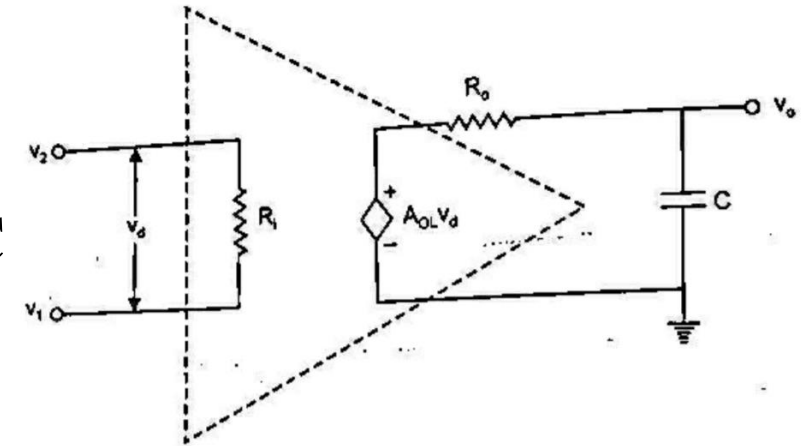


Fig 1: High frequency model of op-amp with single corner frequency.

- The open loop voltage gain of an op-amp with only one corner frequency is obtained from figure 1.

$$v_o = \frac{-jX_c}{R_o - jX_c} A_{OL} v_d$$

$$A = \frac{v_o}{v_d} = \frac{A_{OL}}{1 + j2\pi f R_o C}$$

$$A = \frac{A_{OL}}{1 + j(f/f_1)}$$

where

$$f_1 = \frac{1}{2\pi R_o C}$$

- The magnitude and phase angle of open loop voltage gain are:

$$|A| = \frac{A_{OL}}{\sqrt{1 + (f/f_1)^2}}$$

$$\phi = -\tan^{-1}(f/f_1)$$

- The magnitude and phase responses are shown in figure 2.
1. For frequency  $f \ll f_1$ , the magnitude of gain is  $20 \log A_{OL}$  in dB.
  2. At frequency  $f = f_1$ , the gain is 3dB down the dc value of  $A_{OL}$ . The frequency  $f_1$  is called corner frequency.
  3. For  $f \gg f_1$ , the gain rolls – off at the rate of  $-20\text{dB/decade}$  or  $-6\text{dB/octave}$ .

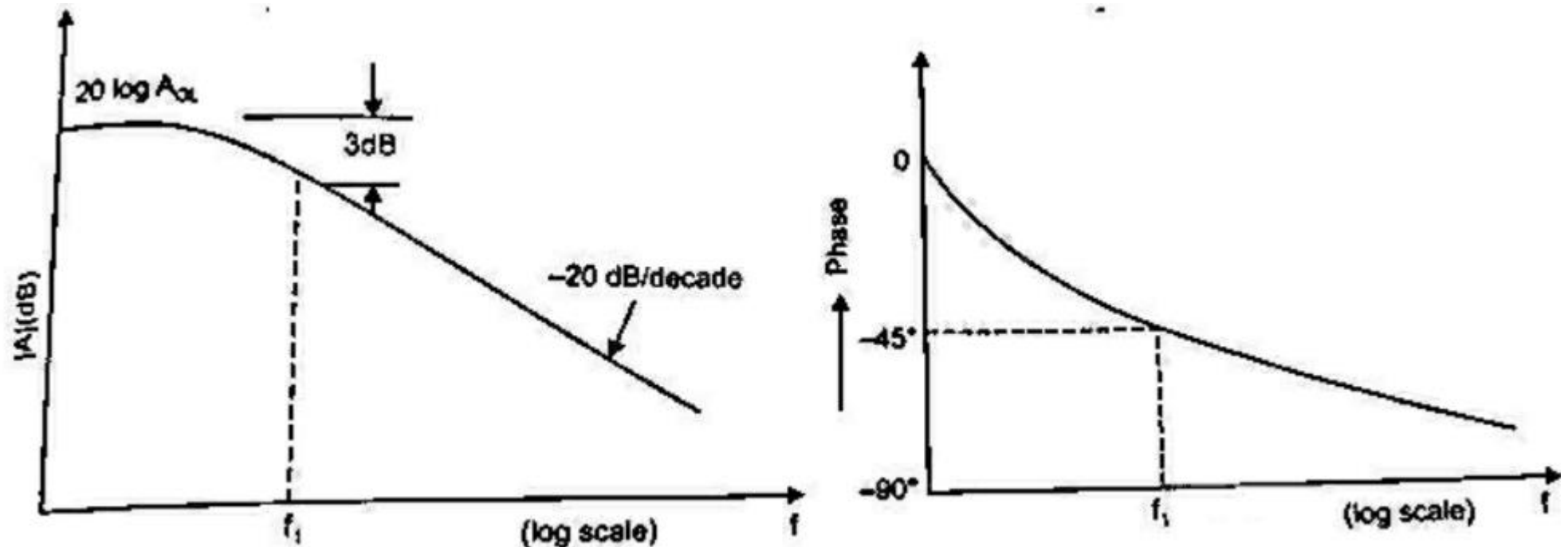


Fig 2: Open loop magnitude and phase characteristics for an op-amp with single break frequency

- The phase angle is zero at frequency  $f=0$ .
- At corner frequency, the phase angle is -45 degrees and at infinite frequency the phase angle is -90 degrees.
- The voltage transfer function in s-domain can be written as:


$$A = \frac{A_{OL}}{1 + j(f/f_1)} = \frac{A_{OL}}{1 + j(\omega/\omega_1)}$$

$$= \frac{A_{OL} \cdot \omega_1}{j\omega + \omega_1} = \frac{A_{OL} \cdot \omega_1}{s + \omega_1}$$

- A practical op-amp, has number of stages and each stage produces a capacitive component. Thus there will be different break frequencies due to number of RC pole pairs. The transfer function of an op-amp with three break frequencies:

- $$A = \frac{A_{OL}}{(1+j\frac{f}{f_1})(1+j\frac{f}{f_2})(1+j\frac{f}{f_3})}; 0 < f_1 < f_2 < f_3$$

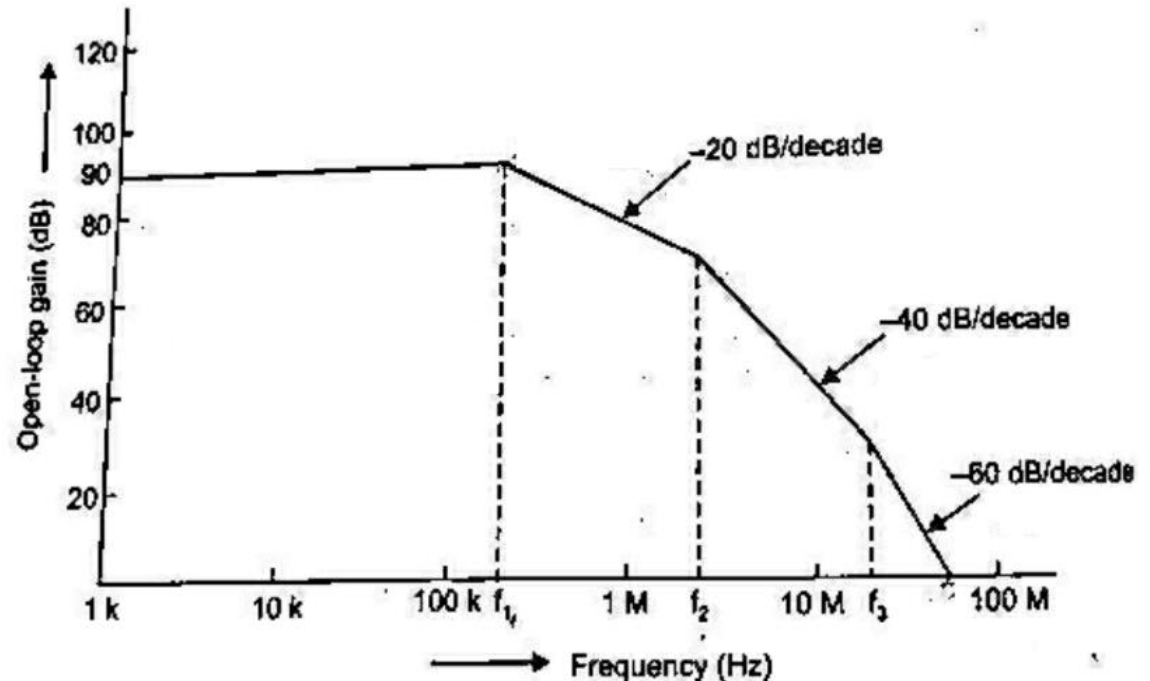Transfer function:  $A = \frac{A_{OL}\omega_1\omega_2\omega_3}{(s+\omega_1)(s+\omega_2)(s+\omega_3)}$  with  $0 < \omega_1 < \omega_2 < \omega_3$



## II. Stability of an Op-Amp

- Op-amps are rarely used in open loop configurations because of its high gain. The feedback affects the frequency response.
- Consider an op-amp amplifier using resistive feedback as shown in figure.
- Using the concept of negative feedback, the closed loop transfer function is:


$$A_{CL} = \frac{A}{1 + A\beta}, \text{ where } A \text{ is open loop voltage gain and } \beta \text{ is feedback ratio.}$$

- If  $(1 + A\beta) = 0$ , the circuit becomes unstable with sustained oscillations.

$$1 + A\beta = 0$$

$$\text{Or } 1 - (-A\beta) = 0 \Rightarrow -A\beta = 1$$

- $|A\beta| = 1$  and  $\angle -A\beta = 0$  or  $\angle A\beta = \pi$ .

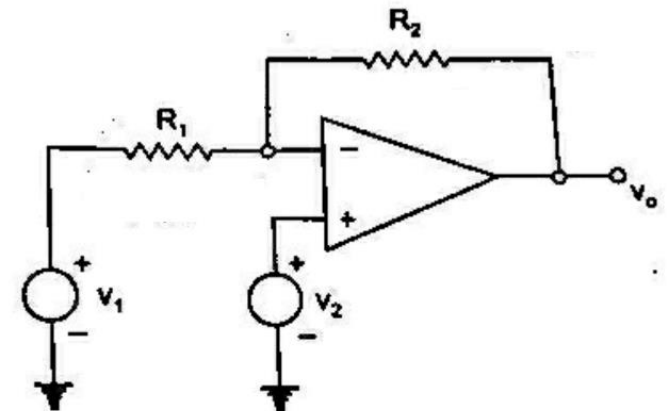

- Since op-amp is connected in inverting mode, it provides a phase shift of 180 degrees at low frequencies.
- At high frequencies, due to each corner frequency, an additional phase shift of maximum -90 degrees can take place in open loop gain A. For two corner frequencies, a maximum of phase shift associated with gain A is -180 degrees.
- Thus, at high frequencies, for some value of  $\beta$ , the magnitude of  $A\beta$  becomes unity when A has an additional phase shift of 180 degrees making total phase shift zero.
- Then the amplifier oscillates leading to instability.
- The condition for instability means unbounded output i.e.,

$$(1 + A\beta) < 1 \text{ or } A\beta < 0$$



### III. Frequency Compensation

- For larger bandwidth and lower closed loop gain, suitable compensation techniques are used. Two types of compensation provided: (1) External (2) Internal

#### (1) External frequency compensation

The compensating network alters the open loop gain so that the roll-off is -20 dB/decade over a wide range of frequencies.

##### 1.1 Dominant pole compensation

Let  $A$  be the uncompensated transfer function of an op-amp.

$$A = \frac{A_{ol}\omega_1\omega_2\omega_3}{(s + \omega_1)(s + \omega_2)(s + \omega_3)}$$


Introduce a dominant pole by adding RC network in series with op-amp.

The compensated transfer function is:

$$A' = \frac{v_o}{v_i} = A \cdot \frac{\frac{-j}{\omega C}}{R - \frac{j}{\omega C}} = \frac{A}{1 + j\frac{f}{f_d}}$$

where

$$f_d = \frac{1}{2\pi RC}$$

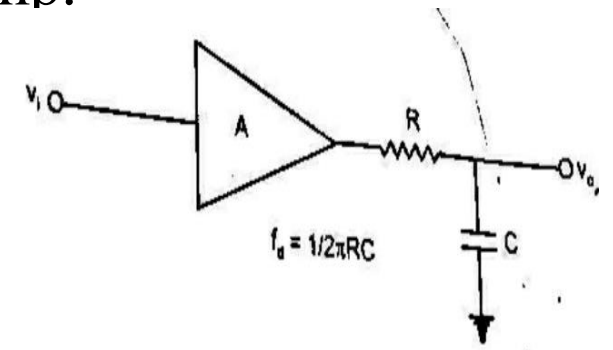


- Therefore

$$A' = \frac{A_{OL}}{\left(1 + j\frac{f}{f_d}\right)\left(1 + j\frac{f}{f_1}\right)\left(1 + j\frac{f}{f_2}\right)\left(1 + j\frac{f}{f_3}\right)}$$

$$f_d < f_1 < f_2 < f_3,$$

- Usually  $f_d$  is selected so that the compensated transfer function  $A$  passes through 0dB at the pole  $f_1$  of uncompensated  $A$ .
- The frequency  $f_d$  can be found graphically by having  $A'$  pass through 0dB at  $f_1$  with a slope of -20dB/dec. The value of  $C$  is calculated as
 
$$f_d = \frac{1}{2\pi RC}$$
- The disadvantage is that it reduces the open loop bandwidth drastically.

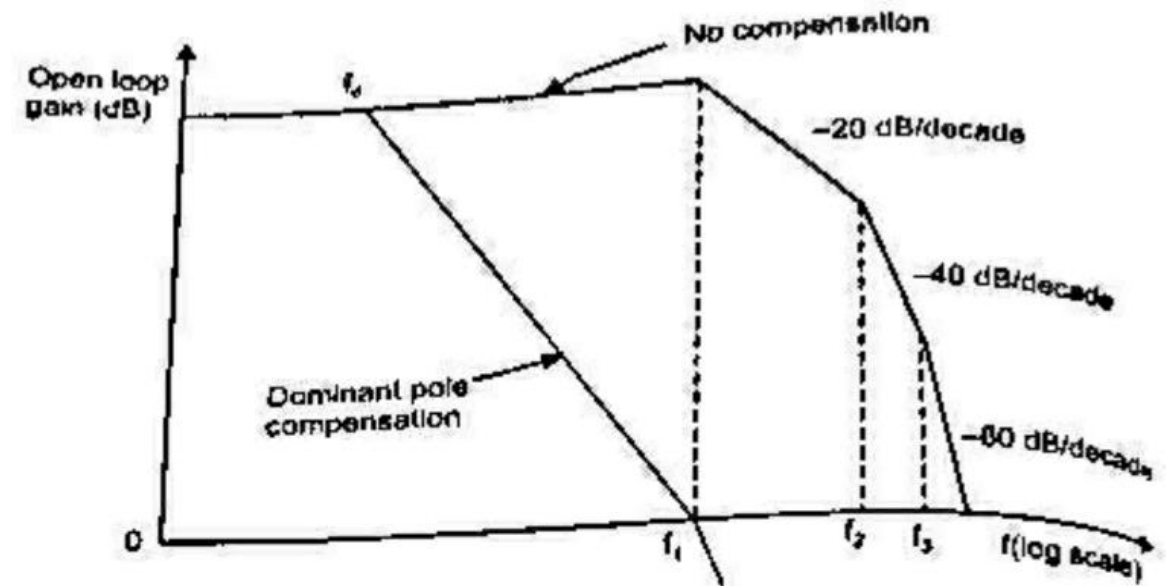


## 1.2 Pole zero compensation

- The uncompensated transfer function is altered by adding both pole and a zero.
- The zero should be at higher frequency than pole
- For the compensating network,

$$\frac{v_o}{v_2} = \frac{Z_2}{Z_1 + Z_2} = \frac{R_2}{R_1 + R_2} \frac{1 + j \frac{f}{f_1}}{1 + j \frac{f}{f_o}}$$

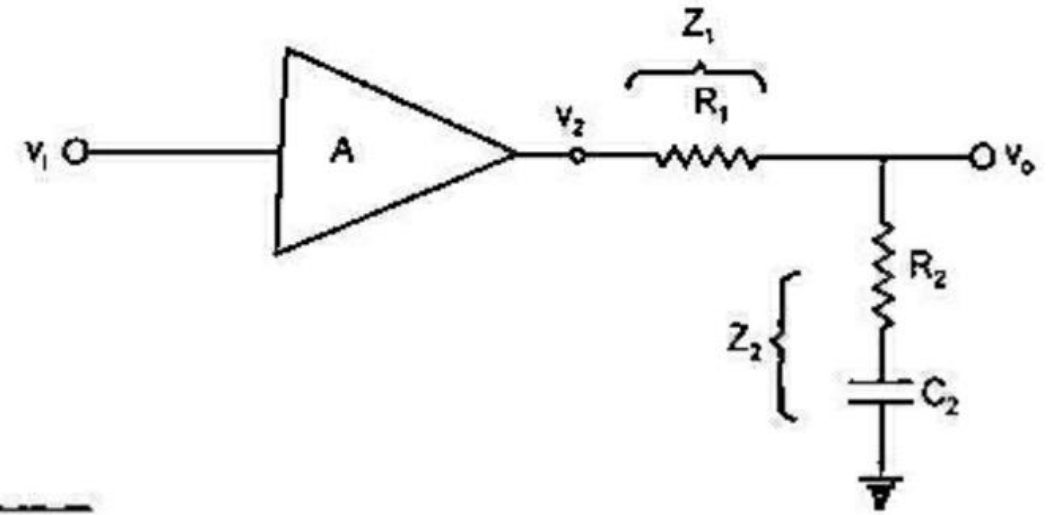
$$\text{where } Z_1 = R_1, Z_2 = R_2 + \frac{1}{j\omega C_2}, f_1 = \frac{1}{2\pi R_2 C_2}, f_o = \frac{1}{2\pi(R_1 + R_2)C_2}$$




- The compensating network is designed to produce a zero at the first corner frequency  $f_1$  of the uncompensated transfer function  $A$ . The zero will cancel the effect of the pole at  $f_1$ .

- The pole of the compensating network at  $f'_0$  is selected so that the compensated transfer function  $A'$  passes through 0dB at the second corner frequency  $f_2$  of the uncompensated transfer function  $A$ .
- The frequency can be found graphically by having  $A'$  passes through 0dB at  $f_2$  with a slope of -20dB/dec. Assuming the compensating network doesn't load the amplifier i.e.,  $R_2 \gg R_1$ , then

$$\begin{aligned}
 A' &= \frac{v_o}{v_i} = \frac{v_o}{v_2} \cdot \frac{v_2}{v_i} = A \cdot \frac{R_2}{R_1 + R_2} \cdot \frac{1 + j\frac{f}{f_1}}{1 + j\frac{f}{f_0}} \\
 &= \frac{A_{OL}}{\left(1 + j\frac{f}{f_1}\right)\left(1 + j\frac{f}{f_2}\right)\left(1 + j\frac{f}{f_3}\right)} \cdot \frac{R_2}{R_1 + R_2} \cdot \frac{1 + j\frac{f}{f_1}}{1 + j\frac{f}{f_0}} \\
 &= \frac{A_{OL}}{\left(1 + j\frac{f}{f_0}\right)\left(1 + j\frac{f}{f_2}\right)\left(1 + j\frac{f}{f_3}\right)} \\
 &\quad 0 < f_0 < f_1 < f_2 < f_3
 \end{aligned}$$

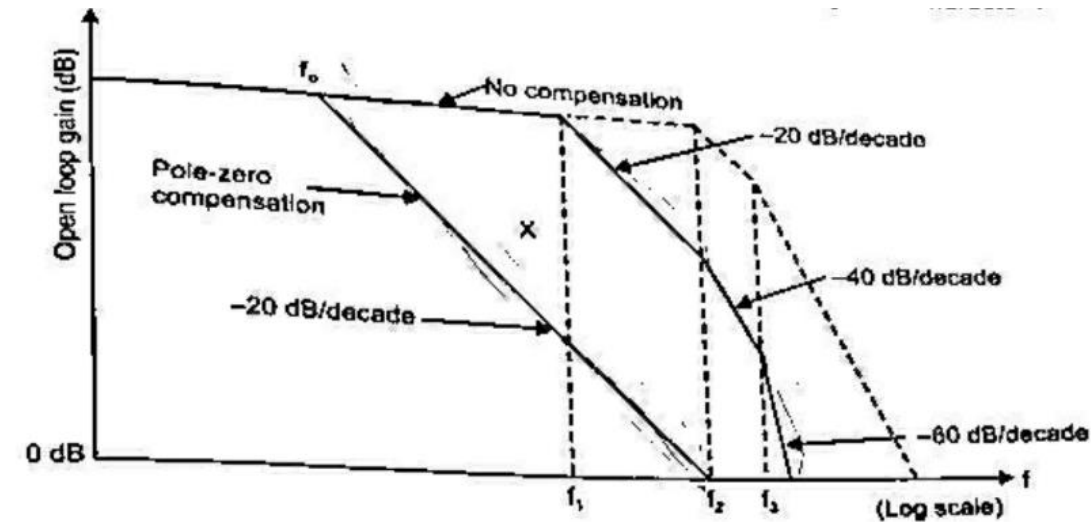


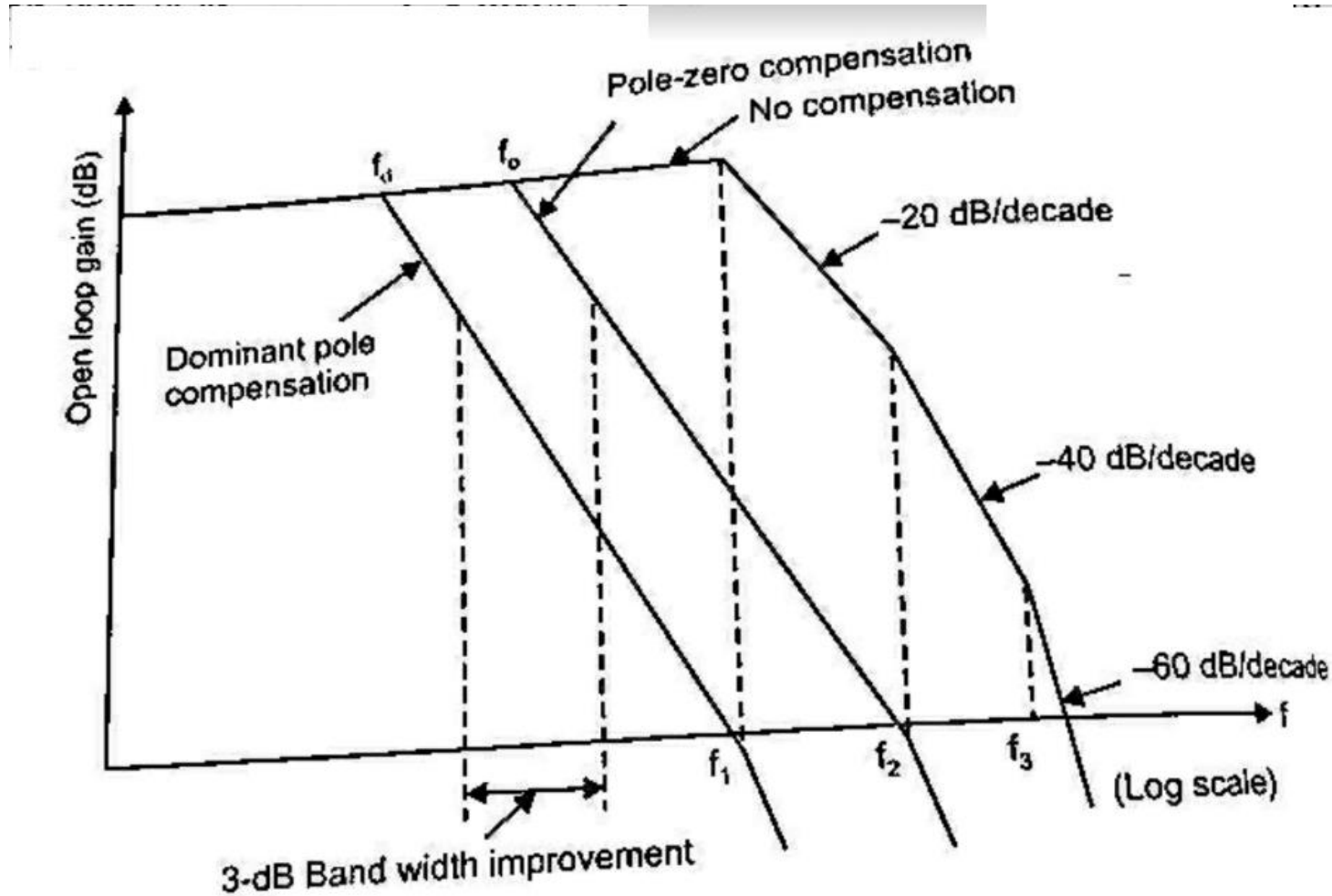- The improvement in bandwidth due to pole-zero compensation is given by  $f_2 - f_1$


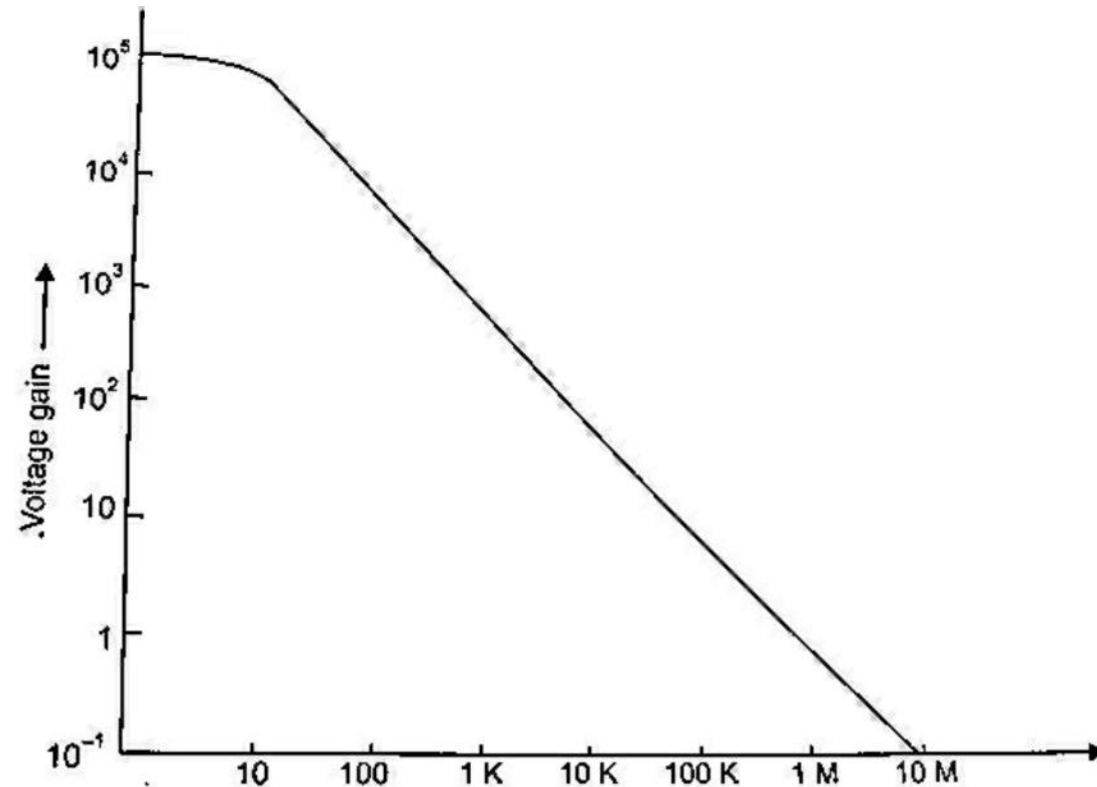
## (2) Internal compensated op-amp

- For certain applications, the relatively broad bandwidth of uncompensated op-amp is not needed.
- For eg. in instrumentation circuit the op-amp is required to amplify relatively slow changing signals. It doesn't require good high frequency response. For such applications, internally compensated op-amps are used.
- $\mu A741$  contains a capacitance of 30pF that internally shunts off signal current and thus reduces the available output signal at higher frequency.
- This internal compensating capacitor causes the open loop gain to roll-off at  $-20\text{dB/dec}$  and thus assures a stable circuit.



## IV. Slew rate

- The rise time of an amplifier is defined as the time of output takes to change from 10%-90% of the final value for a step input.
- Ideal response time should be zero i.e. output voltage respond instantaneously to any change in input.
- For large signal output, the op-amp's speed is limited by Slew rate, that measure how quickly an op-amp respond to changes in the input voltage.
- Op-amp slew rate is related to its frequency response. Op-amps with wider bandwidth have better slew rate.
- *Slew rate is defined as the maximum rate of change of output voltage caused by a step input voltage and is specified in  $V/\mu s$ .*
- An ideal SR is infinity and practical value is  $0.1 V/\mu s$  to  $1000 V/\mu s$ .
- The SR improves with higher closed loop gain and dc supply voltage. It also decreases with increase in temperature.

### *Causes of Slew rate*

- The capacitor used within or outside an op-amp to prevent oscillator. This capacitor prevents the output voltage from responding immediately to a fast changing input.
- The rate at which the voltage across the capacitor  $V_c$  increases is given by  $\frac{dv_c}{dt} = \frac{I}{C}$
- $I$  is the maximum current furnished by op-amp to the capacitor  $C$ .
- For obtaining faster slew rate, op-amp should have either higher current or small compensating capacitor.

$$SR = \left. \frac{dv_c}{dt} \right|_{\max} = \frac{I_{\max}}{C} = \frac{15 \mu A}{30 \text{ pF}} = 0.5 \text{ V}/\mu s$$



### *Slew rate for Sine wave*

SR limits the response speed of all large signal waveshapes.


Consider a voltage follower

$$v_s = V_m \sin \omega t$$

$$v_o = V_m \sin \omega t$$

The rate of change of output is given by  $\frac{dv_o}{dt} = V_m \omega \cos \omega t$

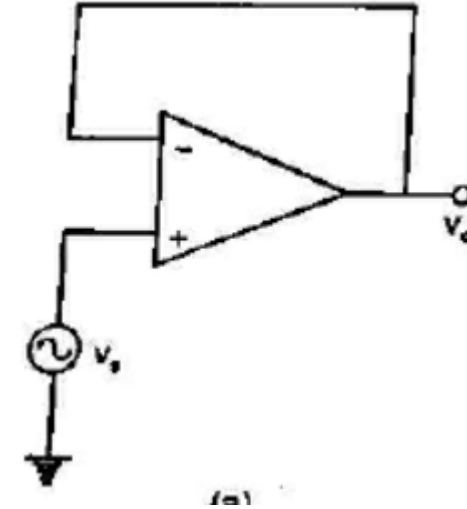The maximum rate of change of output occurs when  $\cos \omega t = 1$ .



$$SR = \left. \frac{dv_o}{dt} \right|_{\max} = \omega V_m$$

Therefore, Slew Rate =  $2\pi f V_m$  V/s

$$= \frac{2\pi f V_m}{10^6} \text{ V}/\mu\text{s}$$

$f$  = input frequency (Hz),

$V_m$  = peak output amplitude

$f_{\max}$  is the maximum frequency at which we obtain undistorted output voltage of peak value  $V_m$  is given by

$$f_{\max} \text{ (Hz)} = \frac{\text{Slew Rate}}{6.28 \times V_m} \times 10^6$$

$f_{\max}$  is the full power response