

**S. Kunal Keshan**  
**RA2011004010051**


**ECE – A**

**Control Systems –**  
**18ECS201T**

ASSIGNMENT - I


S KUNAL KESHAN  
RA2011004010051  
ECE - A.

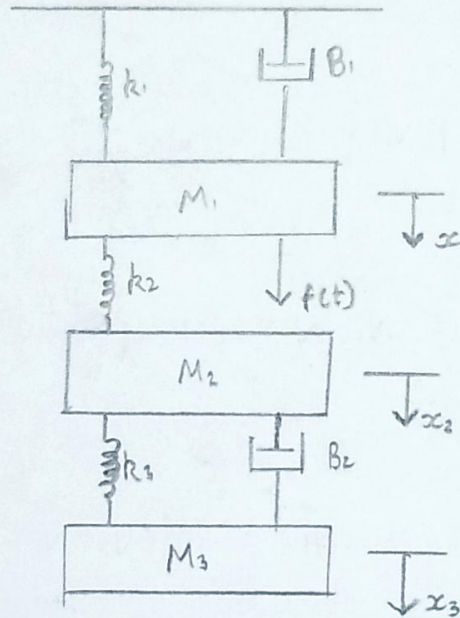1. Write the differential equations governing the mechanical system in Force - Voltage and Force - Current analogy.




Soln. Given System is a Mechanical Translational System, where the number of nodes = 3.

Free body diagram for each node is,

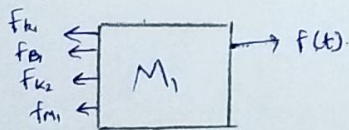


$$f(t) = M_1 \frac{d^2 x_1(t)}{dt^2} + K_1 x_1(t) + B_1 \frac{dx_1(t)}{dt} + K_2 (x_1(t) - x_2(t)).$$

- (1)

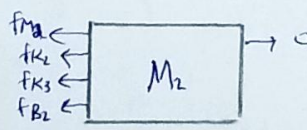

$$0 = M_2 \frac{d^2 x_2(t)}{dt^2} + K_2 (x_2(t) - x_1(t)) + K_3 (x_2(t) - x_3(t)) + B_2 \frac{d}{dt} (x_2(t) - x_3(t)).$$

- (2)

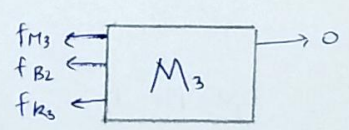

$$0 = M_3 \frac{d^2 x_3(t)}{dt^2} + B_2 \frac{d}{dt} (x_3(t) - x_2(t)) + K_3 (x_3(t) - x_2(t)).$$

- (3)

In eqs (1), (2), and (3) can be rewritten as,

$$\frac{d^2 x}{dt^2} = \frac{dv}{dt},$$

$$\frac{dx}{dt} = v, \text{ and}$$

$$x = \int v dt.$$

(1) becomes,

$$f(t) = M_1 \frac{dv_1}{dt} + B_1 v_1 + K_1 \int v_1 dt + K_2 \int (v_1 - v_2) dt$$

(2) becomes,

$$0 = M_2 \frac{dv_2}{dt} + B_2 (v_2 - v_3) + K_2 \int (v_2 - v_1) dt + K_3 \int (v_2 - v_3) dt$$

(3) becomes,

$$0 = M_3 \frac{dv_3}{dt} + B_2 (v_3 - v_2) + K_3 \int (v_3 - v_2) dt.$$

Converting the above equations to Force - Voltage Analogy:


$$f(t) \rightarrow e(t).$$

$$B_1, B_2 \rightarrow R_1, R_2$$

$$K_1, K_2, K_3 \rightarrow 1/C_1, 1/C_2, 1/C_3$$

$$M_1, M_2, M_3 \rightarrow L_1$$
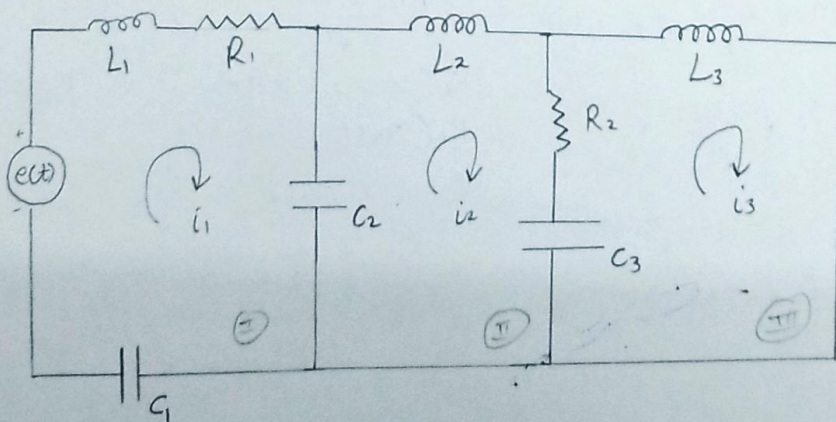
$$v_1, v_2, v_3 \rightarrow i_1, i_2, i_3$$





By applying KVL, across all three meshes, we get  
In mesh (I)

$$e(t) = L_1 \frac{di_1}{dt} + R_1 i_1 + \frac{1}{C_1} \int i_1 \cdot dt + \frac{1}{C_2} \int (i_1 - i_2) \cdot dt \quad \text{--- (4)}$$

In mesh (II)

$$0 = L_2 \frac{di_2}{dt} + \frac{1}{C_2} \int (i_2 - i_1) dt + R_2 (i_2 - i_3) + \frac{1}{C_3} \int (i_2 - i_3) \cdot dt \quad \text{--- (5)}$$

In mesh - III

$$0 = L_3 \frac{di_3}{dt} + \frac{1}{C_3} \int (i_3 - i_2) dt + R_2 (i_3 - i_2) \quad \text{--- (6)}$$

Comparing Equations (1), (2), (3) and (4), (5), (6) we get the Force-Voltage Analogy.

Converting the Force equations to Force - Current analogy.

$$f(t) \rightarrow i(t)$$


$$M_1, M_2, M_3 - C_1, C_2, C_3$$

$$B_1, B_2, B_3 - 1/R_1, 1/R_2, 1/R_3$$

$$K_1, K_2, K_3 - 1/L_1, 1/L_2, 1/L_3$$

$$V_1, V_2, V_3 - v_1, v_2, v_3$$

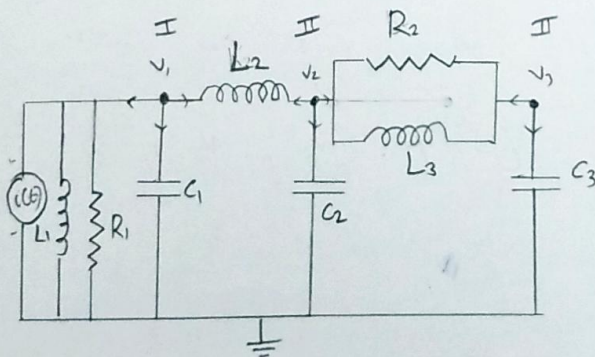(velocity)                      (voltage)



Applying KCL across all nodes we get.

In node (I).

$$i(t) = C_1 \frac{dv_1}{dt} + \frac{v_1}{R_1} + \frac{1}{L_1} \int v_1 dt + \frac{1}{L_2} \int (v_1 - v_2) dt \quad - (7)$$

In node (II)


$$0 = C_2 \frac{dv_2}{dt} + \frac{1}{L_2} \int (v_2 - v_1) dt + \frac{v_2 - v_3}{R_2} + \frac{1}{L_3} \int (v_2 - v_3) dt \quad - (8)$$

In node (III)

$$0 = C_3 \frac{dv_3}{dt} + \frac{v_3 - v_2}{R_2} + \frac{1}{L_3} \int (v_3 - v_2) dt \quad - (9)$$


Comparing Eqs (1), (2), (3) and (7), (8), (9) we get the Force-Current analogy.

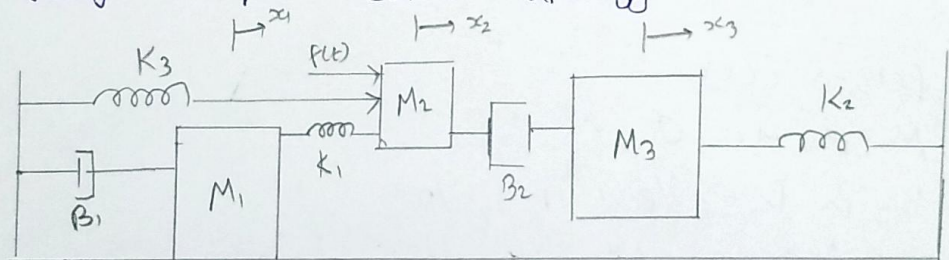2. Obtain the mathematical model of the mechanical system in Force Voltage and Force Current analogy.




Soln. No of nodes = 3.  $\therefore$  no of equations = 3.

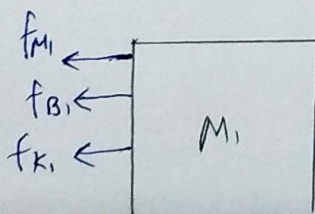Free body diagram of each node is given as.



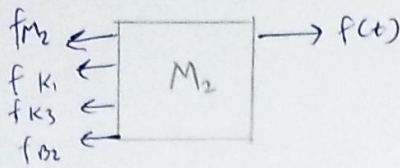
$$0 = M_1 \frac{d^2 x_1}{dt^2} + B_1 \frac{dx_1}{dt} + K_1 (x_1 - x_2) \quad - (1)$$




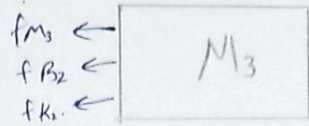
$$f(t) = M_2 \frac{d^2 x_2}{dt^2} + K_3 x_2 + K_1 (x_2 - x_1) + B_2 \frac{d}{dt} (x_2 - x_3) \quad \text{--- (2)}$$



$$0 = M_3 \frac{d^2 x_3}{dt^2} + K_2 x_3 + B_2 \frac{d}{dt} (x_3 - x_2) \quad \text{--- (3)}$$

Eqs ①, ② and ③ can be rewritten as.

① becomes.

$$0 = M_1 \frac{dv_1}{dt} + B_1 v_1 + K_1 \int (v_1 - v_2) dt$$

② becomes.

$$f(t) = M_2 \frac{dv_2}{dt} + K_3 \int v_2 dt + K_1 \int (v_2 - v_1) dt + B_2 (v_2 - v_3)$$

③ becomes.

$$0 = M_3 \frac{dv_3}{dt} + K_2 \int v_3 dt + B_2 (v_3 - v_2)$$

Converting the above equations to force-voltage analogy.


$$M_1, M_2, M_3 - L_1, L_2, L_3$$

$$B_1, B_2 - R_1, R_2$$

$$K_1, K_2, K_3 - 1/C_1, 1/C_2, 1/C_3$$

$$f(t) - Q(t)$$

$$v_1, v_2, v_3 - i_1, i_2, i_3$$

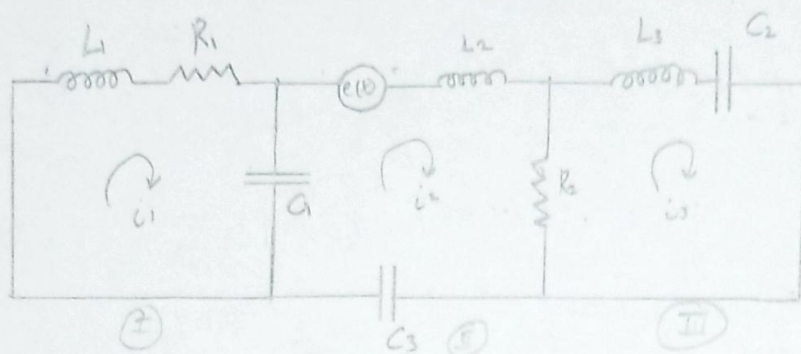

Applying KVL to all the meshes, we get.  
In Mesh (I).

$$0 = L_1 \frac{di_1}{dt} + R_1 i_1 + \frac{1}{C_1} \int (i_1 - i_2) dt. \quad - (4)$$

In Mesh (II).

$$e(t) = L_2 \frac{di_2}{dt} + \frac{1}{C_3} \int i_2 \cdot dt + \frac{R_2}{R_2} (i_2 - i_3) + \frac{1}{C_1} \int (i_2 - i_1) dt. \quad - (5)$$

In Mesh (III)

$$0 = L_3 \frac{di_3}{dt} + \frac{1}{C_2} \int i_3 \cdot dt + R_2 (i_3 - i_2) \quad - (6)$$

Comparing eqs (1), (2), (3) and (4), (5), (6), we get the force-voltage analogy.

Converting the force equations to Force Current Analogy

$$M_1, M_2, M_3 - C_1, C_2, C_3$$

$$B_1, B_2 - 1/R_1, 1/R_2$$


$$K_1, K_2, K_3 - 1/L_1, 1/L_2, 1/L_3.$$

$$f(t) - i(t).$$

$$V_1, V_2, V_3 - V_1, V_2, V_3$$

(velocity) (voltage).



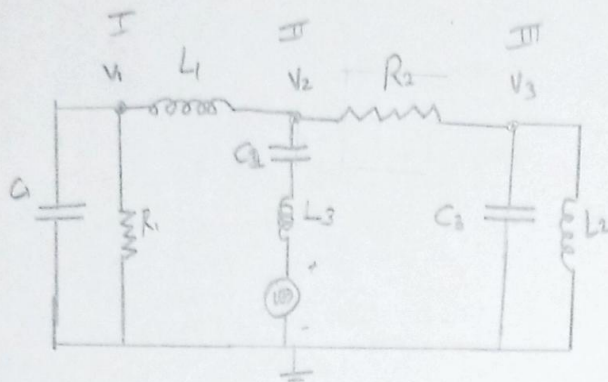

Applying KCL across all 3 nodes, we get.  
in node (I).

$$0 = C_1 \frac{dv_1}{dt} + \frac{v_1}{R_1} + \frac{1}{L_1} \int (v_1 - v_2) dt. \quad \text{--- (7)}$$

In node (II)

$$i(t) = C_2 \frac{dv_2}{dt} + \frac{1}{L_3} \int v_2 dt + \frac{1}{L_1} \int (v_2 - v_1) dt + \frac{1}{R_2} (v_2 - v_3) \quad \text{--- (8)}$$

In node (III)

$$0 = C_3 \frac{dv_3}{dt} + \frac{1}{L_2} \int v_3 dt + \frac{1}{R_2} (v_3 - v_2) \quad \text{--- (9)}$$

Comparing eqs (1), (2), (3) and (7), (8), (9). we get the  
force-current analogy.