
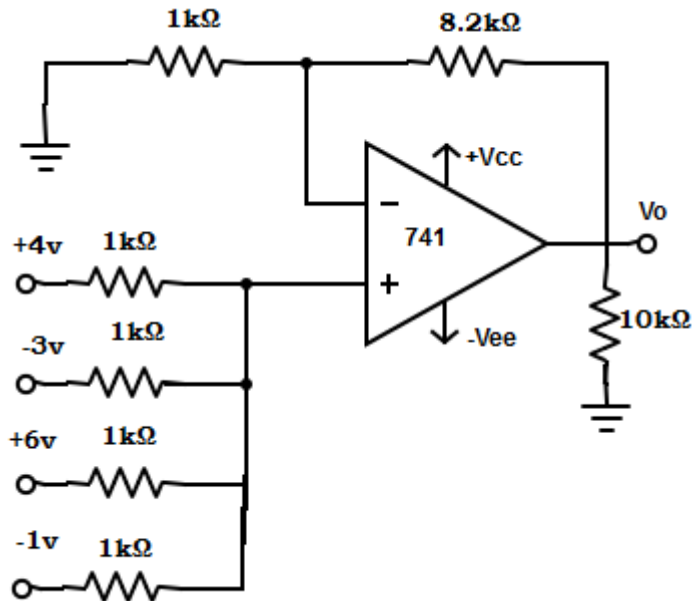


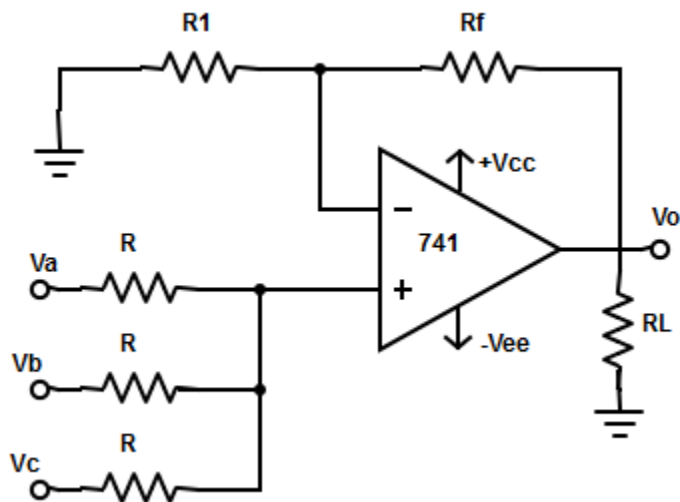1. Find the value of V_1 in the circuit shown below?



Using the superposition theorem the voltage V_1 at non-inverting terminal is $V_1 = V_a/4 + V_b/4 + V_c/4 + V_d/4 = [V_a + V_b + V_c + V_d] / 4 = [4 + (-3) + 6 + (-1)] / 4 = 1.5\text{V}$.

2. In the circuit shown, supply voltage = $\pm 15\text{V}$, $V_a = +3\text{V}$, $V_b = -4\text{V}$, $V_c = +5\text{V}$, $R = R_1 = 1\text{k}\Omega$ and $R_F = 2\text{k}\Omega$. 741 op-amp has $A = 2 \times 10^5$ and $R_i = 10\text{k}\Omega$. Determine the output voltage internal resistance of the circuit?




The output voltage $V_o = [1 + (R_F/R_1)] \times [(V_a + V_b + V_c)/3] = [1 + (2\text{k}\Omega/1\text{k}\Omega)] \times [(3 - 4 + 5)/3] = 2.67 \cong 3\text{V}$.

Internal resistance of circuit, $R_{iF} = R_i [A \times R_1 / (R_1 + R_F)] = 100\Omega \times [(200000 \times 1\text{k}\Omega) / (1\text{k}\Omega + 2\text{k}\Omega)] \Rightarrow R_{iF} = 6.67\text{M}\Omega$.

3. Consider the entire resistors in the bridge circuit are equal. The resistance and change in resistance are given as $3k\Omega$ and $30k\Omega$. Calculate the output voltage of differential instrumentation amplifier?

The output voltage of the circuit is $V_o = -(R_F/R_1) \times (\Delta R/R) \times V_{dc}$
 $= (5.5k\Omega/100\Omega) \times (30k\Omega/3k\Omega) \times 3 = 1.65v$

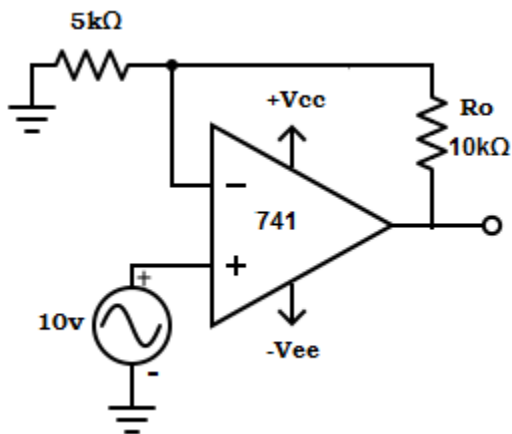4. Given voltage to current converter with floating load. Determine the output current?




Output current, $I_o = V_{in}/R_1 = 10/5k\Omega = 2mA$.

5. Find the gain of the voltage to current converter with grounded load?

In voltage to current converter with grounded load all resistor must be equal in value.
 $\therefore \text{Gain} = V_o/V_{in} = [1 + (R_F/R_1)] = 1 + R/R = 1 + 1 = 2$.

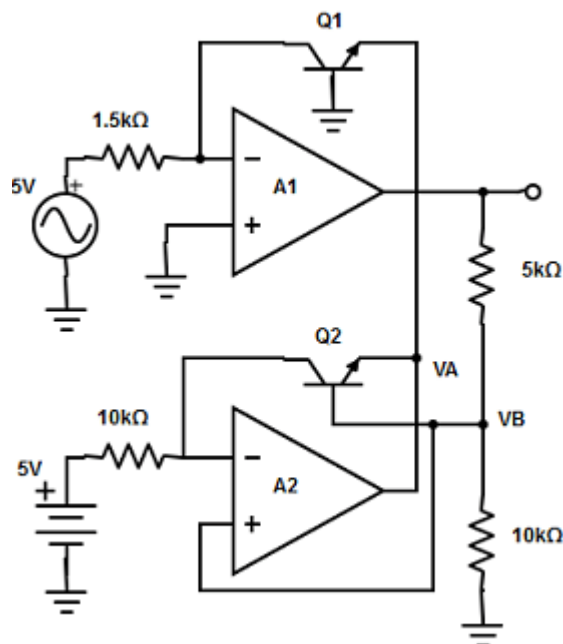6. Calculate the base voltage of Q_2 transistor in the log-amp using two op-amps?



The base voltage of Q_2 transistor, $V_B = [R_{TC} / (R_2 + R_{TC})] \times (V_i) = [10k\Omega / (5k\Omega + 10k\Omega)] \times 5V = 3.33V$.

7. Calculate the phase difference between two input signals applied to a multiplier, if the input signals are $V_x = 2\sin\omega t$ and $V_y = 4\sin(\omega t + \theta)$. (Take $V_{ref} = 12V$).


$$V_o = [V_{mx} \times V_{my} / (2 \times V_{ref})] \times \cos\theta$$

$$\Rightarrow (V_o \times 2 \times V_{ref}) / (V_{mx} \times V_{my}) = \cos\theta$$

$$\Rightarrow \cos\theta = (10 \times 2 \times 12) / (2 \times 4) = 30.$$

$$\Rightarrow \theta = \cos^{-1}30 = 1.019.$$

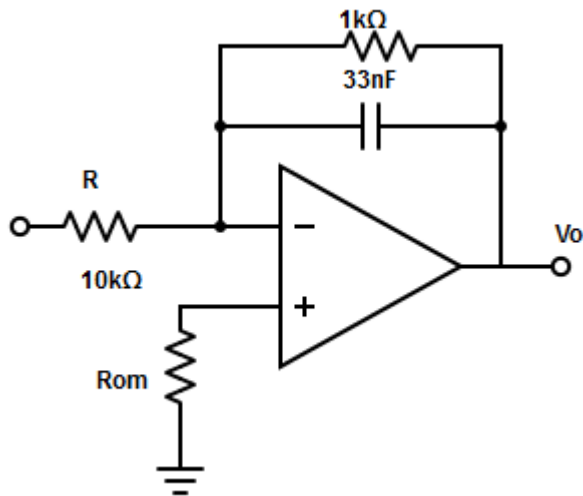8. Determine the lower frequency limit of integration for the circuit given below.



The lower frequency limit of integration, $f = 1 / (2\pi R_F C_F) = 1 / (2\pi \times 1k\Omega \times 33nF) = 4.82kHz$.

9. A sine wave of $1V_{peak}$ at $1000Hz$ is applied to a differentiator with the following specification: $R_F = 1k\Omega$ and $C_1 = 0.33\mu F$, find the output waveform?

Given, $V_{in} = V_p \times \sin\omega t = \sin(2\pi \times 1000)t$

The output of differentiator $V_o = -R_F \times C_1 \times (dV_{in}/dt) = (1k\Omega) \times (0.33\mu F) \times d[\sin 2\pi \times 1000t]/dt$

$$= -3.3 \times 10^{-4} \times 2\pi \times 1000 \times [\cos 2\pi(1000)t] = -2.07 \times [\cos 2\pi(1000)t].$$

10. Calculate the frequency of oscillation for RC phase shift oscillator having the value of R and C as 35Ω and $3.7\mu F$ respectively.

The frequency of oscillation of RC phase shift oscillator is,

$$f_o = 1 / (2\pi RC\sqrt{6}) = 1 / (2 \times 3.14 \times \sqrt{6} \times 3.7\mu F \times 35\Omega)$$

$$\Rightarrow f_o = 1 / 1.9921 \times 10^{-3} = 502Hz.$$

11. Calculate the value of capacitance in wein bridge oscillator, such that $f_o = 1755Hz$ and $R = 3.3k\Omega$.

The frequency of oscillation is given as $f_o = 0.159/RC$

$$\Rightarrow C = 0.159 / R \times f_o = 0.159 / 3.3k\Omega \times 1755Hz$$

$$\Rightarrow C = 0.027\mu F = 0.03\mu F.$$

12. . What will be the frequency of output waveform of a square wave generator if $R_2 = 1.16 R_1$?

When $R_2 = 1.16 R_1$, then $f_o = 1/2RC \times \ln[(2R_1 + R_2) / R_2] = 1/2RC \times \ln[(2R_1 + 1.161R_1) / (1.161R_1)] = 1/(2RC \times \ln 2.700) = 1/2RC$.

13. A square wave oscillator has $f_o = 1\text{kHz}$. Assume the resistor value to be $10\text{k}\Omega$ and find the capacitor value?

Let's take $R_2 = 1.16 R_1$, therefore the output frequency $f_o = 1/2RC$
 $\Rightarrow C = 1/2Rf_o = 1/(2 \times 10\text{k}\Omega \times 1\text{kHz}) = 0.05\mu\text{F}$.

14. Find the capacitor value for a the output frequency, $f_o = 2\text{kHz}$ & $V_o(\text{pp}) = 7\text{v}$, in a triangular wave generator. The op-amp is 1458/741 and supply voltage = $\pm 15\text{v}$. (Take internal resistor = $10\text{k}\Omega$)

Given, $V_{\text{sat}} = 15\text{v}$

$$\therefore V_o(\text{pp}) = (2R_2/R_3) \times V_{\text{sat}}$$

$$\Rightarrow R_2 = (V_o(\text{pp}) \times R_3) / (V_{\text{sat}} \times 2) = [7/(2 \times 15)] \times R_3 = 0.233R_3$$

\therefore Internal resistor, $R_2 = R_1 = 10\text{k}\Omega$


$$\Rightarrow R_3 = 0.233 \times 10\text{k}\Omega = 2.33\text{k}\Omega$$

So, the output frequency $f_o = R_3 / (4 \times R_1 \times C_1 \times R_2)$

$$\Rightarrow 2\text{kHz} = 2.33\text{kHz} / (4 \times 10\text{k}\Omega \times 10\text{k}\Omega \times C_1)$$

$$\Rightarrow C_1 = 2.33\text{k}\Omega / (8 \times 10^{-11}) = 2.9 \times 10^{-9} \cong 3\text{nF}$$

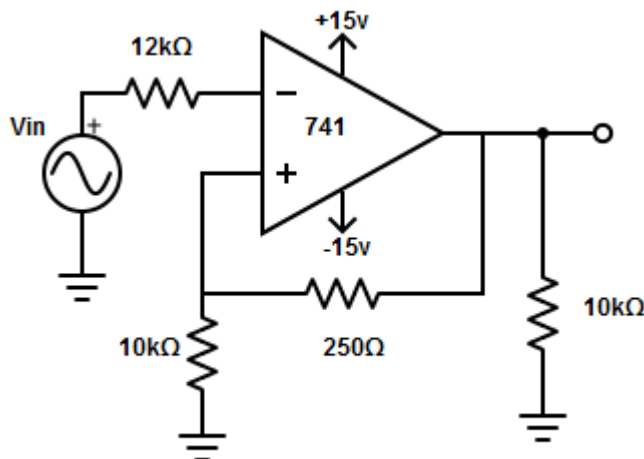14. Determine the upper and lower threshold voltage



Upper threshold voltage, $V_{UT} = [R_1/(R_1 + R_2)] \times (+V_{\text{sat}}) = [10\text{k}\Omega/(10\text{k}\Omega + 250\Omega)] \times (+15\text{v}) = +14.63\text{v}$.

Lower threshold voltage $V_{LT} = [R_1/(R_1 + R_2)] \times (-V_{\text{sat}}) = [10\text{k}\Omega/(10\text{k}\Omega + 250\Omega)] \times (-15\text{v}) = -14.63\text{v}$.

15. Calculate the hysteresis voltage for the schmitt trigger from the given specification:

$R_2 = 56\text{k}\Omega$, $R_1 = 100\Omega$, $V_{\text{ref}} = 0\text{v}$ & $V_{\text{sat}} = \pm 14\text{v}$

Upper threshold voltage, $V_{UT} = [R_1 / (R_1 + R_2)] \times (+V_{sat}) = [100k\Omega / (56k\Omega + 100\Omega)] \times (+14V) = +25mV$.

Lower threshold voltage $V_{LT} = [R_1 / (R_1 + R_2)] \times (-V_{sat}) = [100k\Omega / (56k\Omega + 100\Omega)] \times (-14V) = -25mV$.

\therefore Hysteresis voltage $= V_{UT} - V_{LT} = 25 - (-25) = 50mV$.

16. A monostable multivibrator has $R = 120k\Omega$ and the time delay $T = 1000ms$, calculate the value of C ?

Time delay for a monostable multivibrator, $T = 1.1RC$

$\Rightarrow C = T / (1.1R) = 1000ms / (1.1 \times 120k\Omega) = 7.57\mu F$.

17. Astable multivibrator operating at 150Hz has a discharge time of 2.5ms. Find the duty cycle of the circuit.

Given $f = 150Hz$. Therefore, $T = 1/f = 1/150 = 6.67ms$.

\therefore Duty cycle, $D\% = (t_{Low} / T) \times 100\% = (2.5ms / 6.67ms) \times 100\% = 37.5\%$.

18. Calculate the value of external timing capacitor, if no modulating input signal is applied to VCO. Consider $f_o = 25kHz$ and $R_T = 5k\Omega$.

When modulating input signal is not applied to VCO, the output frequency becomes

$f_o = 1 / (4 \times R_T \times C_T)$

$\Rightarrow C_T = 1 / (4 \times R_T \times f_o) = 1 / (4 \times 5k\Omega \times 25kHz) = 2 \times 10^{-9} = 2nF$.

19. Calculate the voltage to frequency conversion factor, where $f_o = 155Hz$ and $V_{cc} = 10V$.

The voltage to frequency conversion factor, $K_v = \Delta f_o / \Delta V_{cc} = 8 \times f_o / V_{cc} = (8 \times 155) / 10 = 124$.

20.