

21/05/22

(1)

Test - CLAT2 - Answer Key

Course code: MEECS0013 - Analog Electronic Circuits

Year/Sem: D/D

Max marks: 50

Set - A

Part-A: (10x1 = 10) Marks.

1. b) 1.23 V/V
2. a) mobility decreases
3. c) $-g_m R_o / (1 + g_m R_i)$
4. c) Common gate
5. a) coupling capacitor short circuit and load capacitor open circuit
6. b) Error signal
7. b) increases
8. a) Distortion
9. c) High, high
10. b) Oscillator

Part-B: (4x10 = 40) Marks.

11. Common Gate Configuration

Sol!

$$I_Q = I_{DQ} = K_n (V_{GSQ} - V_{TN})^2$$

$$1 = 1 (V_{GSQ} - 1)^2$$

$$\boxed{V_{GSQ} = 2V}$$

→ (2m)

$$g_m = 2K_n (V_{GS} - V_{TN})$$

$$= 2(1)(2-1)$$

$$= 2 \text{ mA/V}$$

→ (2m)

from Ai, we can write

$$I_o = I_i \left(\frac{R_D}{R_D + R_L} \right) \left(\frac{g_m R_{si}}{1 + g_m R_{si}} \right)$$

$$V_o = I_o R_L$$

$$V_o = I_i \left(\frac{R_D}{R_D + R_L} \right) \left(\frac{g_m R_{si}}{1 + g_m R_{si}} \right) \times R_L$$

$$= \left[\frac{(10)(5)}{5+10} \right] \left[\frac{2(50)}{1+(2)(50)} \right] \times R_L$$

(0.1)
sin wt


$$\boxed{V_o = 0.2 \sin wt}$$

→ (6m)

2

12) N-channel CKT & derive the expression for i/p, o/p & voltage gain.

Common Drain Amplifier

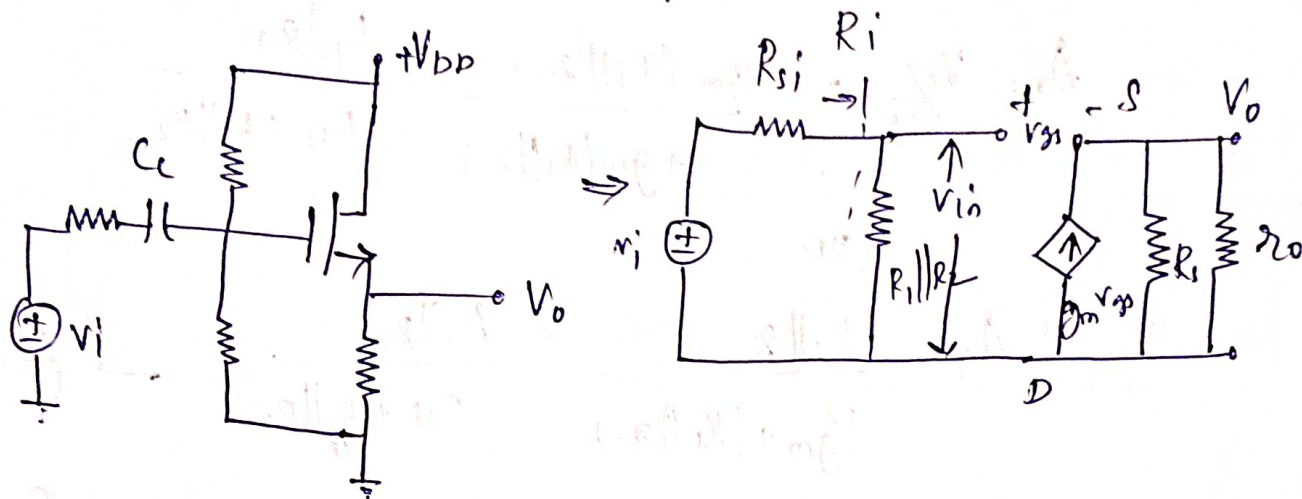

$$A_v = V_o / V_i$$

$$V_o = g_m V_{gs} (R_S \parallel r_{o0})$$

$$V_{in} = \frac{V_i \times R_{i1} \parallel R_2}{R_{Si} + R_{i1} \parallel R_2} \rightarrow \text{①}$$

$$\text{b.t. } V_{in} = V_{gs} + (g_m V_{gs}) (R_S \parallel r_{o0})$$

$$V_{in} = V_{gs} [1 + g_m (R_S \parallel r_{o0})]$$

$$V_{gs} = \frac{V_{in}}{1 + g_m (R_S \parallel r_{o0})}$$

Sub in V_o

$$V_o = \frac{g_m V_{in} (R_S \parallel r_{o0})}{1 + g_m (R_S \parallel r_{o0})} \rightarrow \text{②}$$

$\rightarrow \text{③m}$

Sub ① in ②

$$V_o = \frac{g_m V_i (R_1 \parallel R_2) (R_s \parallel g_o)}{(R_{si} + R_1 \parallel R_2) (1 + g_m (R_s \parallel g_o))}$$


$$A_v = \frac{V_o}{V_i} = \frac{g_m (R_s \parallel g_o)}{1 + g_m (R_s \parallel g_o)} \cdot \frac{R_1 \parallel R_2}{R_{si} + R_1 \parallel R_2}$$

(or)

$$A_v = \frac{R_s \parallel g_o}{1/g_m + (R_s \parallel g_o)} \cdot \frac{R_1 \parallel R_2}{R_{si} + R_1 \parallel R_2} \rightarrow \textcircled{2m}$$

$I_p \text{ imp: } R_i = R_1 \parallel R_2 \rightarrow \textcircled{1m}$

$O/p \text{ imp:}$

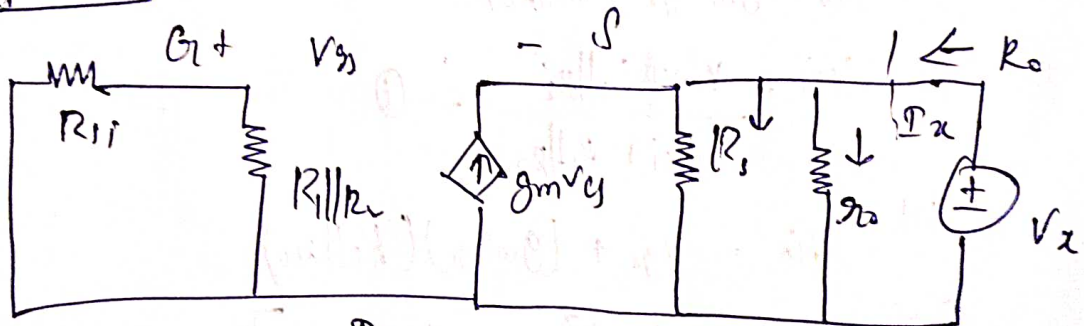

$$R_o = V_x / I_x$$

Apply KCL at the o/p terminal

$$I_x + g_m V_{gs} = \frac{V_x}{g_o} + \frac{V_x}{R_1}$$

Sub. $V_{gs} = -V_x$ in the above eq.

$$R_o = \frac{V_x}{I_x} = (g_o \parallel R_1 \parallel 1/g_m)$$

$\rightarrow \textcircled{4m}$

13) a) Bypass Capacitor is frequency response.

Explanation \rightarrow (2m)

Circuit & Equivalent circuit \rightarrow (2m)

Voltage gain $A_v = V_o/V_i$
 $= -g_m R_D \rightarrow$ (1m)

b) Small Signal Voltage gain of Common Source with Source Bypass Capacitor.

Sol !:

$$I_{DQ} = I_Q = K_n (V_{GSQ} - V_{TN})^2$$

$$0.5 = (1) (V_{GSQ} - 0.8)^2 = 1.51V$$

$$g_m = 2K_n (V_{GS} - V_{TN}) = 1.4$$

\rightarrow (3m)

$$A_v = V_o/V_i$$


$$= -g_m R_D = - (1.4) (7) = -9.8$$

\rightarrow (2m)

Section - B2:

14) Series Shunt feedback Topology.

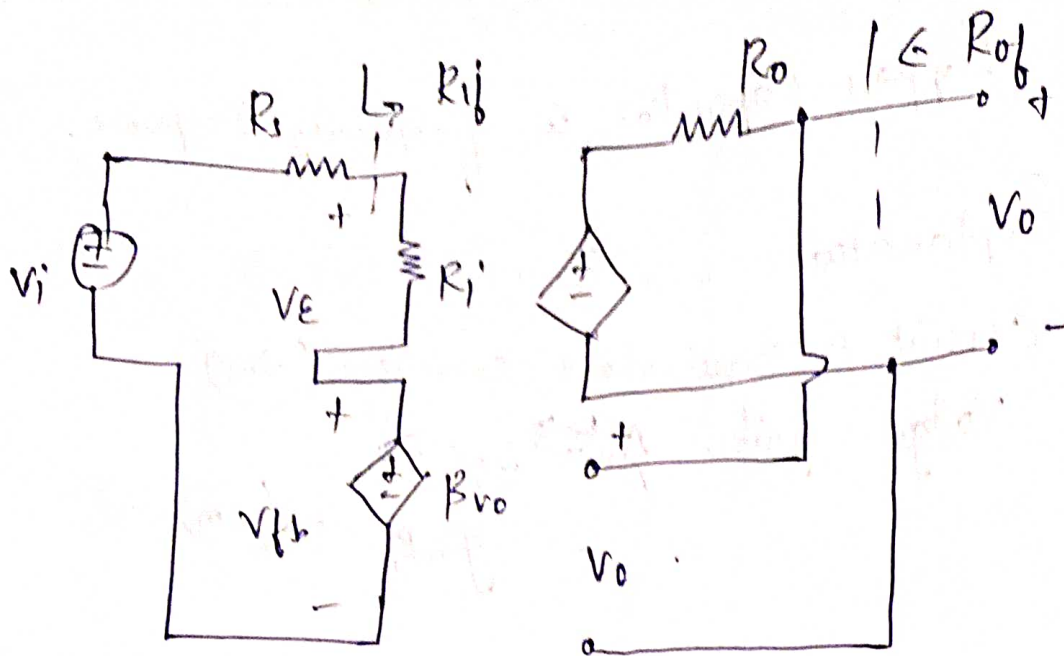a) $1/p$ res, $0/p$ res + gain with feedback.



→ (1m)

$\frac{I}{P} \rightarrow$ Series Connection

$\frac{O}{P} \Rightarrow$ Shunt Connection

$V_E \Rightarrow$ Error Voltage = difference between $\frac{1}{r}$ feedback.

$\frac{O}{P}$ of feedback n/w is open circuit

$$A_{vf} = \frac{V_o}{V_i}$$

$$V_o = A_v V_E \Rightarrow V_E = \frac{V_o}{A_v}$$

$$V_i = V_E + V_{fb} = V_E + \beta_v V_o$$

$$\therefore V_i = \frac{V_o}{A_v} + \beta_v V_o$$

→ (2m)

$$A_{vf} = \frac{V_o}{V_i} = \frac{A_v}{1 + \beta_v A_v}$$

(4)

 R_{if} :

$$R_{if} = \frac{V_i}{I_i}$$

$$V_i = V_E + V_{fb}$$

o/p side:

$$V_o = A_v V_E$$

$$V_{fb} = \beta_v V_o = \beta_v A_v V_E$$

Sub in V_i

$$V_i = V_E + \beta_v A_v V_E$$

$$V_i = V_E (1 + \beta_v A_v)$$

from i/p side



$$V_E = I_i R_i$$

Sub in the above eq

$$V_i = I_i R_i (1 + \beta_v A_v)$$

$$\boxed{V_i / I_i = R_{if} = R_i (1 + \beta_v A_v)}$$

→ (2m)

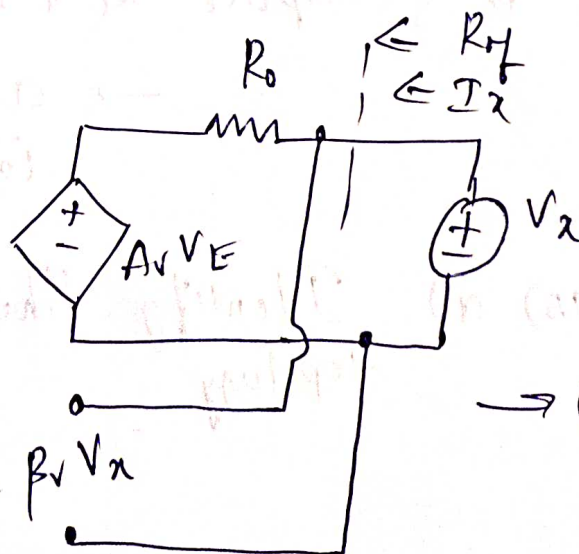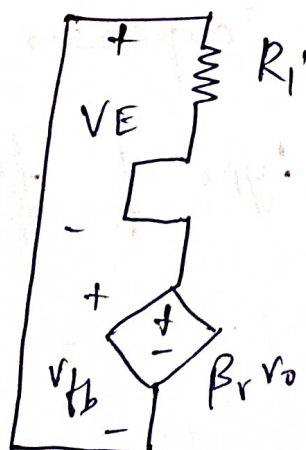o/p R_{out} , R_{of} :

→ (1m)

$$R_{of} = \frac{V_x}{I_x}$$

$$I_x = \frac{V_x - A_v V_E}{R_o}$$


from i/p Since $V_i = 0$
 $V_E + V_{fb} = 0 \Rightarrow V_E = -V_{fb} = -\beta_r V_o = -\beta_r V_x$

Sub in I_x

$$I_x = \frac{V_x + \beta_r V_x A_v}{R_o} = \frac{V_x (1 + \beta_r A_v)}{R_o}$$

$$R_{of} = \frac{V_x}{I_x} = \frac{R_o}{1 + \beta_r A_v}$$

Equivalent Circuit

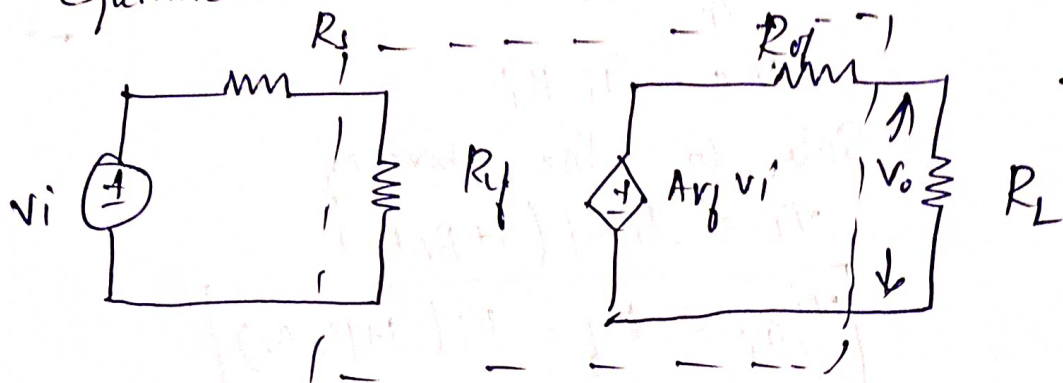

→ (2m)

14) b) Compare RC & LC Oscillator

→ any 2 points
 is Comparison

→ (2m)

15) a) Identify the type of feedback topology

Shunt Series Configuration

- $I_E = I_i - I_{fb}$
- Current amplifier
- i/p \rightarrow Shunt ; o/p \rightarrow Series

$$A_{ij} = I_o / I_i$$

$$I_i = I_E + I_{fb}$$

$$I_o = A_i I_E \Rightarrow I_E = \frac{I_o}{A_i}$$

Sub in I_i

$$I_i = \frac{I_o}{A_i} + I_{fb}$$

$$I_o / I_i = A_{ij} = \frac{A_i}{1 + A_i \beta_i}$$

\rightarrow (2m)

I/p Resistance with feedback A_{ij} :

$$R_{ij} = \frac{V_i}{I_i}$$

$$I_i = I_E + I_{fb}$$

$$I_{fb} = \beta_i I_o = \beta_i A_i I_E$$


$$I_i = I_E (1 + \beta_i A_i)$$

$$\therefore I_i = \frac{V_i}{R_i} (1 + \beta_i A_i)$$

\rightarrow (2m)

$$R_{ij} = V_i / I_i = \frac{R_i}{1 + \beta_i A_i}$$

o/p resistance R_{of} :

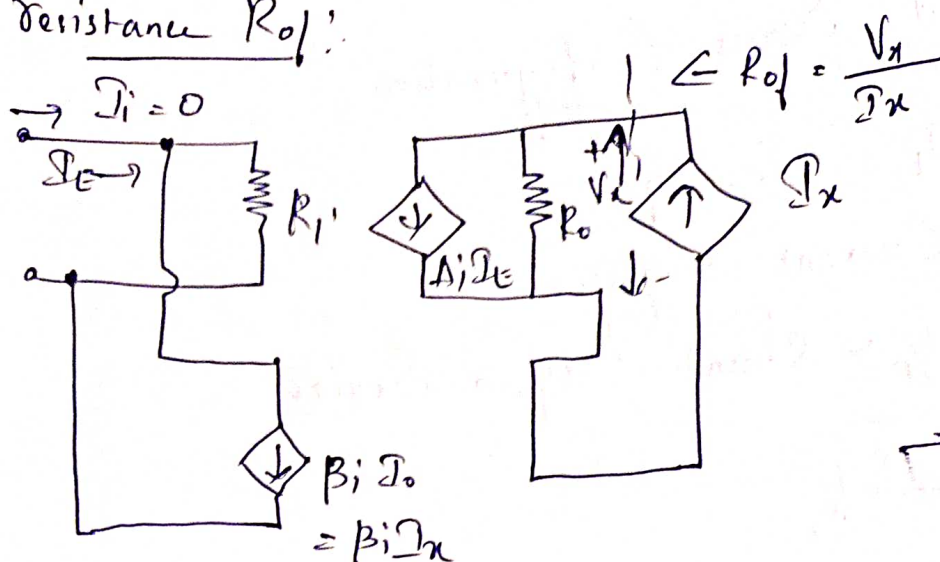

$$R_{of} = \frac{V_x}{I_x}; \quad I_x = \frac{V_x}{R_o} + A_i I_E$$

from i/p

$$I_E = -I_{fb} = -\beta_i I_x$$


Sub in I_x

$$I_x (1 + A_i \beta_i) = \frac{V_x}{R_o}$$

$\rightarrow (1m)$

$$R_{of} = \frac{V_x}{I_x} = R_o (1 + A_i \beta_i)$$

Eqn 1:

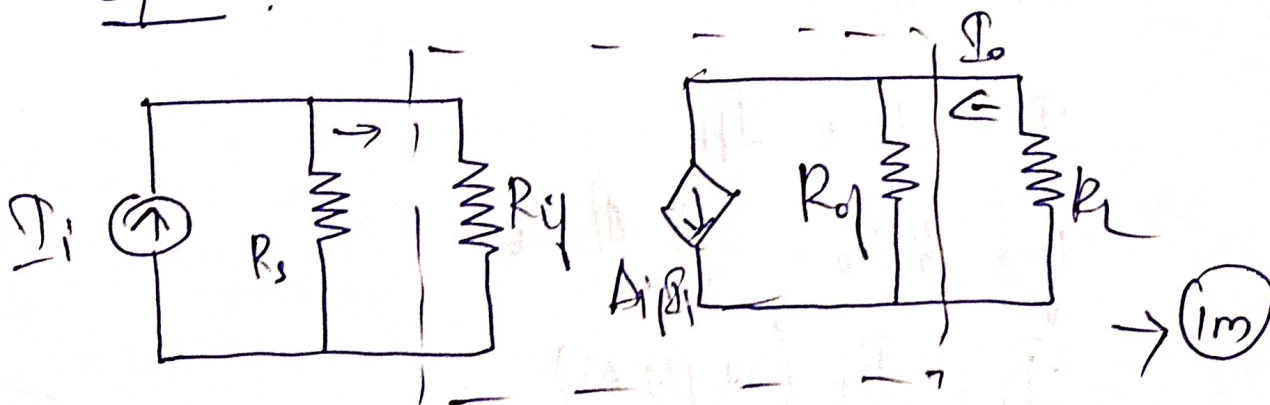

⑥

1c) b)


Clapp osc.

Diagram →

(2m)

Frequency expression →

(1m) →

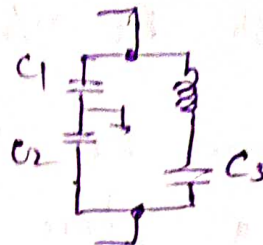

$$f = \frac{1}{2\pi \sqrt{LC_{eq}}}$$

1b) a)

$$L_1 = 1000 \mu H$$

$$L_2 = 500 \mu H$$

$$C = 50 pF$$

$$M = 20 \mu H$$

$$C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$$


Sol.

$$L_T = L_1 + L_2 + 2M = 1000 + 500 + 2(20) = 1540 \mu H$$

$$f = \frac{1}{2\pi \sqrt{L_T C}} = \frac{1}{2\pi \sqrt{1540 \times 50}} = 57.4 \text{ MHz}$$

(2m) ↙ ↘ (2m)

1b) b) R_c phase shift Osc

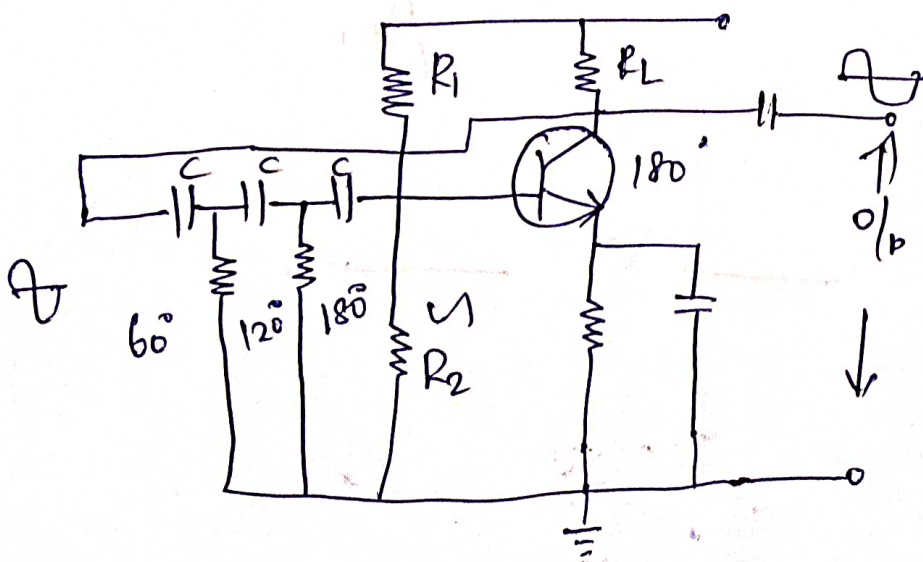

→ (2m)

- Each RC n/w provides a phase shift of 60° .
- Three RC stages are cascaded to provide a phase shift of 180° .
- Value of RC components determine the frequency of oscillation → (2m)

$$f_c = \frac{1}{2\pi RC \sqrt{2N}}$$

$N \rightarrow$ no. of stages

$$\therefore f = \frac{1}{2\pi RC \sqrt{6}}$$

The amplifier gain $A \geq 29$; $\beta = 1/29$.

Advantages: → Simple to design

→ produces sine wave → (2m)

Disadvantages → frequency + stability
Poor

— X —