

Voltage multiplier

- A *voltage multiplier* is a specialized **rectifier** circuit which can potentially produce an output voltage many times greater than of the applied input voltage
- Usually an integer times the AC peak input, for example, 2, 3, or 4 times the AC peak input.
- Thus, for a $100\text{ V}_{\text{peak}}$ AC source it is possible to get 200 V_{DC} from a using a **doubler**, 400 V_{DC} from a **quadrupler**.
- Voltage multipliers are AC-to-DC power conversion devices, comprised of **diodes and capacitors**, that produce a high potential DC voltage from a lower voltage AC source.
- Multipliers are made up of multiple stages. Each stage is comprised of one diode and one capacitor.

Types of voltage multiplier

- Depending on the output voltage, multipliers can be of different types
 - Voltage doublers
 - Voltage triplers
 - Voltage quadrupler

Voltage doublers


- A Voltage doubler produces a DC voltage almost twice the rms value of the input AC voltage.
- Voltage doubler can be of two types;
 - Half wave voltage doubler
 - Full wave voltage doubler

Half wave voltage doubler

The half-wave voltage doubler


(a) clamper at

(b) peak detector (half-wave rectifier)

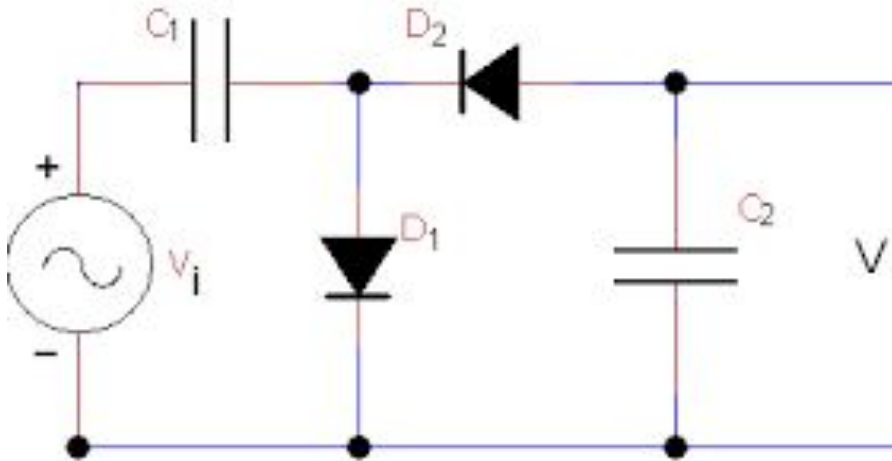


$$V_{\text{out}} = V_{C2} = 2V_m$$


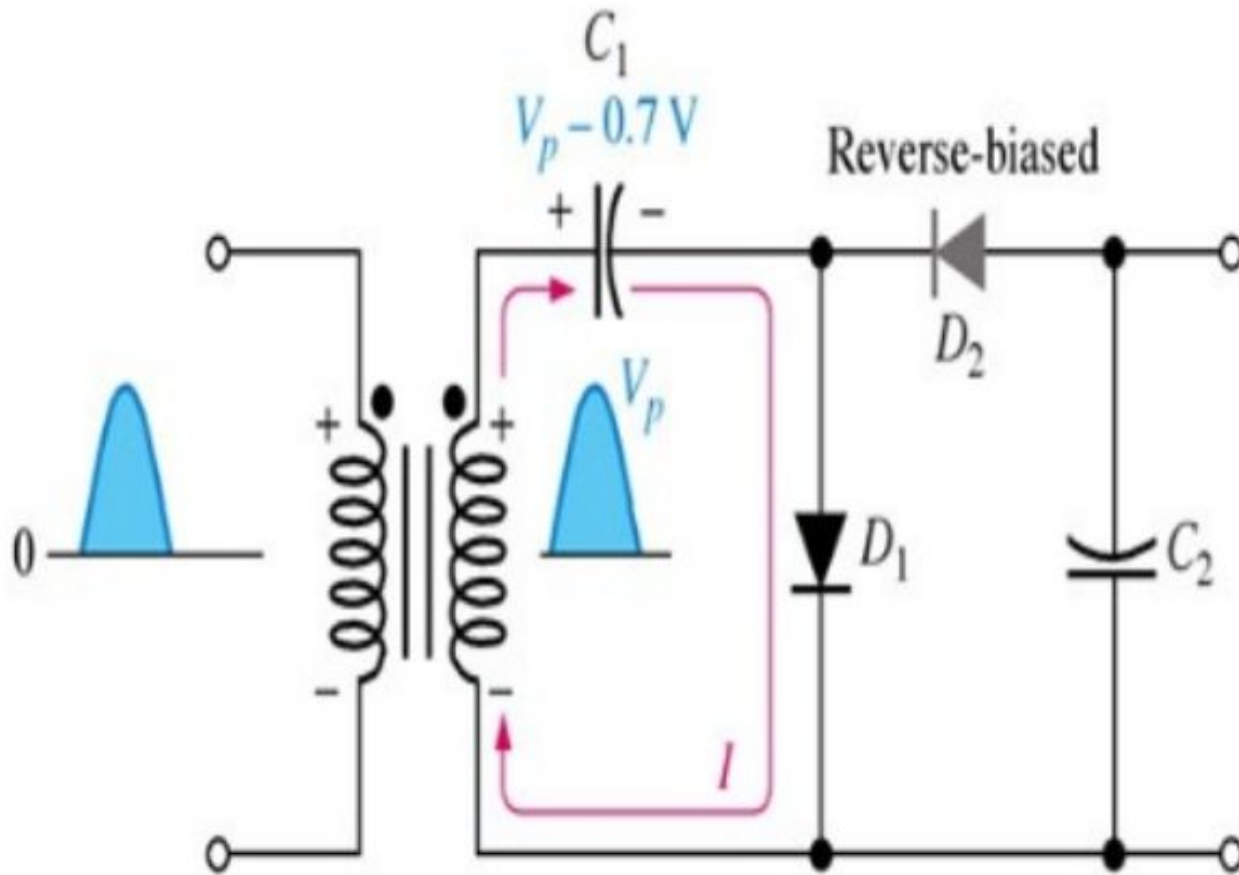
- During the positive half cycle of the secondary voltage diode D_1 conducts and D_2 is cut off.
- Now capacitor C_1 charges to the peak rectified voltage V_p



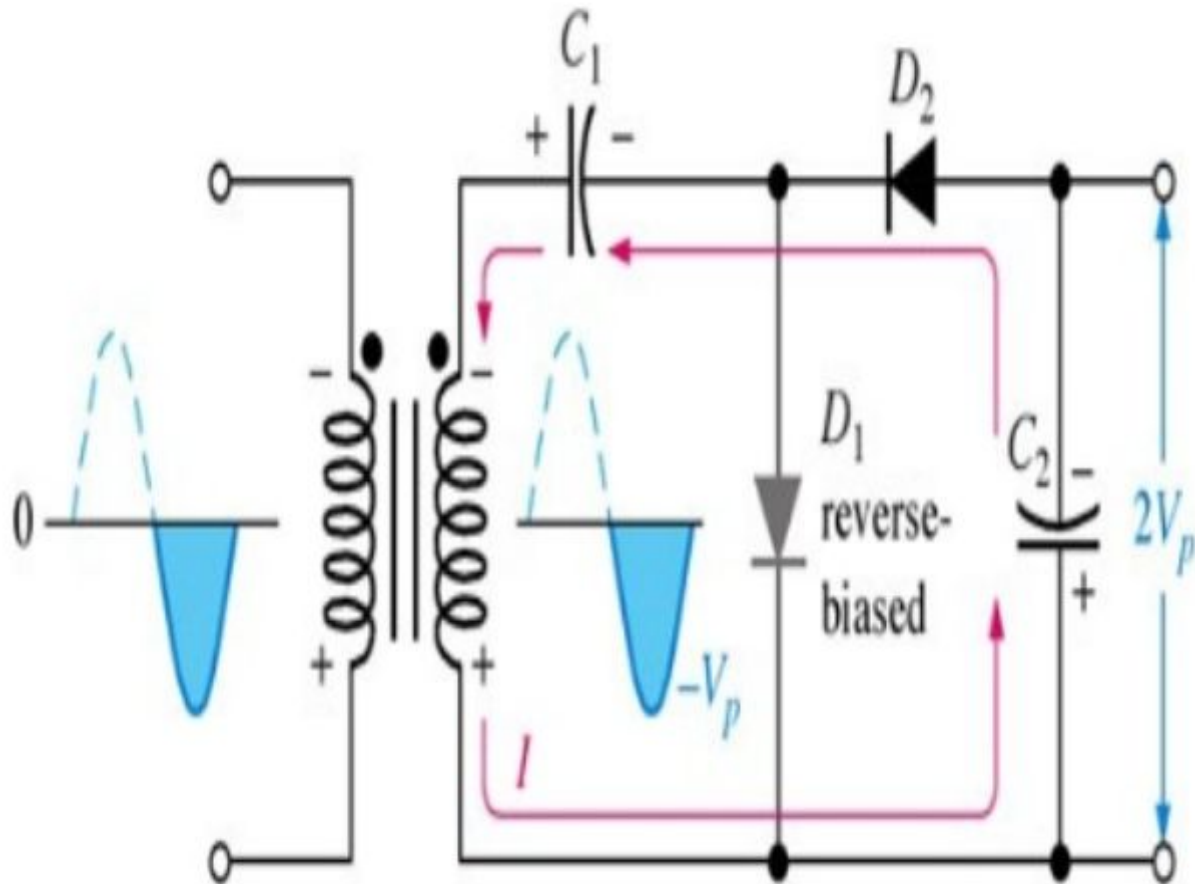- During the negative half cycle, the secondary voltage comes in series with voltage across the capacitor C_1 .
- Thus C_2 will try to charge towards $2V_p$ (V_p of the input and V_p of the capacitor C_1).




- After few cycles the voltage across the capacitor C_2 will be equal to $2V_m$
- Since diode D_2 acts as a short during the negative half-cycle (and diode D_1 is open), we can sum the voltages around the outside loop.
- In the circuit capacitor C_1 will discharge in the negative half cycle.
- Again in the positive half cycle, it starts charging.
- Thus the half wave voltage doubler supplies the voltage to the load in one half cycles.
- Therefore regulation of the half wave voltage doubler is poor.

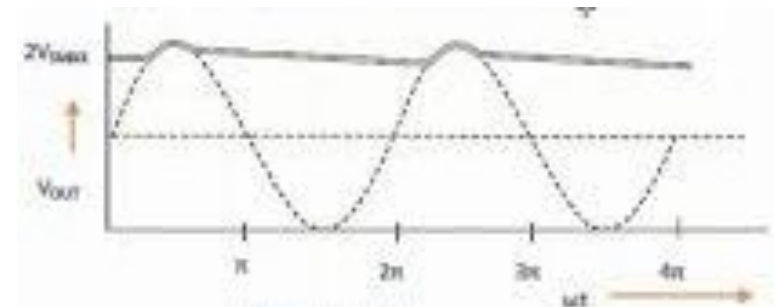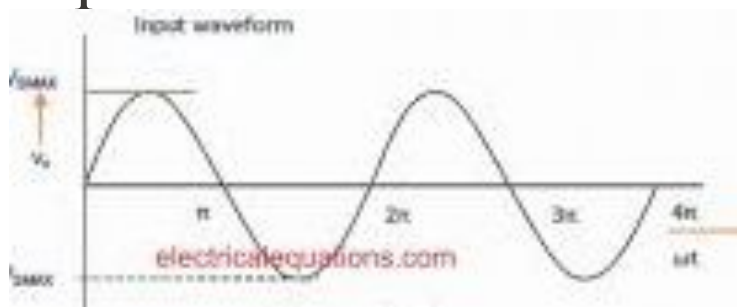

Full wave voltage doubler

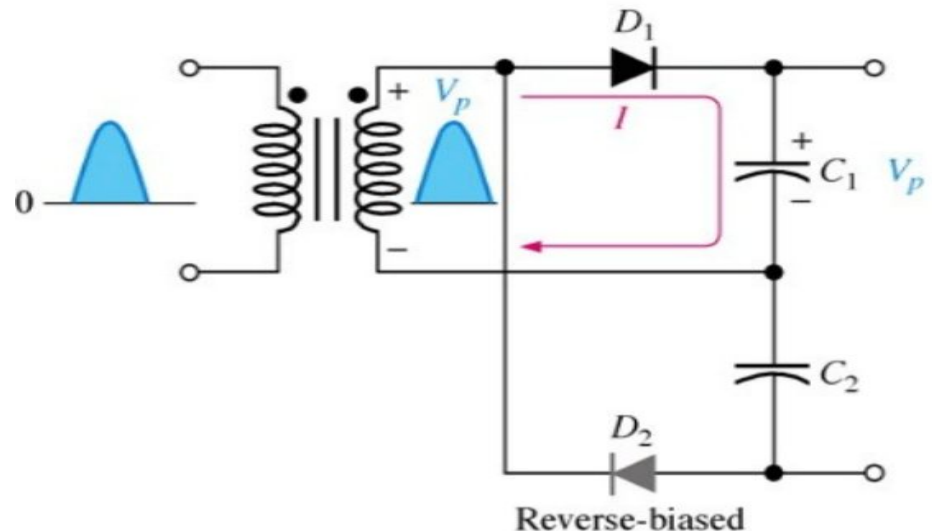- The full-wave voltage doubler is composed of a pair of series stacked half-wave rectifiers.
- Positive Half-Cycle
 - D_1 conducts
 - D_2 is switched off
 - Capacitor C_1 charges to V_m





- **Negative Half-Cycle**

- D_1 is switched off
- D_2 conducts
- Capacitor C_2 charges to V_p


Since both capacitors C_1 and C_2 are in series, the final output voltage is approximately $2V_p$

Full Wave Voltage Multiplier
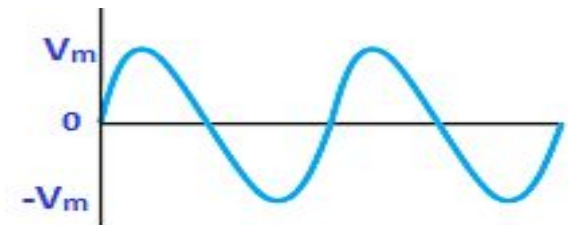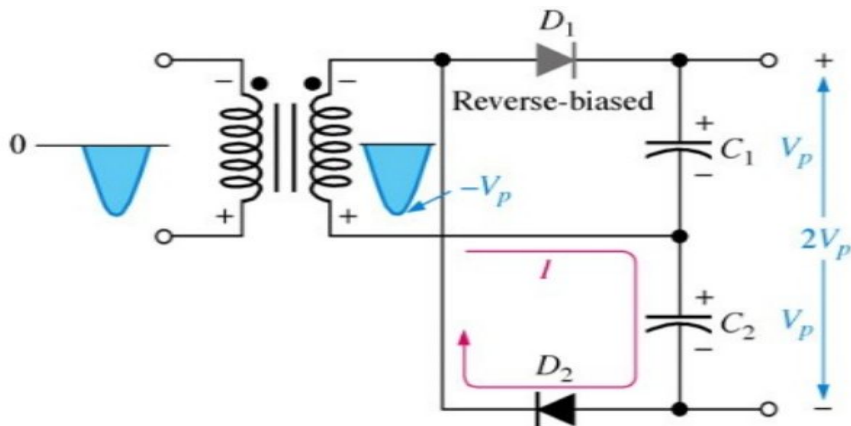
$$V_{\text{out}} = V_{C1} + V_{C2} = 2V_p$$




Input waveform

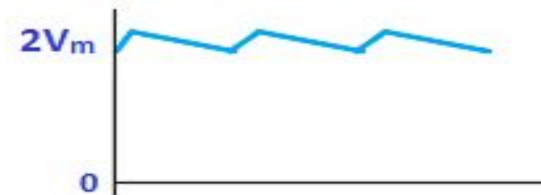



Output waveform

Voltage tripler and Quadrapler

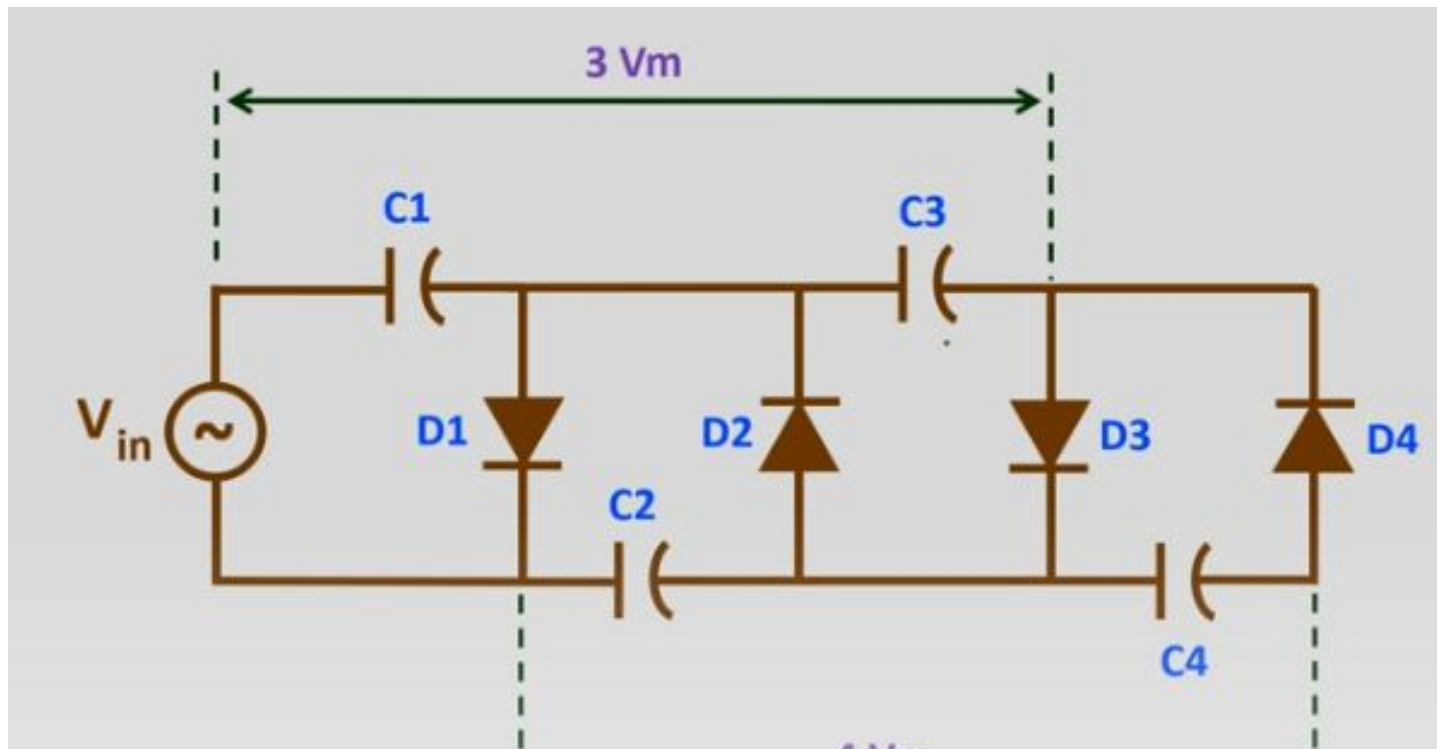- To build the voltage **Tripler** circuit, we just need to add 1 more Diode and capacitor to the above Half wave Voltage Doubler
- Again we just need to add one more diode and capacitor to Voltage Tripler circuit, to build the **Voltage Quadruple circuit** (4 times the input voltage).





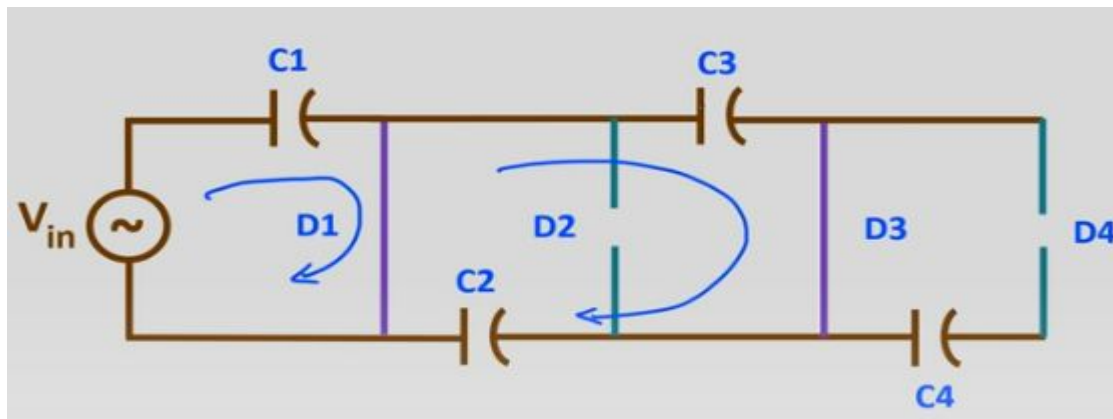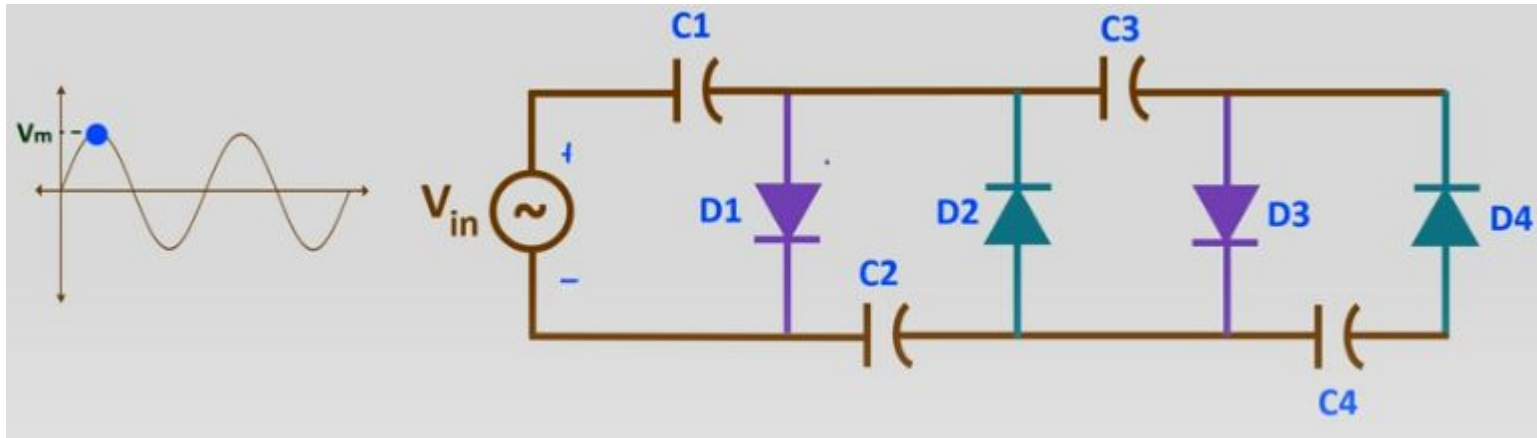- Positive half-cycle: D1 and D3 conducts



- C_1 charges to V_p through D_1


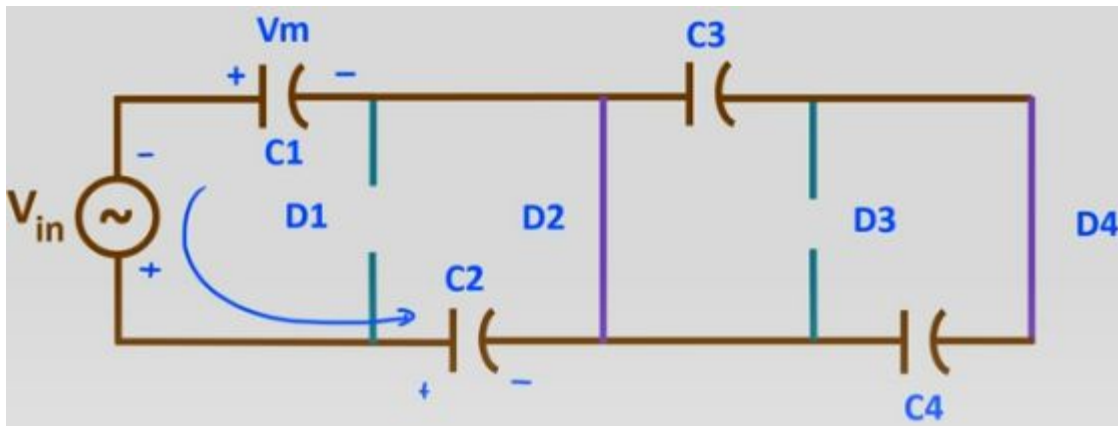
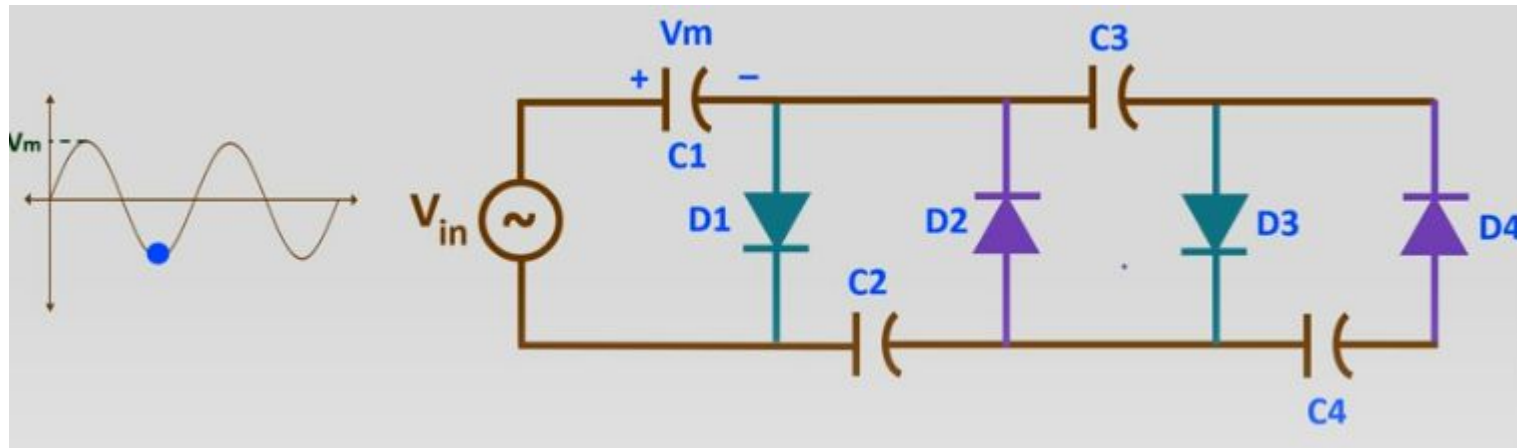
- Negative half-cycle: D2 and D4 conducts



$$V_{in} - V_{c2} - V_m = 0$$

$$V_{c2} = V_{in} + V_m$$

$$= 2 V_m$$

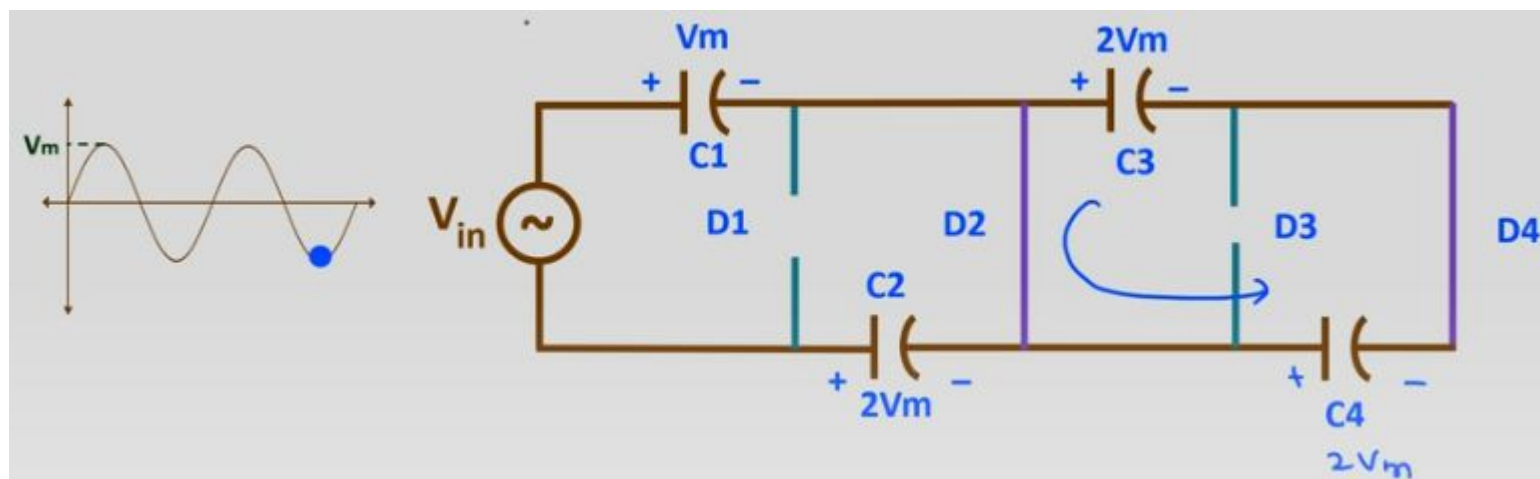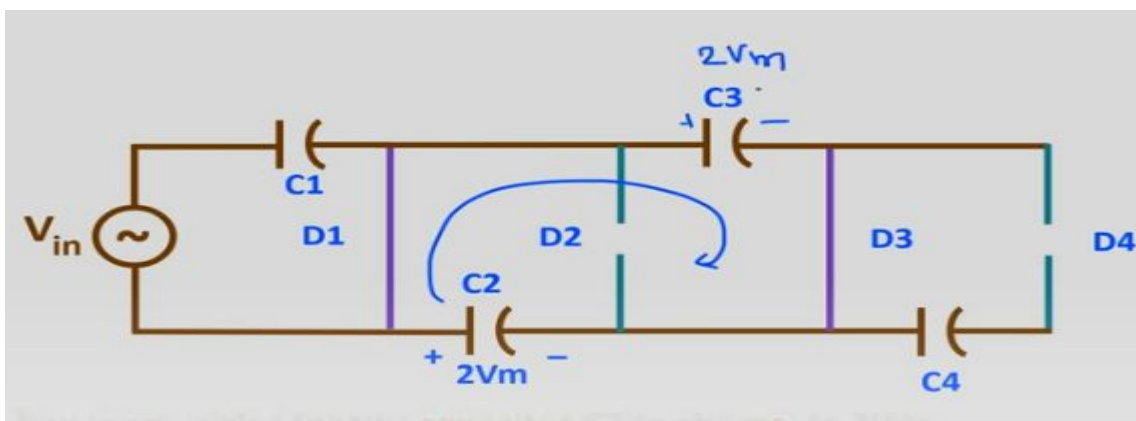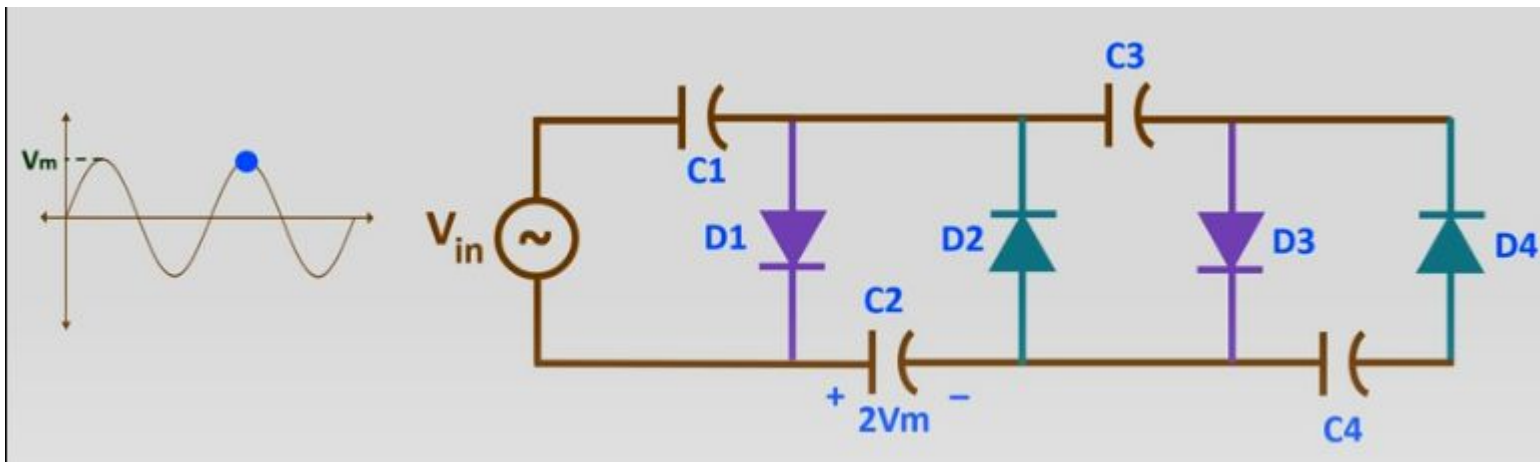

Voltage Quadruplers

- **+ half-cycle:**
- C_1 charges to V_p through D_1 ,
- **- half-cycle:** C_2 charges to $2V_p$ through C_2
- **Next + half-cycle:**
- C_3 charges to $2V_p$ through C_3 .
- **Next - half-cycle:** C_4 charges to $2V_p$ through C_4 • Quadruple Output is across C_2 & C_4 .

Multiplier Applications

- Originally used for television CRT's,
- voltage multipliers are now used for
 - lasers,
 - x-ray systems,
 - traveling wave tubes (TWT's),
 - photomultiplier tubes,

