

Reg. No.	R	A	2	0	1	1	0	0	4	0	1	0	2	2	6
----------	---	---	---	---	---	---	---	---	---	---	---	---	---	---	---

B.Tech. DEGREE EXAMINATION, JULY 2022
Fourth Semester

18ECC202J – LINEAR INTEGRATED CIRCUITS

(For the candidates admitted from the academic year 2020-2021 to 2021-2022)

Note:

- (i) **Part - A** should be answered in OMR sheet within first 40 minutes and OMR sheet should be handed over to hall invigilator at the end of 40th minute.
- (ii) **Part - B** should be answered in answer booklet.

Time: 2½ Hours

Max. Marks: 75

PART – A (25 × 1 = 25 Marks)

Answer ALL Questions

Marks BL CO PO

- | | | | | |
|--|---|---|---|---|
| 1. The operating temperature range of a military grade op-amp is | 1 | 1 | 1 | 2 |
| (A) -55°C to + 125°C | | | | |
| (B) -20°C to + 85°C | | | | |
| (C) -55°C to + 225°C | | | | |
| (D) 0°C to + 70°C | | | | |
| | | | | |
| 2. Output stage of an op-amp is designed to provide | 1 | 1 | 1 | 2 |
| (A) Low output impedance | | | | |
| (B) High output impedance | | | | |
| (C) Very high output impedance | | | | |
| (D) Low input impedance | | | | |
| | | | | |
| 3. An ideal op-amp has | 1 | 1 | 1 | 2 |
| (A) Infinite voltage gain | | | | |
| (B) Finite voltage gain | | | | |
| (C) Finite current gain | | | | |
| (D) Infinite current gain | | | | |
| | | | | |
| 4. If the gain-bandwidth product of an op-amp is 2MHz, what is its bandwidth when it is connected as a voltage follower? | 1 | 2 | 1 | 1 |
| (A) 1 MHz | | | | |
| (B) 2 MHz | | | | |
| (C) 3 MHz | | | | |
| (D) 4 MHz | | | | |
| | | | | |
| 5. In an operational amplifier, which of the following component is responsible for gain roll-off at higher frequencies | 1 | 1 | 1 | 1 |
| (A) Resistance | | | | |
| (B) Capacitance | | | | |
| (C) Inductance | | | | |
| (D) Diode | | | | |
| | | | | |
| 6. Input voltages 2V, 6V, 8V are applied to the inverting terminal of an averaging amplifier, find the output voltage? | 1 | 2 | 2 | 2 |
| (A) -5.33 V | | | | |
| (B) -8.34 V | | | | |
| (C) 6.8 V | | | | |
| (D) -6.6 V | | | | |
| | | | | |
| 7. Find the scaling factor of an inverting amplifier if $R_F = 3M\Omega$ and $R_i = 3k\Omega$. | 1 | 2 | 2 | 3 |
| (A) 1000 | | | | |
| (B) -1000 | | | | |
| (C) 10^{-3} | | | | |
| (D) -10^{-3} | | | | |
| | | | | |
| 8. If $V_o = V_i$ both in magnitude and phase, then the circuit is called | 1 | 1 | 2 | 2 |
| (A) Summer | | | | |
| (B) Differential amplifier | | | | |
| (C) Subtractor | | | | |
| (D) Voltage follower | | | | |

9. Which one of the following is not the features of instrumentation amplifier? 1 2 2 2
 (A) High gain (B) Low dc offset
 (C) Low output impedance (D) Low CMRR
10. The clamper is also known as 1 1 2 2
 (A) DC inserter (B) DC clipper
 (C) DC leveller (D) DC detector
11. The phase shift provided by the feedback network of a RC phase shift oscillator is 1 2 3 3
 (A) 60° (B) 120°
 (C) 180° (D) 360° or 0°
12. If a resistor of a monostable circuit is replaced by a constant source then circuit will act as a 1 2 3 2
 (A) Frequency divider (B) Pulse width modulator
 (C) Pulse position modulator (D) Linear Ramp generator
13. IC 555 Timer can drive a load up to 1 1 3 2
 (A) 100 mA (B) 150 mA
 (C) 200 mA (D) 300 mA
14. The frequency range that a Phase Locks Loop (PLL) maintains lock is called 1 1 3 2
 (A) Lock in range (B) Capture range
 (C) Pull in time (D) Pull out time
15. Which of the following is not correct? 1 1 3 2
 (A) The output frequency of the VCO can be changed by R_T
 (B) The output frequency of the VCO can be changed by C_T
 (C) The output frequency of the VCO can be changed by the voltage V_c , at the modulating input terminal.
 (D) The output frequency of the VCO can be changed by V_{CC} .
16. The filter that allows the range of frequency between f_h and f_l , and attenuates the signals outside the band is 1 1 4 3
 (A) Band pass filter (B) Band reject filter
 (C) Low pass filter (D) High pass filter
17. What is damping coefficient value for second order Bessel filter? 1 2 4 2
 (A) 1.414 (B) 0.765
 (C) 1.73 (D) 1.932
18. In a low pass n^{th} order filter, roll-off rate will be 1 2 4 2
 (A) $-n \times 20$ dB/decade (B) $n \times 20$ dB/decade
 (C) $-n \times 40$ dB/decade (D) $n \times 40$ dB/decade
19. What is the drop out voltage in a three terminal IC regulator? 1 2 4 2
 (A) $|V_{in}| \geq |V_0| + 2V$ (B) $|V_{in}| < |V_0| - 2V$
 (C) $|V_{in}| = |V_0|$ (D) $|V_{in}| \leq |V_0|$

- | | | | | |
|--|---|---|---|---|
| 20. Which among the following can act as a switch in switching regulator? | 1 | 1 | 4 | 2 |
| (A) Rectifiers | | | | |
| (B) Diode | | | | |
| (C) Transistors | | | | |
| (D) Relays | | | | |
| 21. The maximum deviation between actual and ideal converter output after gain and offset error have been removed is | 1 | 2 | 5 | 2 |
| (A) Absolute accuracy | | | | |
| (B) Relative accuracy | | | | |
| (C) Monotonicity | | | | |
| (D) Linearity | | | | |
| 22. A monotonic DAC is one whose analog output increases for | 1 | 1 | 5 | 2 |
| (A) decrease in digital input | | | | |
| (B) increase in analog input | | | | |
| (C) increase in digital input | | | | |
| (D) decrease in analog input | | | | |
| 23. Number of comparators that are required in flash type ADC | 1 | 2 | 5 | 3 |
| (A) Triples for each bit added | | | | |
| (B) Remains the same | | | | |
| (C) Doubles itself for each bit added | | | | |
| (D) Decreases twice for each bit added | | | | |
| 24. Which of the following ADC has fixed conversion time? | 1 | 1 | 5 | 2 |
| (A) Flash | | | | |
| (B) Successive approximation | | | | |
| (C) Dual slope | | | | |
| (D) Monolithic | | | | |
| 25. If successive approximation type ADC exhibits non monotonic characteristics it leads to | 1 | 1 | 5 | 2 |
| (A) Change in output code | | | | |
| (B) Change in input code | | | | |
| (C) Missing codes | | | | |
| (D) Inaccurate output | | | | |

PART - B (5 × 10 = 50 Marks)

Answer ALL Questions

Marks BL CO PO

- | | | | | |
|--|---|---|---|---|
| 26. a.i. List the DC characteristics of the op-amp. Explain any one. | 8 | 3 | 1 | 2 |
| ii. A non-inverting amplifier with a gain of 200 is nulled at 25°C. What will happen to the output voltage if the temperature rises to 60°C for an offset voltage drift of 0.15 mV/°C? | 2 | 4 | 1 | 3 |
| (OR) | | | | |
| b.i. List the types of frequency compensation techniques. Explain any one. | 8 | 3 | 1 | 2 |
| ii. A square wave of peak to peak amplitude of 500 mV has to be amplified to a peak-to-peak amplitude of 4 volts, with a rise time of 5 μsec. Can a 741 be used? Justify your answer. | 2 | 4 | 1 | 3 |
| 27. a.i. What are the limitations of an ordinary op-amp differentiator? Draw the circuit of a practical differentiator that will eliminate these limitations and explain. | 8 | 3 | 2 | 2 |
| ii. Design an op-amp differentiator that will differentiate an input signal with $f_{\max} = 100\text{Hz}$. Assume $C_1 = 0.1\mu F$. | 2 | 4 | 2 | 3 |

(OR)

b.j. Draw the circuit for log amplifier and explain.

8 2 2 2

ii. In an integrator, the voltage V_c across capacitor is zero at $t = 0$, input voltage $V_i = -1V$ is applied at $t=0$. Determine the time constant required to reach output voltage $+10V$ at $t=1$ msec. Assume $C = 0.01\mu F$. Find R .

2 4 2 3

28. a.i. With a neat diagram, explain the operation of triangular wave generator.

8 3 3 2

ii. Design a RC phase shift oscillator to oscillate at 200 Hz.

2 4 3 3

(OR)

b.i. Explain the operation of an Astable multivibrator using IC555 timer with neat diagram.

8 2 3 2

ii. In the monostable multivibrator $R = 50K\Omega$ and the time delay $T=50$ msec. Calculate the value of C .

2 3 3 3

29. a.i. Design a second order Butterworth low-pass filter having upper cut-off frequency of 2 kHz. Draw the diagram.

4 4 4 3


ii. With neat diagram explain All-pass filter.

6 2 4 2

(OR)

b.i. Specify suitable component values to get $V_0 = 7.5V$ in the give circuit 4 using a 7805 regulator $I_Q = 4.2mA$, $I_{R1} = 25mA$.

4 4 4 3

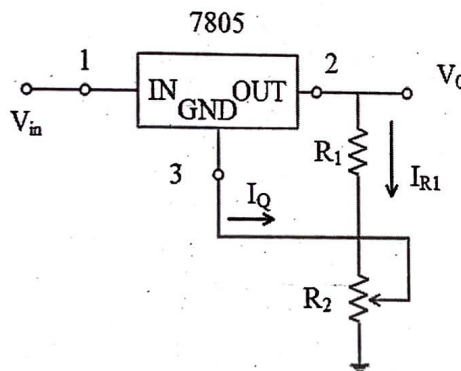

ii. Draw the functional diagram of 723 regulator and explain its operation.

6 3 4 2

30. a.i. The basic step of a 9-bit DAC is 10.3 mV. If 000000000 represents 0V, what output is produced if the input is 110010011?

2 4 5 3

ii. Why is an inverted R-2R ladder network DAC better than R-2R ladder DAC? Explain R-2R ladder DAC.

8 3 5 2

(OR)

b.i. Calculate the values of LSB and MSB for an 8-bit DAC of 0 to 20V range.

2 4 5 3

ii. Explain the operation of dual-slope ADC with a neat diagram.

8 2 5 2
