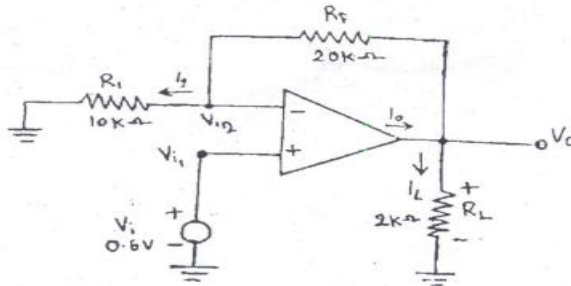


1.

The output voltage of a certain op-amp circuit changes by 20 V in 4 μ s. What is its slew rate?

2.

For the given non-inverting amplifier shown in figure below, determine (i) A_v ; (ii) V_o ; (iii) I_L and (iv) I_o .




3. An operational amplifier has a slew rate of 4V/ μ s. Determine the maximum frequency of operation to produce distortion less output swing of 12V

4. A differential amplifier has a differential voltage gain of 2000 and a common mode gain of 0.2. Determine the CMRR in dB

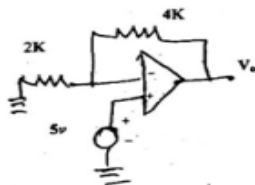5.

For the op-amp shown in figure determine the voltage gain



6. Calculate the time taken by the output to swing from +14V to -14V for a 741C op-amp having a slew rate of 0.5V/ μ s?

Slew rate = dv/dt

\Rightarrow Time taken = $14 - (-14) / 0.5V/\mu s = 28V / 0.5V/\mu s = 56\mu s$.

7. Consider a square wave having a peak to peak amplitude of 275mV and it is amplified to a peak to peak amplitude of 4V, with rise time of 5.2 μ s. Calculate the slew rate?

From the definition of rise time, the change in the output voltage is 5.2 μ s

$\Delta v = (90\% - 10\%) \times 4V = (0.9 - 0.1) \times 4V = 3.2V$.

Therefore, slew rate = $3.2V / 5.2\mu s = 0.615V/\mu s$.