

Chapter 5 – Minimization of Boolean Functions

We now continue our study of Boolean circuits to consider the possibility that there might be more than one implementation of a specific Boolean function. We are particularly focused on the idea of simplifying a Boolean function in the sense of reducing the number of basic logic gates (NOT, AND, and OR gates) required to implement the function.

There are a number of methods for simplifying Boolean expressions: algebraic, Karnaugh maps, and Quine-McCluskey being the more popular. We have already discussed algebraic simplification in an unstructured way. We now study Karnaugh maps (K-Maps). The tabular methods, known as Quine-McCluskey, are interesting but will not be covered in this course. Most students prefer K-Maps as a simplification method.

Logical Adjacency

Logical adjacency is the basis for all Boolean simplification methods. The facility of the K-Map approach is that it transforms logical adjacency into physical adjacency so that simplifications can be done by inspection.

To understand the idea of logical adjacency, we review two simplifications based on the fundamental properties of Boolean algebra. For any Boolean variables X and Y:

$$X \bullet Y + X \bullet Y' = X \bullet (Y + Y') = X \bullet 1 = X$$

$$\begin{aligned} (X + Y) \bullet (X + Y') &= X \bullet X + X \bullet Y' + Y \bullet X + Y \bullet Y' \\ &= X \bullet X + X \bullet Y' + X \bullet Y + 0 \\ &= X + X \bullet (Y' + Y) = X + X = X \end{aligned}$$

Two Boolean terms are said to be **logically adjacent** when they contain the same variables and differ in the form of exactly one variable; i.e., one variable will appear negated in one term and in true form in the other term and all other variables have the same appearance in both terms. Consider the following lists of terms, the first in 1 variable and the others in 2.

X	X'		
X • Y	X • Y'	X' • Y'	X' • Y
(X + Y)	(X + Y')	(X' + Y')	(X' + Y)

The terms in the first list are easily seen to be logically adjacent. The first term has a single variable in the true form and the next has the same variable in the negated form.

We now examine the second list, which is a list of product terms each with two variables. Note that each of the terms differs from the term following it in exactly one variable and thus is logically adjacent to it: X • Y is logically adjacent to X • Y', X • Y' is logically adjacent to X' • Y', X' • Y' is logically adjacent to X' • Y, and X' • Y is logically adjacent to X • Y. Note that logical adjacency is a commutative relation thus X • Y' is logically adjacent to both X • Y and X' • Y'. Using the SOP notation, we represent this list as 11, 10, 00, 01.

The third list also displays logical adjacencies in its sequence: $(X + Y)$ is logically adjacent to $(X + Y')$, which is logically adjacent to $(X' + Y')$, which is logically adjacent to $(X' + Y)$. Using POS notation, we represent this list as 00, 01, 11, 10.

Consider the list of product terms when written in the more usual sequence


$X' \bullet Y'$ $X' \bullet Y$ $X \bullet Y'$ $X \bullet Y$, or 00, 01, 10, 11 in the SOP notation.

In viewing this list, we see that the first term is logically adjacent to the second term, but that the second term is not logically adjacent to the third term: $X' \bullet Y$ and $X \bullet Y'$ differ in two variables. This is seen also in viewing the numeric list 00, 01, 10, and 11. Note that each of the digits in 01 and 10 is different, so that 01 and 10 can't represent logically adjacent terms.


Karnaugh Maps for 2, 3, and 4 variables

All books seem to define K-Maps for 2, 3, 4, 5, and 6 variables. It is this author's opinion that K-Maps for 5 and 6 variables are a waste of time, so he will not discuss them. The reason for this opinion is that K-Maps are designed to be a simple tool for simplifying Boolean expressions; K-Maps with 5 or more variables are hopelessly complex.

 This figure shows the basic K-Maps for 2, 3, and 4 variables. Note that there are two equivalent forms of the 3-variable K-Map; the student should pick one style and use it.



 We now examine three equivalent forms of the K-Map of an unspecified function. We show these K-Maps only to comment on the form of K-Maps and not to discuss simplification.



Each of these K-Maps represents the same function, shown at right in the truth-table form. One way to view a K-Map is as a truth-table with the main exception of the ordering 00, 01, 11, 10 seen on the top. For those interested, this ordering is called a **Gray code**.

The full K-Map is shown at left, with each square filled in either with a 0 or a 1. K-Maps are never written in this fashion – either one omits the 0's or one omits the 1's.

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

The form omitting the 0's is used when simplifying SOP expressions; to simplify POS one omits the 1's.

One final note – K-Maps are used to simplify Boolean expressions written in canonical form.

K-Maps for Sum of Products (SOP)

Consider the Canonical SOP expression $F(X,Y,Z) = X' \bullet Y \bullet Z + X \bullet Y' \bullet Z + X \bullet Y \bullet Z' + X \bullet Y \bullet Z$.

The first step in using K-Maps to simplify this expression is to use the SOP numbering to represent these as 0's and 1's. The negated variable is written as a 0, the plain as a 1. Thus, this function is represented as 011, 101, 110, and 111.

Z \ XY	00	01	11	10
0			1	
1		1	1	1

Place a 1 in each of the squares with the “coordinates” given in the list above. In the K-Map at left, the entry in the top row corresponds to 110 and the entries in the bottom row correspond to 011, 111, and 101 respectively. Remember that we do not write the 0's when we are simplifying expressions in SOP form.

The next step is to notice the physical adjacencies. We group adjacent 1's into “rectangular” groupings of 2, 4, or 8 boxes. Here there are no groupings of 4 boxes in the form or a rectangle, so we group by two's. There are three such groupings, labeled A, B, and C.

Z \ XY	00	01	11	10
0			1	
1		1	1	1

A
B
C

The grouping labeled A represents the product term XY . The B group represents the product term YZ and the C group represents the product term XZ . Examine the B grouping: it has 011 and 111. In this we have Y and Z staying the same and X having both values; thus the product term YZ . This function is

$$X \bullet Y + X \bullet Z + Y \bullet Z.$$

The next example is to simplify $F(A, B, C) = \Pi(3, 5)$. We shall consider use of K-Maps to simplify POS expressions, but for now the solution is to convert the expression to the SOP form $F(A, B, C) = \Sigma(0, 1, 2, 4, 6, 7)$. We could write each of the six product terms, but the easiest solution is to write the numbers as binary: 000, 001, 010, 100, 110, and 111.

The top row of the K-Map corresponds to the entries 000, 010, 100, and 110, arranged in the order 000, 010, 110, and 100 to preserve logical adjacency. The bottom row corresponds to the entries 001 and 111. The top row simplifies to C' . The first column

AB		00	01	11	10
C	0	1	1	1	1
	1	1		1	

simplifies to $A'B'$ and the third column to AB . Thus we have $F(A, B, C) = A' \cdot B' + A \cdot B + C'$.

We next consider a somewhat offbeat example not in a canonical form.

$$F(W, X, Y, Z) = W' \cdot X' \cdot Y' \cdot Z' + W' \cdot X' \cdot Y' \cdot Z + W \cdot X' \cdot Y'$$

The trouble with K-Maps is that the technique is designed to be used only with expressions in canonical form. In order to use the K-Map method we need to convert the term $W \cdot X' \cdot Y'$ to its equivalent $W \cdot X' \cdot Y' \cdot Z' + W \cdot X' \cdot Y' \cdot Z$, thus obtaining a four-term canonical SOP.

Before actually doing the K-Map, we first apply simple algebraic simplification to F .

$$\begin{aligned} F(W, X, Y, Z) &= W' \cdot X' \cdot Y' \cdot Z' + W' \cdot X' \cdot Y' \cdot Z + W \cdot X' \cdot Y' \\ &= W' \cdot X' \cdot Y' \cdot (Z' + Z) + W \cdot X' \cdot Y' \\ &= W' \cdot X' \cdot Y' + W \cdot X' \cdot Y' \\ &= (W' + W) \cdot X' \cdot Y' = X' \cdot Y' \end{aligned}$$

Now that we see where we need to go with the tool, we draw the four-variable K-Map.

$F(W, X, Y, Z) = W' \cdot X' \cdot Y' \cdot Z' + W' \cdot X' \cdot Y' \cdot Z + W \cdot X' \cdot Y' \cdot Z' + W \cdot X' \cdot Y' \cdot Z$. Using the SOP encoding method, these are terms 0000, 0001, 1000, and 1001. The K-Map is

WX		00	01	11	10
YZ	00	1			1
	01	1			1
	11				
	10				

The first row in the K-Map represents the entries 0000 and 1000. The second row in the K-Map represents the entries 0001 and 1001. The trick here is to see that the last column is adjacent to the first column. The four cells in the K-Map are thus adjacent and can be grouped into a square. We simplify by noting the values that are constant in the square: $X = 0$ and $Y = 0$. Thus, the expression simplifies to $X' \cdot Y'$, as required.

We close the discussion of SOP K-Maps with the example at right, which shows that the four corners of the square are adjacent and can be grouped into a 2 by 2 square. This K-Map represents the terms 0000, 0010, 1000, 1010 or $W' \cdot X' \cdot Y' \cdot Z' + W' \cdot X' \cdot Y \cdot Z' + W \cdot X' \cdot Y' \cdot Z' + W \cdot X' \cdot Y \cdot Z'$. The values in the square that are constant are $X = 0$ and $Z = 0$, thus the expression simplifies to $X' \cdot Z'$.

WX YZ	00	01	11	10
00	1			1
01				
11				
10	1			1

K-Maps for POS

K-Maps for Product of Sums simplification are constructed similarly to those for Sum of Products simplification, except that the POS copy rule must be enforced: 1 for a negated variable and 0 for a non-negated (plain) variable.

As our first example we consider $F(A, B, C) = \prod(3, 5) = (A + B' + C') \cdot (A' + B + C')$. Recall that the term $(A + B' + C')$ corresponds to 011 and that $(A' + B + C')$ to 101.

AB C	00	01	11	10
0				
1		0		0

This is really somewhat of a trick question used only to illustrate placing of the terms for POS. Place a 0 at each location, rather than the 1 placed for SOP. Note that the two 0's placed are not adjacent, so we cannot simplify the expression.

For the next example consider $F2 = (A + B + C) \cdot (A + B + C') \cdot (A + B' + C) \cdot (A' + B + C)$. Using the POS copy rule, we translate this to 000, 001, 010, and 100.

Before we attempt to simplify $F2$, we note that it is a very good candidate for simplification. Compare the first term 000 to each of the following three terms. The term 000 differs from the term 001 in exactly one position. The same applies for comparison to the other two terms. Any two terms that differ in exactly one position can be combined in a simplification.

We begin the K-Map for POS simplification by placing a 0 in each of the four positions 000, 001, 010, 100. Noting that 000 is adjacent to 001, just below it, we combine to get 00– or

$(A + B)$. The term 000 is adjacent to 010 to its right to get 0–0 or $(A + C)$. The term 000 is adjacent to 100 to its “left” to get –00 or $(B + C)$. As a result, we get the simplified form. $F2 = (A + B) \cdot (A + C) \cdot (B + C)$

Just for fun, we simplify this expression algebraically, using the derived Boolean identity $X \bullet X \bullet X = X$ for any Boolean expression X .

$$\begin{aligned} F2 &= (A + B + C) \bullet (A + B + C') \bullet (A + B' + C) \bullet (A' + B + C) \\ &= (A + B + C) \bullet (A + B + C') \bullet (A + B' + C) \bullet (A + B + C) \bullet (A' + B + C) \\ &= (A + B) \bullet (A + C) \bullet (B + C) \end{aligned}$$

		AB			
		00	01	11	10
C	0	0	0		0
	1	0			

It is encouraging that we get the same answer.

We now consider simplification of a POS function specified by a truth table.

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

		AB			
		00	01	11	10
C	0		0	0	
	1				

We plot two 0's for the POS representation of the function – one at 010 and one at 110. The two are combined to get $\neg 10$, which translates to $(B' + C)$.

More Examples of K-Maps

		Y ₁ Y ₀			
		00	01	11	10
X	0	1	1	1	1
	1	1	1	1	1

The sample at left, based on an earlier design shows a particularly simple problem. We find that all the entries in the K-Map are covered with a single grouping, thus removing all three variables. Since the entire K-Map is covered, the simplification is $F = 1$.

The K-Map at right shows an example with overlap of two groupings of 1's. All 1's in the map must be covered and some should be covered twice. The top row corresponds to X' . We then form the 2-by-2 grouping at the right to obtain the term Y_1 . Thus $F = X' + Y_1$.

There is another simplification that

should be considered. This corresponds to two 2-by-2 groupings. The 2-by-2 grouping at the right still corresponds to Y_1 . The new 2-by-2 grouping in the

		$Y_1 Y_0$			
		00	01	11	10
X	0	1	1	1	1
	1			1	1

		$Y_1 Y_0$			
		00	01	11	10
X	0		1	1	1
	1		1	1	1

middle gives rise to Y_0 , so we get another simplification $F = Y_0 + Y_1$.

Just One More K-Map: Overlapping Circles

We close the discussion of K-Maps with a technique that applies to both SOP and POS simplifications. We shall apply it to SOP simplification.

Consider the following K-Map.

		WX			
		00	01	11	10
YZ	00				
	01	1	1	1	
	11	1	1	1	
	10				

The six ones can be grouped in a number of ways. Consider the following. This grouping of four and two covers the six one's in the K-Map.

The four ones in the square form the term $W' \bullet Z$. The two ones in the rectangle form the term $W \bullet X \bullet Z$.

The K-Map simplifies to $W' \bullet Z + W \bullet X \bullet Z$.

WX \ YZ	00	01	11	10
00				
01	1	1	1	
11	1	1	1	
10				

Another way to consider the simplification of the K-Map is to group the rectangle and the square as in the figure at right.

The rectangle corresponds to the term $W' \bullet X' \bullet Z$.

The square corresponds to the term $X \bullet Z$.

This simplification yields $W' \bullet X' \bullet Z + X \bullet Z$.

WX \ YZ	00	01	11	10
00				
01	1	1	1	
11	1	1	1	
10				

It is important to note that the groupings can overlap if this yields a simpler reduction.

Here we show two overlapping squares.

The square at left corresponds to the term $W' \bullet Z$.

The square at right corresponds to the term $X \bullet Z$.

This simplification yields $W' \bullet Z + X \bullet Z$, which is simpler than either of the other two forms validly produced by the K-Map method.

Try 1: $W' \bullet Z + W \bullet X \bullet Z$

Try 2: $W' \bullet X' \bullet Z + X \bullet Z$

YZ \ WX				
	00	01	11	10
00				
01	1	1	1	
11	1	1	1	
10				

Try 3: $W' \bullet Z + X \bullet Z$. This seems better.

Simplification with Don't-Care Conditions

We now consider the use of K-Maps to simplify expressions that include the “d” or Don't-Care condition often generated when considering digital designs using flip-flops. We give a number of examples related to our previous designs of sequential circuits.

	X = 0	X = 1
$Y_1 Y_0$	J_1	J_1
0 0	0	1
0 1	1	0
1 0	d	d
1 1	d	d

The general rule in considering a simplification with the Don't-Care conditions is to count the number of 0's and number of 1's in the table and to use SOP simplification when the number of 1's is greater and POS simplification when the number of 0's is greater. Again we admit that most students prefer the SOP simplification. With a two-two split, we try

SOP simplification.

First we should explain the above table in some detail. The first thing to say about it is that we shall see similar tables again when we study flip-flops. For the moment, we call it a “folded over” truth table, equivalent to the full truth table at right. The function to be represented is J_1 . Lines 0, 1, 4, and 5 of the truth table seem to be standard, but what of the other rows in which J_1 has a value of “d”. This indicates that in these rows it is equally acceptable to have $J_1 = 0$ or $J_1 = 1$. We have four “Don't-Cares” or “d” in this table; each can be a 0 or 1 independently of the others – in other words we are not setting the value of d as a variable.

Y_1	Y_0	X	J_1
0	0	0	0
0	0	1	1
0	1	0	d
0	1	1	d
1	0	0	1
1	0	1	0
1	1	0	d
1	1	1	d

Design with flip-flops is the subject of another course.

When attempting a K-Map for SOP simplification, we drop the 0's and plot the 1's and d's. We then attempt to group the 1's into 2-by-1, 2-by-2 groupings, etc. We use the d's as

are convenient and have no requirement to cover any or all of them. Note that 3-by-1 groupings are not valid and that the 2-by-2 grouping of d's does not add anything to the simplification, but only adds an extra useless term.

		$Y_1 Y_0$			
		00	01	11	10
X	0		1	d	d
	1	1		d	d

The terms in the top row, labeled 001 and 011 for $X'Y_1'Y_0$ and $X'Y_1Y_0$, simplify to $0-1$ for $X'Y_0$, and the terms in the bottom row, labeled 100 and 110 for $XY_1'Y_0'$ and XY_1Y_0' , simplify to $1-0$ for XY_0' , so the simplified expression is $X' \bullet Y_0 + X \bullet Y_0' = X \oplus Y_0$.

		$Y_1 Y_0$			
		00	01	11	10
X	0	1	d	d	1
	1	1	d	d	1

The sample at left, based on an earlier design shows a particularly simple problem. We find that using the d's to combine with the 1's to produce a 4-by-2 grouping of 1's. Since the entire K-Map is covered, the simplification is $F = 1$.

The K-Map at right corresponds to an input table with one 0 and three 1's. This immediately suggests a SOP approach to the K-Map; we plot the 1's and d's and drop the 0. The top row corresponds to X' . We then form the 2-by-2 grouping at the right to obtain the term Y_1 . Thus $F = X' + Y_1$.

		$Y_1 Y_0$			
		00	01	11	10
X	0	d	1	1	d
	1		d	d	1

		$Y_1 Y_0$			
		00	01	11	10
X	0	d	1	1	d
	1		d	d	1

There is another simplification that should be considered. This corresponds to two 2-by-2 groupings. The 2-by-2 grouping at the right still corresponds to Y_1 . The new 2-by-2 grouping in

the middle gives rise to Y_0 , so we get another simplification $F = Y_0 + Y_1$.

	X = 0	X = 1
$Y_1 Y_0$	K_0	K_0
0 0	d	d
0 1	d	d
1 0	0	0
1 1	1	1

As a final example, we consider the input table, which contains two 0's and two 1's. According to the theory, this could be simplified equally well either as a SOP or POS expression. To gain confidence, we do both simplifications, with the SOP first.

Considered as a SOP problem, we plot the 1's and d's, then form the largest possible group that covers all of the 1's. Note that 3-by-2 is not a valid grouping, so we go with the 2-by-2 grouping. The square corresponds to Y_0 . The top row simplifies to 0-1 and the bottom to 1-1, thus we have -- 1 or Y_0 .

$Y_1 Y_0$	00	01	11	10
X				
0	d	d	1	
1	d	d	1	

$Y_1 Y_0$	00	01	11	10
X				
0	d	d		0
1	d	d		0

The POS simplification is shown at left. The top row simplifies to 0-0 and the bottom row simplifies to 1-0 so the K-Map simplifies to -- 0. Using the POS copy rule, this translates to Y_0 , as before.

It's a good thing that the two methods agree.

A Diversion: Application of Simplification Techniques to Programming

This next section attempts to apply some of the Boolean simplification techniques to issues sometimes seen in software development, especially C++ programming.

Consider the Boolean expressions in C++ that relate to equality. For variable x , we can have expressions such as $(x == 0)$, $(x != 0)$, and $!(x == 0)$. The last two are logically identical, and all are distinct from the assignment statement $(x = 0)$, which evaluates to False.

In our diversion, we consider three variables: x , y , and z . The only assumption made here is that each of the three is of a type that can validly be compared to 0; assuming that all are integer variables is one valid way to read these examples. Each of the expressions $(x == 0)$, $(y == 0)$, and $(z == 0)$ evaluates to either T (True) or F (False).

Consider a function that is to be called conditionally based on the values of three variables: x , y , and z . We write the Boolean expression as follows

```
if ( ( (x != 0) && (y != 0) && (z != 0) )
```

```

|| ( (x != 0) && (y != 0) && (z == 0) )
|| ( (x != 0) && (y == 0) && (z == 0) )
|| ( (x == 0) && (y != 0) && (z != 0) )
|| ( (x == 0) && (y != 0) && (z == 0) )
|| ( (x == 0) && (y == 0) && (z == 0) ) ) y = fzero(
)

```

We can apply the truth-table approach to analysis of the conditions under which the function fzero is invoked. The following table illustrates when the function is to be called.

(x == 0)	(y == 0)	(z == 0)	Call fzero
F	F	F	Yes
F	F	T	Yes
F	T	F	No
F	T	T	Yes
T	F	F	Yes
T	F	T	Yes
T	T	F	No
T	T	T	Yes

If this looks a bit like a truth table, it is because it is equivalent to a truth table and can be converted to one. Consider the following definitions of Boolean variables A, B, and C.

$$A = (x == 0)$$

$$B = (y == 0)$$

$$C = (z == 0)$$

Consider the expression $A = (x == 0)$ in the C++ programming language. It may seem a bit strange, but is perfectly legitimate. The expression $(x == 0)$ is a Boolean expression – it evaluates to True or False. The variable A is a Boolean variable, it also takes on one of the Boolean values. In order to translate the table above into a truth table that we recognize, we replace the expressions $(x == 0)$, $(y == 0)$, and $(z == 0)$ by their equivalents – the Boolean variables A, B, and C. We are beginning to construct a Truth Table.

In order to apply the truth table approach to this problem, we must define a Boolean function. For our purpose, we define $F(A, B, C)$ as follows

$$\begin{aligned}
 F(A, B, C) &= 1 && \text{if fzero is called} \\
 &= 0 && \text{if fzero is not called}
 \end{aligned}$$

Returning to our convention of 0 for False and 1 for True, we have the truth table.

This is a truth table that we have considered and simplified in an earlier section of the work. Using terminology we have already discussed, we see that this function $F(A, B, C)$ can be expressed as either a SOP with six product terms or a POS with two sum terms. Reading this as a POS, we get

A	B	C	F(A, B, C)
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0

$$F(A, B, C) = (A + \bar{B} + C) \cdot (\bar{A} + \bar{B} + C),$$

1	1	1	1
---	---	---	---

which simplifies to $F(A, B, C) = (\bar{B} + C)$.

We now convert back to the original notation. Recalling that $B = (y == 0)$ and $C = (z == 0)$, we note that $B' = (y != 0)$ and the condition for calling the function `fzero` becomes $((y != 0) || (z == 0))$. So the equivalent (and much simpler) expression is

```
if ( (y != 0) || (z == 0) ) y = fzero( )
```

Consider now the Boolean expression $((x == 0) || ((x != 0) \&\& (y == 0)))$. In an attempt to simplify this expression we define two Boolean variables

$A = (x == 0)$

$B = (y == 0)$

Recall that $(x != 0) = !(x == 0) = \bar{A}$. In our terminology, the expression is

$$F(A, B) = A + (\bar{A} \cdot B)$$

There are a number of ways to simplify this expression. The first, and least obvious, is to invoke the theorem of absorption, which states that the formula equals $A + B$.

To illustrate other options, we expand the above to canonical SOP and then examine it by means of both a truth table and a K-map. To expand the expression into canonical SOP, we need to have the first term contain a literal for the variable B .

$$A + \bar{A} \cdot B = A \cdot (\bar{B} + B) + \bar{A} \cdot B = \bar{A} \cdot B + A \cdot \bar{B} + A \cdot B$$

The truth table for this expression is

A	B	F(A, B)
0	0	0
0	1	1
1	1	1
1	0	1

Representing this as a POS formula, we immediately get $F(A, B) = (A + B)$, which translates to the C++ expression $((x == 0) || (y == 0))$.

As a final example, consider the following Boolean expression in C++

```
((x == 0) || (y == 0) || (z == 0)) && ((x == 0) || (y == 0) || (z != 0)) &&
((x == 0) || (y != 0) || (z == 0)) && ((x != 0) || (y == 0) || (z == 0))
```

Define

$A = (x == 0)$
 $B = (y == 0)$
 $C = (z == 0)$

With these definitions our expression becomes

$$F(A, B, C) = (A + B + C) \cdot (A + B + \bar{C}) \cdot (A + \bar{B} + C) \cdot (\bar{A} + B + C)$$

This is known to simplify to

$$F(A, B, C) = (A + B) \cdot (A + C) \cdot (B + C)$$

So our Boolean expression in C++ simplifies to

$$((x == 0) \parallel (y == 0)) \&\& ((x == 0) \parallel (z == 0)) \&\& (y == 0) \parallel (z == 0))$$

Inspection of the above shows that we want at least two of $(x == 0)$, $(y == 0)$, and $(z == 0)$ to be true. Compare this with the original derivation of the function

$$F(A, B, C) = (A + B) \cdot (A + C) \cdot (B + C)$$

used for the carry-out of a Full-Adder, which is 1 if two or three of the inputs are 1.