

Analysis of Clocked Sequential Circuits

Sequential Circuit Analysis

- The behavior of a clocked sequential circuit is determined from
 - The inputs
 - The outputs
 - The state of its flip-flops
- The outputs and the next state are both a function of the inputs and the present state
- To analyze a sequential circuit, we can use
 - State equations
 - State table
 - State diagram
 - Flip-Flop input equations

State Equations

- Specify the next state as a function of the present state and inputs

- Also called transition equation

- Analyze the combinational part directly

- EX:

$$A(t+1) = A(t)x(t) + B(t)x(t)$$


$$\Rightarrow A(t+1) = Ax + Bx$$

$$B(t+1) = A'(t) x(t)$$

$$\Rightarrow B(t+1) = A'x$$

$$y(t) = [A(t) + B(t)] x(t)$$

$$\Rightarrow y = (A + B)x'$$

 

State Table

- Enumerate the time sequence of inputs, outputs, and flip-flop states
 - Also called transition table
 - Similar to list the truth table of state equations
- Consist of four sections
 - Present state, input, next state, and output
- A sequential circuit with m flip-flops and n inputs need 2^{m+n} rows in the state table

Present state		input	Next state		output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

Second Form of State Table

- The state table has only three section: present state, next state, and output
- The input conditions are enumerated under next state and output sections

Present State		Next State				Output	
		X=0		X=1		X=0	X=1
A	B	A	B	A	B	Y	Y
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

State Diagram

- Graphically represent the information in a state table
 - Circle: a state (with its state value inside)
 - Directed lines: state transitions (with inputs/outputs above)
- Ex: starting from state 00
 - If the input is 0, it stays at state 00 with output=0
 - If the input is 1, it goes to state 01 with output=0
- The state table is easier to derive from a given logic diagram and state equations
- The state diagram is suitable for human interpretation

 


Fig. 5-16 State Diagram of the Circuit of Fig. 5-15

Flip-Flop Input Equations

- To draw the logic diagram of a sequential circuit, we need
 - The type of flip-flops
 - A list of Boolean expressions of the combinational circuits
- The Boolean functions for the circuit that generates external outputs is called output equations
- The Boolean functions for the circuit that generates the inputs to flip-flops is flip-flop input equations
 - Sometimes called excitation equations
- The flip-flop input equations provide a convenient form for specifying the logic diagram of a sequential circuit

■ Ex: (Fig. 5-15)

Input:

Output:


$$D_A = Ax + Bx$$

$$y = (A + B)x'$$

$$D_B = A'x$$

Analysis with D Flip-Flop

 
- Input equation: $D_A = A \oplus x \oplus y$



(a) Circuit diagram

Present state	Inputs		Next state
A	x	y	A
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(b) State table

 

(c) State diagram

Fig. 5-17 Sequential Circuit with D Flip-Flop



Analysis with Other Flip-Flops

- The sequential circuit using other flip-flops such as JK or T type can be analyzed as follows
 - Determine the flip-flop input equations in terms of the present state and input variables
 - List the binary values of each input equation
 - Use the corresponding flip-flop characteristic table to determine the next state values in the state table

Analysis with JK Flip-Flops (1/2)

Step 1: input equations

$$J_A = B \quad K_A = Bx' \quad J_B = x' \quad K_B = A \oplus x'$$

Step 2: state equations

$$\begin{aligned} A(t+1) &= JA' + K'A \\ &= BA' + (Bx')'A \\ &= A'B + AB' + Ax \end{aligned}$$

$$\begin{aligned} B(t+1) &= JB' + K'B \\ &= x'B' + (A \oplus x)'B \\ &= B'x' + ABx + A'Bx' \end{aligned}$$

 


Fig. 5-18 Sequential Circuit with JK Flip-Flop

Analysis with JK Flip-Flops (2/2)

Step 3: state table

Present state		Input	Next state		Flip-Flop Inputs			
A	B	X	A	B	J_A	K_A	J_B	K_B
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

Step 4: state diagram


 


Fig. 5-19 State Diagram of the Circuit of Fig. 5-18

Analysis with T Flip-Flops (1/2)

 

(a) Circuit diagram

Step 1: input equations

$$T_A = Bx \quad T_B = x \quad y = AB$$

Step 2: state equations

$$\begin{aligned} A(t+1) &= T'A + TA' \\ &= (Bx)'A + (Bx)A' \\ &= AB' + Ax' + A'Bx \end{aligned}$$


$$\begin{aligned} B(t+1) &= T'B + TB' \\ &= x'B + xB' \\ &= x \oplus B \end{aligned}$$

Analysis with T Flip-Flops (2/2)

Step 3: state table

Present state		Input	Next state		Output
A	B	X	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	1

Step 4: state diagram

 


(b) State diagram

Mealy and Moore Model


- Mealy model :

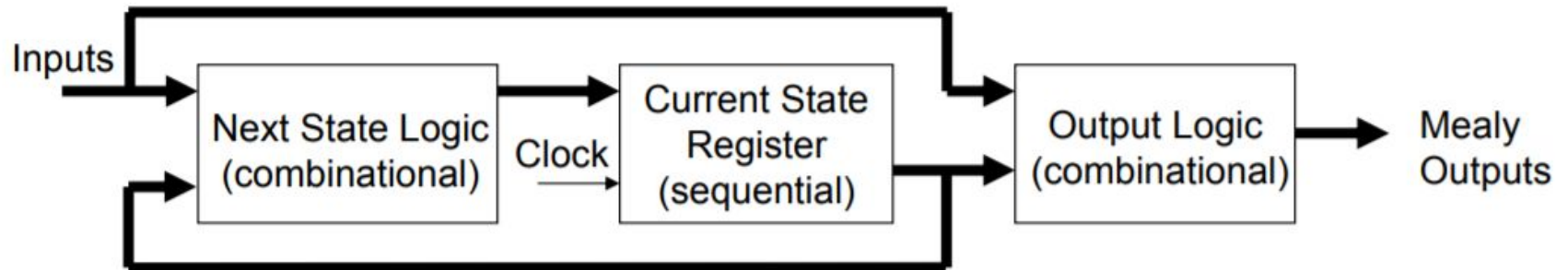- The output is a function of **both** the present state and input
- The output may change if the inputs change during a clock cycle



- Moore model :

 - The output is a function of the **present state only**
- The output are **synchronized** with the clock



State Reduction

State Reduction

- Reducing the number of states in a state table, while keeping the external input-output requirements unchanged
- Example:
 - Total 7 states
 - A sequence as follows

state	a	a	b	c	d	e	f	f	g	f	g	a
input	0	1	0	1	0	1	1	0	1	0	0	
output	0	0	0	0	0	1	1	0	1	0	0	

 


Fig. 5-22 State Diagram

State Reduction Rules

- Two states are said to be equivalent if, for every possible inputs, they give exactly the same output and have equivalent next state

Present State	Next State		Output	
	X=0	X=1	X=0	X=1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	g	f	0	1
g	a	f	0	1

Present State	Next State		Output	
	X=0	X=1	X=0	X=1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	e	f	0	1

delete state g and
replaced with state e

Further State Reduction

- After the first reduction, we can see that state d and state f will have the same output and next state for both $x=0$ and $x=1$
 - Further reduce one state

Present State	Next State		Output	
	X=0	X=1	X=0	X=1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	e	f	0	1

Present State	Next State		Output	
	X=0	X=1	X=0	X=1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	d	0	1
e	a	d	0	1

delete state f and
replaced with state d

Reduced State Diagram

- After reduction, the circuit has only 5 states with same input/output requirements
- Original output sequence:

state	a	a	b	c	d	e	f	f	g	f	g	a
input	0	1	0	1	0	1	1	0	1	0	0	
output	0	0	0	0	0	1	1	0	1	0	0	

- Reduced output sequence:

state	a	a	b	c	d	e	d	d	e	d	e	a
input	0	1	0	1	0	1	1	0	1	0	0	
output	0	0	0	0	0	1	1	0	1	0	0	

 


Fig. 5-23 Reduced State Diagram