

Unit -V : Digital Electronics Principles

Design of Counters

Dr B Srinath
Assistant Professor
Dept. of Electronics and Communication Engineering
SRM Institute of Science and Technology
Kattankulathur Campus


Table of contents

1. Counters
2. Types of counter designs
 - Difference: Asynchronous and Synchronous designs
3. Steps to design a Synchronous counter
4. Steps to design a Asynchronous counter


Introduction

- Counters are the basic elements of a digital circuit.
- For every clock pulse, it counts in two different ways, namely
 - *Up count:* 0, 1, 2, 3,14, 15.
 - *Down count:* 15, 14, 13, 12, 11, 10,2,1,0.
- Designing a counter requires flip flops as it need to record every bit in each clock pulse.
- Two types of counter designs:
 - Asynchronous
 - Synchronous

Types of counter designs

 

(a) Synchronous design

 

(b) Asynchronous design

Difference: Asynchronous and Synchronous designs

Asynchronous:

- In this type of design, flip-flops are connected in such a way that output of first flip-flop drives the clock for the next flip-flop.
- All the flip-flops are not clocked simultaneously.
- Logic circuit is very simple even for more number of states.
- *Low speed:* The clock is propagated through number of flip-flops before it reaches last flip-flop.

Synchronous:

- In this type of design, no connection between the output of first flip-flops and the clock input of next flip-flop.
- All the flip-flops are clocked simultaneously.
- Design involves complex logic circuit as the number of states increases.
- *High speed:* The clock is propagated uniformly to all the flip-flops.

Waveform

 


Figure 2: Asynchronous waveform

 


Figure 3: Synchronous waveform

Up/Down Counter

 


Figure 4: Logic Diagram

Up/Down Counter


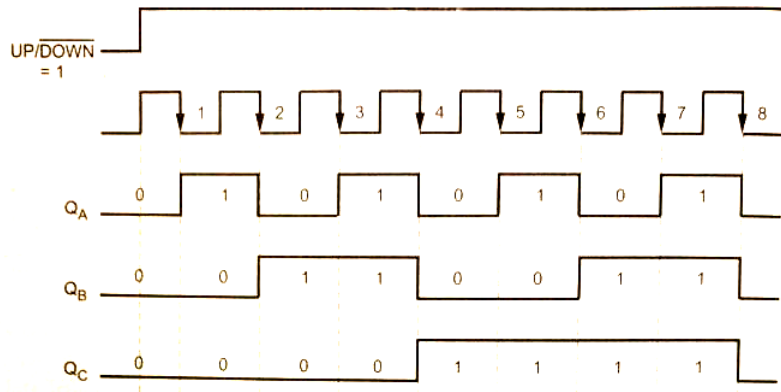


Figure 5: Up-count waveform

Up/Down Counter

 

Steps to design a Synchronous counter

- It is necessary to first obtain the stable table from the given circuit information.
- Assign binary values to each state in the state table.
- Determine the number of flip flops needed and assign a letter symbol to each state.
- Choose the type of flip flop to be used.
- From the state table , derive the circuit excitation and output tables.
- Using K-map or any other simplification method, derive the circuit output functions and the flip-flop input functions.
- Draw the logic diagram.

Synchronous: Sequence counter

- Design a Synchronous counter using JK flip flop to count the sequence $4 \rightarrow 6 \rightarrow 7 \rightarrow 3 \rightarrow 1 \rightarrow 4...$
- According to $2^n \geq N$. Here, $N=7$ therefor $n=3$ flip-flops.

Present state			Next state			Flip flop inputs					
A	B	C	A_{+1}	B_{+1}	C_{+1}	J_A	K_A	J_B	K_B	J_C	K_C
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	1	0	0	1	X	0	X	X	1
0	1	0	0	1	1	0	X	X	0	1	X
0	1	1	0	0	1	0	X	X	1	X	0
1	0	0	1	1	0	X	0	1	X	0	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	1	1	1	X	0	X	0	1	X
1	1	1	0	1	1	X	1	X	0	X	0

K-map

	$\overline{B} \overline{C}$	$\overline{B} C$	$B C$	$B \overline{C}$
\overline{A}	0	1	0	0
A	X	X	X	X

Table 1: $J_A = \overline{B}C$

	$\overline{B} \overline{C}$	$\overline{B} C$	$B C$	$B \overline{C}$
\overline{A}	X	X	X	X
A	0	0	1	0

Table 2: $K_A = BC$

	$\overline{B} \overline{C}$	$\overline{B} C$	$B C$	$B \overline{C}$
\overline{A}	0	0	X	X
A	1	1	X	X

Table 3: $J_A = A$

	$\overline{B} \overline{C}$	$\overline{B} C$	$B C$	$B \overline{C}$
\overline{A}	X	X	1	0
A	X	X	0	0


Table 4: $K_B = \overline{A}C$

contin..

	$\overline{B} \overline{C}$	$\overline{B} C$	$B C$	$B \overline{C}$
\overline{A}	1	X	X	1
A	0	X	X	1

Table 5: $J_C = A$

	$\overline{B} \overline{C}$	$\overline{B} C$	$B C$	$B \overline{C}$
\overline{A}	X	1	0	X
A	X	1	0	X

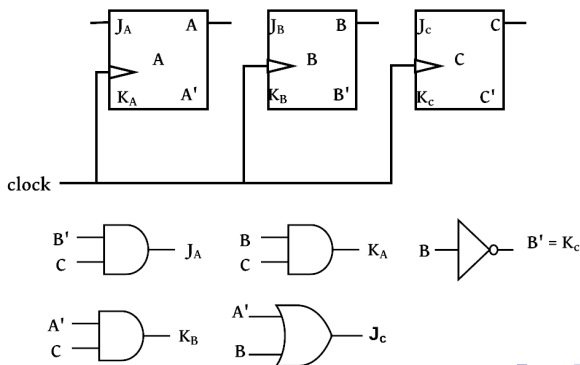Table 6: $K_C = \overline{A}C$ 

Synchronous: Decade counter

- Design a synchronous decade (count till 10 states) counter using D flip-flop.
- According to $2^n \geq N$. Here, $N = 10$ therefore $n = 4$ flip-flops.

Present state				Next state				Flip flop inputs			
A	B	C	D	D_{+1}	C_{+1}	B_{+1}	A_{+1}	D_D	D_C	D_B	D_A
0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	1	0	0	1	0	0	0	1	0
0	0	1	0	0	0	1	1	0	0	1	1
0	0	1	1	0	1	0	0	0	1	0	0
0	1	0	0	0	1	0	1	0	1	0	1
0	1	0	1	0	1	1	0	0	1	1	0
0	1	1	0	0	1	1	1	0	1	1	1
0	1	1	1	1	0	0	0	1	0	0	0
1	0	0	1	0	0	0	0	0	0	0	0

Decade K-map

For Q_{D+1}

$Q_D \backslash Q_C$	$Q_B \ Q_A$ 00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	X	X	X	X
10	1	0	X	X

$$Q_{D+1} = Q_D \bar{Q}_A + Q_C Q_B Q_A$$

For Q_{C+1}

$Q_D \backslash Q_C$	$Q_B \ Q_A$ 00	01	11	10
00	0	0	1	0
01	1	1	0	1
11	X	X	X	X
10	0	0	X	X

$$Q_{C+1} = Q_C \bar{Q}_B + Q_C \bar{Q}_A + \bar{Q}_C Q_B Q_A$$

For Q_{B+1}

$Q_D \backslash Q_C$	$Q_B \ Q_A$ 00	01	11	10
00	0	1	0	1
01	0	1	0	1
11	X	X	X	X
10	0	0	X	X


$$Q_{B+1} = \bar{Q}_D \bar{Q}_B Q_A + Q_B \bar{Q}_A$$

For Q_{A+1}

$Q_D \backslash Q_C$	$Q_B \ Q_A$ 00	01	11	10
00	1	0	0	1
01	1	0	0	1
11	X	X	X	X
10	1	0	X	X

$$Q_{A+1} = \bar{Q}_A$$

Logic diagram

 

Steps to design a Asynchronous counter

- Determine the number of flip-flops needed.
- Choose the flip-flop to be used.
- Write the truth table for the counter.
- Derive the reset logic by K-map simplification.
- Draw the logic diagram.

Asynchronous: BCD ripple counter using JK Flip flop

- BCD counter goes through states 0-9, i.e. total 10 states. Thus, $N = 10$, and for $2^n \geq N$, we need $n = 4$ i.e. 4 flip-flops.

CLK	A	B	C	D	Y
1	0	0	0	0	1
1	0	0	0	1	1
1	0	0	1	0	1
1	0	0	1	1	1
1	0	1	0	0	1
1	0	1	0	1	1
1	0	1	1	0	1
1	0	1	1	1	1
1	1	0	0	0	1
1	1	0	0	1	1

CLK	A	B	C	D	Y
0	1	0	1	0	0
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	0	1	0
0	1	1	1	0	0
0	1	1	1	1	0


*Y is the output port of the BCD ripple counter

Contin..

- Derive the reset logic expression.

		CD			
		00	01	11	10
AB	00	1	1	1	1
	01	1	1	1	1
	11				
	10	1	1		

Figure 8: $Y = \overline{A} + \overline{B} \overline{C}$

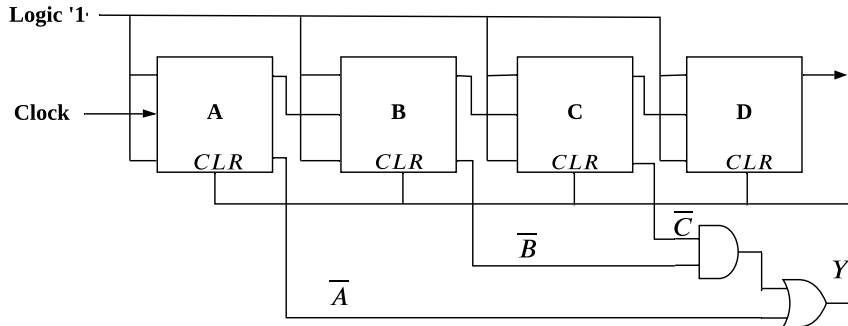

Mod-6 ripple counter using T flip-flop

- 0 - 5 states.
- According to $2^n \geq N$. Here, $N = 6$ therefore $n = 3$ flip-flops.

Clk	A	B	C	Y
0	0	0	0	1
1	0	0	1	1
2	0	1	0	1
3	0	1	1	1
4	1	0	0	1
5	1	0	1	1
-	1	1	0	0
-	1	1	1	0

K-map

		BC			
		00	01	11	10
A	0	1	1	1	1
	1	1	1		

Figure 9: $Y = \overline{A} + \overline{B}$

Logic diagram

 


Figure 10: Logic diagram

Ring Counter


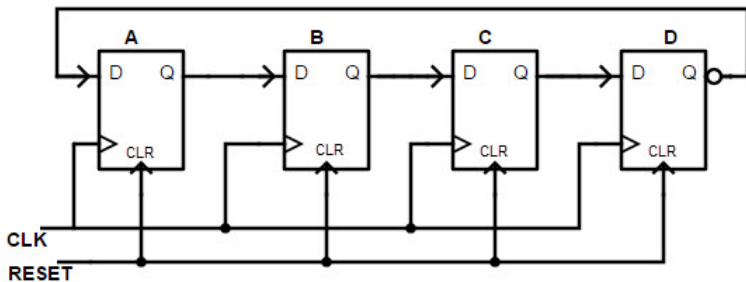


Figure 11: Ring Counter

Johnson Counter

 

Johnson counter (note the \overline{Q}_D to D_A feedback connection)

Figure 12: Johnson Counter