

5. WAVE SHAPING CIRCUIT USING OPERATIONAL AMPLIFIER - CLIPPER AND CLAMPER

5.1 OBJECTIVE

a. To study the operation of wave shaping circuits (clipper and clamper) using op-amps, such as half wave rectifier and full wave rectifier

5.2 HARDWARE REQUIRED

1	IC 741	Refer data sheet in appendix	1
2	Cathode Ray Oscilloscope	(0 – 20MHz) 1	1
3	Resistors	2.2 K Ω , 4.7K, 10KPOT	3
4	Semiconductor(Diode)	1N4002	2
5	Dual Regulated power supply	(0 -30V), 1A	1
6	Function Generator	(0-2) MHz	1
7	ASLK PRO Kit	Refer data sheet in appendix	1

5.2.1 THEORY

ACTIVE CLIPPER

Clipper is a circuit that is used to clip off (remove) a certain portion of the input signal to obtain a desired output wave shape. In op-amp clipper circuits, a rectified diode may be used to clip off certain parts of the input signal. Fig. 2-2-4 (a) shows an active positive clipper, a circuit that removes positive parts of the input signal. The clipping level is determined by the reference voltage

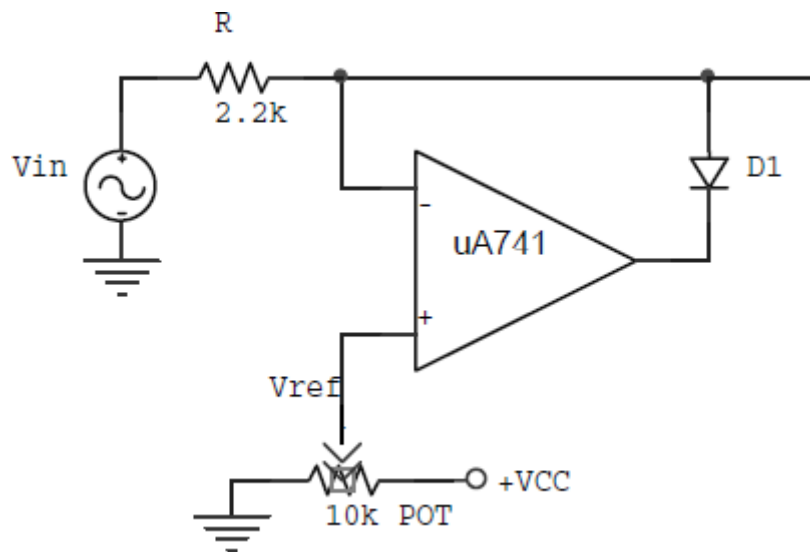


Fig 5(a) Active clipper

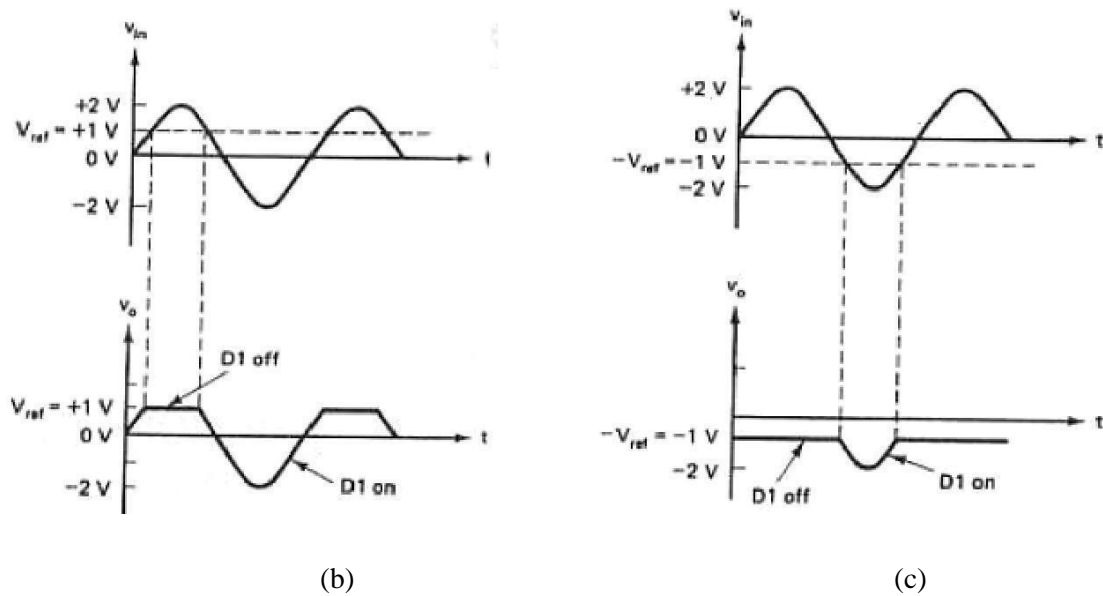


Fig 4 (b) input & output waveforms with $+V_{ref}$, (c) input & output waveforms with $-V_{ref}$


With the wiper all the way to the left, V_{ref} is 0 and the non-inverting input is grounded. When V_{in} goes positive, the error voltage drives the op-amp output negative and turns on the diode. This means the final output V_O is 0 (same as V_{ref}) for any positive value of V_{in} .

When V_{in} goes negative, the op-amp output is positive, which turns off the diode and opens the loop. When this happens, the final output V_O is free to follow the negative half cycle of the input voltage. This is why the negative half cycle appears at the output. To change the clipping level, all we do is adjust V_{ref} as needed.

Active clamper

In clamper circuits, a predetermined dc level is added to the input voltage. In other words, the output is clamped to a desired dc level. If the clamped dc level is positive, the clamper is called a *positive clamper*. On the other hand, if the clamped dc level is negative, it is called a *negative clamper*. The other equivalent terms for clamper are *dc inserter* or *dc restorer*.

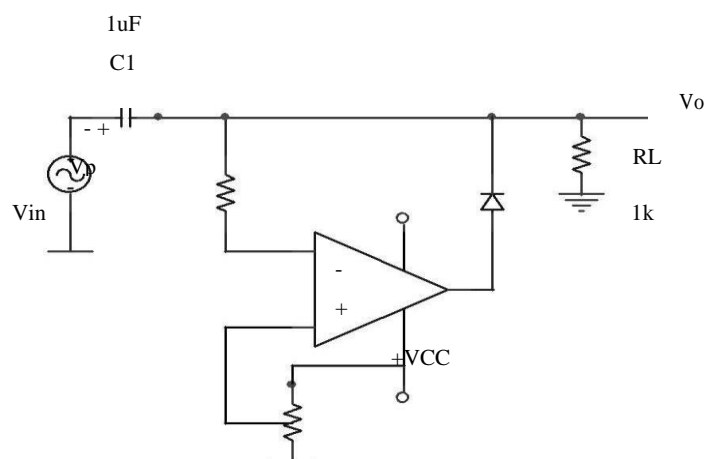A clamper circuit with a variable dc level is shown in fig (a). Here the input wave form is clamped at $+V_{ref}$ and hence the circuit is called a positive clamper.




$$R=4.7k, R_p=10k$$


Fig 5 (b) Peak clamper circuit

The output voltage of the clamper is a net result of ac and dc input voltages applied to the inverting and non-inverting input terminals respectively. Therefore, to understand the circuit Operation, each input must be considered separately. First, consider V_{ref} at the non-inverting Input. Since this voltage is positive, $+V_O$ is positive, which forward biases diode D1. This closes the feedback loop and the op-amp operates as a voltage follower. This is possible because C_1 is an open circuit for dc voltage. Therefore $V_O = V_{ref}$. As for as voltage V_{in} at the


Inverting input is concerned during its negative half-cycle D1 conducts, charging C_1 to the negative peak value of the V_P . However, during the positive half-cycle of V_{IN} diode D1 is reverse biased and hence the voltage V_P across the capacitor acquired during the negative half-cycle is retained. Since this voltage V_P is in series with the positive peak voltage V_P , the output peak voltage $V_O=2V_P$. Thus the net output is $V_{ref} + V_P$, so the negative peak of $2V_P$ is at V_{ref} . For precision clamping $C_1 R_d \ll T/2$, where R_d is the forward resistance of the diode D1 (100Ω typically) and T is the time period of V_{IN} . The input and output wave forms are shown in figure.

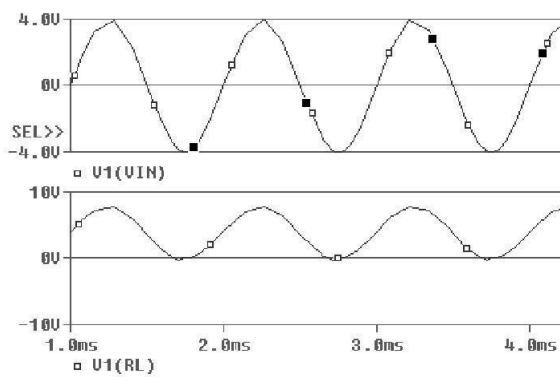

(i)

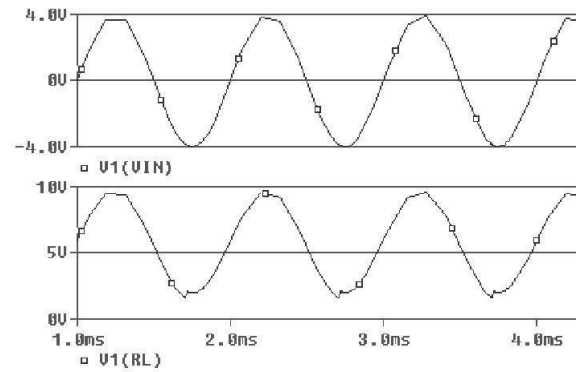

(ii)

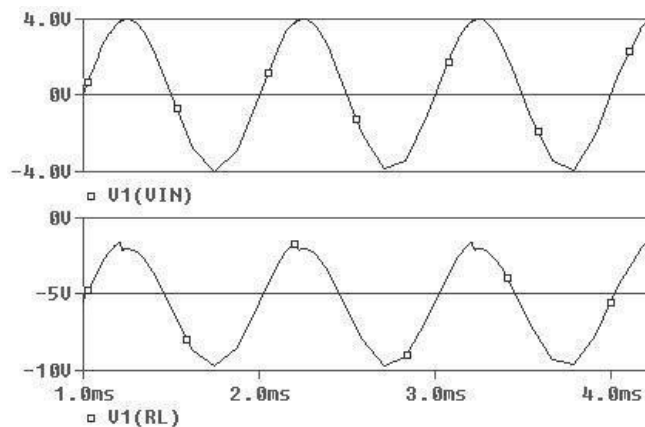

(iii)

Fig 5(c) Input and output waveforms (i) with $V_{ref}=0V$, (ii) with $+V_{ref}$, (iii) with $-V_{ref}$

Resistor R is used to protect the op-amp against excessive discharge currents from capacitor C1 especially when the dc supply voltages are switched off. Negative clamping at a negative voltage is accomplished by reversing diode D1 and using the negative reference voltage – V_{ref} .

5.2.2 Experiment

1. Connect the components/equipment $R=2.2K\Omega$ use IN4002 diode. Sinusoidal input amplitude 3v and frequency 1Khz.as shown in the circuit diagram.
2. Switch ON the power supply.
3. Apply 1V dc voltage as reference voltage at the inverting terminal of IC741.
4. Connect the channel-1 of CRO at the input terminals and channel-2 of CRO at the output terminals.
5. Observe the input sinusoidal signal at channel-1 and the corresponding output square wave at channel-2 of CRO. Note down their amplitude and time period.
6. Overlap both the input and output waves and note down voltages at positions on sine wave where the output changes its state. These voltages denote the Reference voltage.
7. Plot the output wave form.

Active clamper

1. Connect the components/equipment clamping level at zero as shown in fig.5 (a). Note that $V_{ref} = 0V$. Consider $C_1 = 0.1\mu F$, $R = 4.7 K\Omega$ and $R_L = 10 K\Omega$. Use IN4002 diode. Feed 5VPP, 10 KHz sinusoidal inputs.
2. Switch ON the power supply.
3. Apply 1V dc voltage as reference voltage at the inverting terminal of IC741.
4. Connect the channel-1 of CRO at the input terminals and channel-2 of CRO at the output terminals.
5. Observe the input sinusoidal signal at channel-1 and the corresponding output square wave at channel-2 of CRO. Note down their amplitude and time period.
6. Overlap both the input and output waves and note down voltages at positions on sine wave where the output changes its state. These voltages denote the Reference voltage.
7. Plot the output wave form.

Observation Clipper

Clipping Level =

Particulars	Amplitude	Time Period	Frequency
Input Voltage			
Output Voltage			


Observation Clamper

Clamping level =

Particulars	Amplitude	Time Period	Frequency
Input Voltage			
Output Voltage			

Prelab

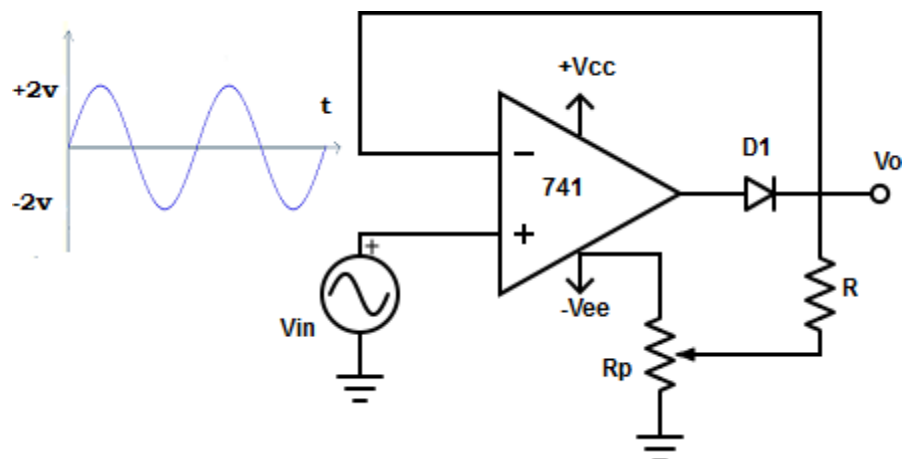
1. Find the output waveform for when $V_{in} < V_{ref}$




2. Determine the output waveform for a clamper with input $=4V_p$ sine wave and $V_{ref}=1V$.
3. Why clamper is called a DC restorer?
4. What are the applications of clippers and clammers?
5. What is the factor which determines clipping level in a clipper?

Postlab

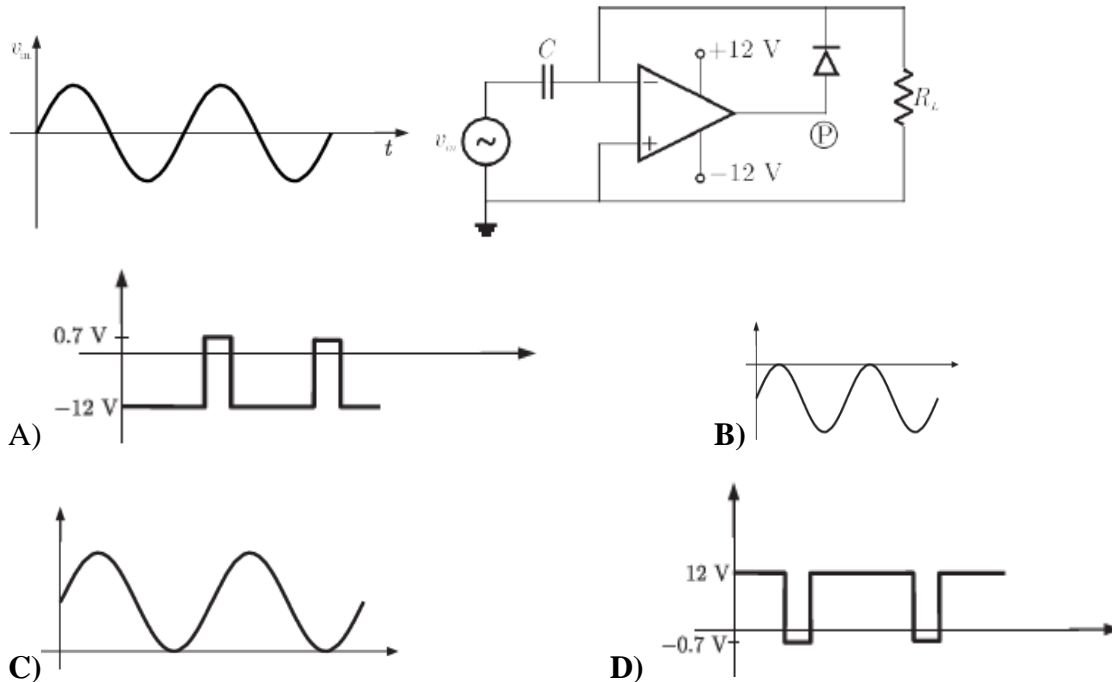1. For a given sinusoidal input voltage, the voltage waveform at point P of the clamper circuit shown in figure will be



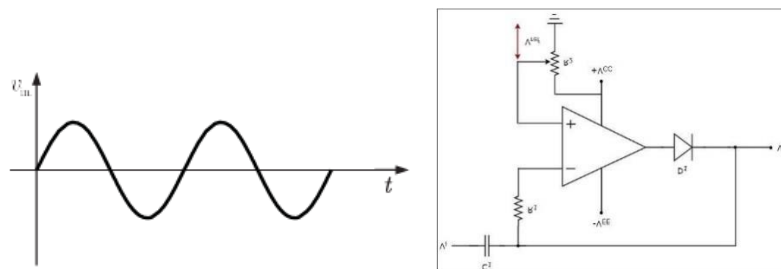2. Compare clipper with clamping circuit
3. Which elements are used in linear and non-linear wave shaping circuits?
4. Draw the output waveform for the following circuit



5. Sketch the negative clamper using opamp

Result