

DEPARTMENT OF ECE

SRM Nagar, Kattankulathur – 603203, Chengalpattu District, Tamilnadu



Academic Year: 2021-2022 (EVEN)
Test: CLAT-1
Date: 08.04.2022
Course Code & Title: 18ECE206J Advanced Digital System Design
Duration: 60 Minutes
Year & Sem: II & IV
Max. Marks: 25
Course Articulation Matrix:

18ECE206J / Advanced Digital System Design		Program Outcomes (POs)														
		Graduate Attributes												Program Specific Outcomes (PSO)		
S. No.	Course Outcomes (CO):	1	2	3	4	5	6	7	8	9	10	11	12	1	2	3
1	Apply advanced theorems to simplify the design aspects of various practical circuits	2	-	2	-	-	-	-	-	-	-	-	-	-	-	-
2	Analyze synchronous sequential circuits and write VHDL Code	-	2	2	-	-	-	-	-	-	-	-	-	-	-	-
3	Analyze Asynchronous sequential circuits and construct circuit using VHDL	-	2	2	-	-	-	-	-	-	-	-	-	-	-	-
4	Implement various digital circuits using Programmable Logic Devices	-	2	2	-	-	-	-	-	-	-	-	-	-	-	-
5	Demonstrate FPGAs and Construct digital circuits using VHDL.	-	3	3	-	3	-	-	-	-	-	-	-	-	-	2
6	Perform experiments in the laboratory with hardware and software to simulate and verify the design	-	-	-	-	3	-	-	-	2	-	-	3	3	-	2

Part - A (5 x 1 = 5 Marks) Answer all						
Q. No	Question	Marks	BL	CO	PO	PI Code
1	For Minimizing Multiple Output Logic Circuits, to use (a) Shannon's theorem (b) K-Map (c) Consensus theorem (d) Reed Muller Expansion	1	1	1	1,3	1.1.1 3.1.1
2	How many states and flip flops required for Moore model of the given sequence "101011"? (a) 6,3 (b) 7,3 (c) 7,7 (d) 6,6	1	2	1	1,3	1.1.1 3.1.1
3	Which among the following constraint/s is/are involved in a state-machine description? (a) State variable & clock (b) State transitions & output specifications	1	1	1	1,3	1.1.1 3.1.1

	(c) Reset condition (d) a,b and c					
4	The elements used in the State diagram are (a) Transition (b) Condition (c) Iteration (d) Optional	1	1	1	1,3	1.1.1 3.1.1
5	One of the Reed muller rule $A+B=?$ (a) $A \oplus B \oplus AB$ (b) $A' \oplus B \oplus AB$ (c) $A \oplus A'B$ (d) Both (a) and (c)	1	2	1	1,3	1.1.1 3.1.1
Part – B (2 x 10 = 20 Marks) Answer any two						
6	Design a circuit to detect the sequence pattern “1110” using Mealy Non overlapping and D flip flop.	10	3	1	1,3	1.1.1 3.1.1
7	Design a sequential circuit for the following state using T flip flop. 0-1-2-3-4-5-6-7-0	10	3	1	1,3	1.1.1 3.1.1
8	(i) Implement full adder using 4 to 1 MUX (ii) What is Reed Muller expansion theorem? Expand the following expression using it and draw the circuit diagram $F=A'B' + AB$	5 5	2	1	1,3	1.1.1 3.1.1

  Course Outcome (CO) and Bloom's level (BL) Coverage in Questions



Evaluation Sheet

Name of the Student:

Register No.:

Part- A (5x 1= 5 Marks)			
Q. No	CO	Marks Obtained	Total
1	1		
2	1		
3	1		
4	1		
5	1		
Part- B (2 x 10= 20 Marks)			
6	1		
7	1		
8	1		

Consolidated Marks:

CO	Marks Scored
CO1	
Total	

Approved by the Course Coordinator

DEPARTMENT OF ECE

SRM Nagar, Kattankulathur – 603203, Chengalpattu District, Tamilnadu

Academic Year: 2021-2022 (EVEN)
Test: CLAT-1
Date: 08.04.2022
Course Code & Title: 18ECE206J Advanced Digital System Design
Duration: 60 Minutes
Year & Sem: II & IV
Max. Marks: 25
Course Articulation Matrix:



18ECE206J / Advanced Digital System Design		Program Outcomes (POs)														
		Graduate Attributes												Program Specific Outcomes (PSO)		
S. No.	Course Outcomes (CO):	1	2	3	4	5	6	7	8	9	10	11	12	1	2	3
1	Apply advanced theorems to simplify the design aspects of various practical circuits	2	-	2	-	-	-	-	-	-	-	-	-	-	-	-
2	Analyze synchronous sequential circuits and write VHDL Code	-	2	2	-	-	-	-	-	-	-	-	-	-	-	-
3	Analyze Asynchronous sequential circuits and construct circuit using VHDL	-	2	2	-	-	-	-	-	-	-	-	-	-	-	-
4	Implement various digital circuits using Programmable Logic Devices	-	2	2	-	-	-	-	-	-	-	-	-	-	-	-
5	Demonstrate FPGAs and Construct digital circuits using VHDL.	-	3	3	-	3	-	-	-	-	-	-	-	-	-	2
6	Perform experiments in the laboratory with hardware and software to simulate and verify the design	-	-	-	-	3	-	-	-	2	-	-	3	3	-	2

Part - A
(5 x 1 = 5 Marks)
Answer all

Q. No	Question	Marks	BL	CO	PO	PI Code
1	Which theorem is used for eliminating the complement term? (a) Shannon's (b) Reed Muller (c) Consensus (d) De Morgan's	1	1	1	1,3	1.1.1 3.1.1
2	How many states and flip flop required for Mealey model of the given sequence "10011" (a) 5,3 (b) 5,5 (c) 6,3 (d) 6,5	1	2	1	1,3	1.1.1 3.1.1
3	A 2 to 1 MUX can be used to realize which of the following (a) only AND,NOT (b) only OR (c) only NOT	1	1	1	1,3	1.1.1 3.1.1

	(d) AND,OR ,NOT					
4	In a sequence detector, if the required bit is at its input while checking the sequence bit by bit, the detector moves to (a) Previous state (b) Next state (c) Remains in the same state (present state) (d) Null state	1	1	1	1,3	1.1.1 3.1.1
5	$A \oplus B \oplus BA \oplus B \oplus = ?$ (a) $A \oplus AB$ (b) A (c) $A \oplus B$ (d) B	1	2	1	1,3	1.1.1 3.1.1
Part – B (2 x 10 = 20 Marks) Instructions: Answer any two						
6	Design a circuit to detect the sequence pattern “1110” using Moore Non overlapping and D flip flop.	10	3	1	1,3	1.1.1 3.1.1
7	Design a sequential circuit for the following state using T flip flop. 7-6-5-4-3-2-1-0-7	10	3	1	1,3	1.1.1 3.1.1
8	(i) Simplified the following expressing using Reed Muller expansion and draw the circuit. $F(A, B, C) = \sum (1,3,5,6)$ (ii) Implement full subtractor using 4 to 1 MUX	5 5	2	1	1,3	1.1.1 3.1.1

  Course Outcome (CO) and Bloom's level (BL) Coverage in Questions



Evaluation Sheet

Name of the Student:

Register No.:

Part- A (5x 1= 5 Marks)			
Q. No	CO	Marks Obtained	Total
1	1		
2	1		
3	1		
4	1		
5	1		
Part- B (2 x 10= 20 Marks)			
6	1		
7	1		
8	1		

Consolidated Marks:

CO	Marks Scored
CO1	
Total	

Approved by the Course Coordinator