

Reg. No.	PA	20	11	00	40	10	22	6
----------	----	----	----	----	----	----	----	---

## B.Tech. DEGREE EXAMINATION, JULY 2022

Fourth Semester

### 18ECC201J – ANALOG ELECTRONIC CIRCUITS

(For the candidates admitted from the academic year 2020-2021 to 2021-2022)

**Note:**

- (i) **Part - A** should be answered in OMR sheet within first 40 minutes and OMR sheet should be handed over to hall invigilator at the end of 40<sup>th</sup> minute.
- (ii) **Part - B** should be answered in answer booklet.

Time: 2½ Hours

Max. Marks: 75

#### PART – A (25 × 1 = 25 Marks)

Marks BL CO PO

Answer **ALL** Questions

- |   |                |
|---|----------------|
| <p>1. What is the condition of <math>I_C</math> and <math>V_{CE}</math> to determine the cutoff and saturation point of DC load line?</p> <p>(A) <math>I_C = 5mA, V_{CE} = 0</math> (B) <math>I_C = 0, V_{CE} = 0</math></p> <p>(C) <math>I_C = 0, V_{CE} = 10V</math> (D) <math>I_C = \text{Infinity}, V_{CE} = 0</math></p>   | <p>1 2 1 2</p> |
| <p>2. The two stage CC-CC amplifier is also called as _____</p> <p>(A) Oscillator (B) Current buffer</p> <p>(C) Darlington pair (D) Phase shifter</p>   | <p>1 1 1 1</p> |
| <p>3. Find <math>V_{th}</math> and <math>R_{th}</math> of a voltage divider circuit having <math>V_{CC} = 18V</math>, <math>R_1 = 33K</math> and <math>R_2 = 12K</math>.</p> <p>(A) <math>V_{th} = 4.8V, R_{th} = 8.8K\Omega</math> (B) <math>V_{th} = 5.8V, R_{th} = 9.8K\Omega</math></p> <p>(C) <math>V_{th} = 5.8V, R_{th} = 10.8K\Omega</math> (D) <math>V_{th} = 6.8V, R_{th} = 7.8K\Omega</math></p> | <p>1 2 1 2</p> |
| <p>4. A certain cascaded amplifier arrangement has the following voltage gains <math>A_{v1} = 10</math>, <math>A_{v2} = 15</math>, <math>A_{v3} = 20</math>. What is the overall voltage gain and voltage gain in dB?</p> <p>(A) 3000, 69.5 dB (B) 2000, 59.5 dB</p> <p>(C) 1000, 79.5 dB (D) 4000, 89.5 dB</p>   | <p>1 2 1 2</p> |
| <p>5. The transconductance <math>g_m</math> of a BJT hybrid <math>\pi</math> model is</p> <p>(A) <math>\frac{V_T}{r_o}</math> (B) <math>\frac{I_{CQ}}{\beta f}</math></p> <p>(C) <math>\frac{V_T}{I_{CQ}}</math> (D) <math>\frac{I_{CQ}}{V_T}</math></p>  | <p>1 1 1 1</p> |
| <p>6. Find <math>V_{gsQ}</math> if <math>I_{DQ} = 1mA</math>, <math>K_n = 1mA/V^2</math>, <math>V_{tn} = 1V</math>.</p> <p>(A) 1 V (B) 2V</p> <p>(C) 3 V (D) 4V</p>   | <p>1 2 2 2</p> |
| <p>7. Source follower can be used as</p> <p>(A) Phase shifter (B) Attenuator</p> <p>(C) Buffer (D) Oscillator</p>   | <p>1 1 2 1</p> |
| <p>8. When a common source amplifier is analysed using hybrid <math>\pi</math> model for high frequency response, the miller capacitance <math>C_m</math> is calculated as _____</p> <p>(A) <math>C_m = 1 + g_m R_L</math> (B) <math>C_m = C_{ds}(1 + g_m R_L)</math></p> <p>(C) <math>C_m = C_{gs}(1 + g_m R_L)</math> (D) <math>C_m = C_{gd}(1 + g_m R_L)</math></p>                                      | <p>1 2 2 3</p> |
| <p>9. Which of the following small signal equivalent circuit parameter of FET amplifier takes channel length modulation effect into consideration?</p> <p>(A) <math>g_m</math> (B) <math>r_\pi</math></p> <p>(C) <math>r_o</math> (D) <math>V_{gsQ}</math></p>  | <p>1 1 2 3</p> |
| <p>10. What is the phase difference between the input signal and the output signal of a common gate amplifier?</p> <p>(A) 0° (B) 90°</p> <p>(C) 45° (D) 180°</p>  | <p>1 1 2 1</p> |

11. Calculate the feedback transfer function  $\beta$ , if  $A = 10^5$  and  $A_f = 50$ .  
 (A) 0.09 (B) 0.019\*  
 (C) 0.9 (D) 0.39
12. In a voltage series feedback amplifier, input impedance \_\_\_\_\_ and output impedance \_\_\_\_\_ by the factor of  $(1 + \beta A)$ .  
 (A) decreases, decreases (B) increases, increases  
 (C) decreases, increases (D) increases, decreases
13. In Colpitt oscillator if  $C_1 = 0.2\mu f$  and  $C_2 = 0.02\mu f$ ,  $f_{osc} = 10KHz$ , find the value of  $L_{eq}$ .  
 (A) 15.9 mH (B) 13.932 mH  
 (C) 14.9 mH (D) 12.93 mH
14. Which one of the following is used as audio frequency oscillator?  
 (A) Wein bridge oscillator (B) Hartley oscillator  
 (C) Colpitt oscillator (D) Crystal oscillator
15. Current series feedback amplifier is a \_\_\_\_\_.  
 (A) Transresistance amplifier (B) Current amplifier  
 (C) Voltage amplifier (D) Transconductance amplifier
16. The efficiency of Class B amplifier is \_\_\_\_\_.  
 (A) 50% (B) 100%  
 (C) 90% (D) 78.5%.
17. In a transformer coupled Class A power amplifier if  $V_{CE(max)} = 15V$ ,  $V_{CE(min)} = 1V$ , find its overall efficiency.  
 (A) 43.75% (B) 53.75%  
 (C) 63.75% (D) 73.75%
18. Cross over distortion occurs in \_\_\_\_\_ amplifier.  
 (A) Push-pull. (B) Class A  
 (C) Class C (D) Class D
19. Calculate the effective resistance looking into the primary of a 15:1 transformer connected to an output load of  $R_L = 8\Omega$ .  
 (A)  $R_L' = 2.8\Omega$  (B)  $R_L' = 1.8\Omega$   
 (C)  $R_L' = 0.8\Omega$  (D)  $R_L' = 2.8k\Omega$
20. What is the advantage of a Complementary Symmetry Push-Pull amplifier?  
 (A) No need of a resistor. (B) Use of transformer  
 (C) Use of dual power supply (D) No need of transformer
21. \_\_\_\_\_ current mirror is used as a current source.  
 (A) PMOS (B) NMOS  
 (C) CMOS. (D) BiCMOS
22. If output is measured between two collectors of BJT transistors, then the differential amplifier with two input signal is said to be configured as \_\_\_\_\_.  
 (A) Dual input, Balanced output. (B) Dual input, Unbalanced output  
 (C) Single input, Balanced output (D) Dual input, Unbalanced output
23. Give the relationship between the output current ( $I_0$ ) and the reference current ( $I_{ref}$ ) of a BJT two transistor current mirror.  
 (A)  $I_0 = \frac{I_{ref}}{\left(\beta + \frac{2}{\beta}\right)}$  (B)  $I_0 = \frac{I_{ref}}{\left(1 + \frac{2}{\beta}\right)}$   
 (C)  $I_0 = \frac{I_{ref}}{I_0 \left(1 + \frac{2}{\beta}\right)}$  (D)  $I_0 = \frac{\left(1 + \frac{2}{\beta}\right)}{I_{ref}}$

24. Mention the significance of the design of differential amplifier configuration.
- (A) To increase the bias current (B) To reduce the power consumption  
(C) To minimize the effect of common mode input signal (D) To increase the speed of operation.

1 1 5 3

25. Active loads are essentially \_\_\_\_\_ used in the place of resistive loads.
- (A) voltage amplifiers (B) transistor current sources  
(C) Capacitors (D) Transformers

1 1 5 3


**PART - B (5 × 10 = 50 Marks)**

Answer **ALL** Questions

Marks BL CO PO

26. a.i. In the emitter bias circuit shown, determine the Q point for  $\beta = 85$  and  $V_{BE} = 0.7V$ .

4 4 1 2

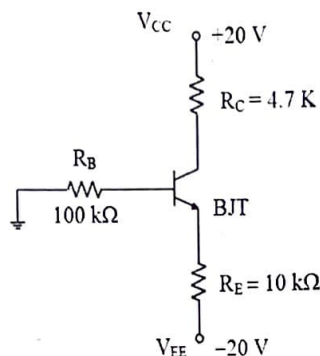


- ii. Draw the hybrid  $\pi$  model for a common collector amplifier and derive the expression for output impedance.

6 3 1 3

(OR)

- b.i. Consider a BJT common emitter amplifier given is the figure having  $R_1 = 56k\Omega$ ,  $R_2 = 12.2k\Omega$ ,  $R_c = 2k\Omega$ ,  $R_E = 0.4k\Omega$ ,  $V_{cc} = 10V$ ,  $V_{BE(ON)} = 0.7V$ ,  $\beta = 100$ ,  $V_A = \infty$ ,  $R_s = 0.5k$ . Calculate  $r_\pi$ ,  $g_m$ ,  $r_o$ ,  $R_{ib}$ ,  $R_i$  and voltage gain  $A_v$ .

8 4 1 2

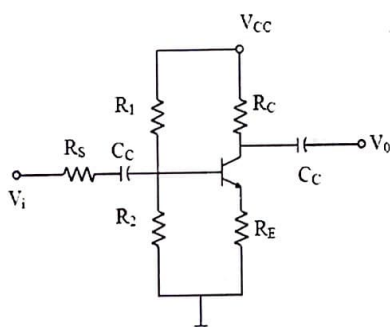

- ii. Calculate the cutoff frequency of a bipolar common emitter amplifier with a coupling capacitor having  $R_1 = 51.2k\Omega$ ,  $R_2 = 9.6k\Omega$ ,  $r_\pi = 1.44k\Omega$ ,  $\beta = 100$ ,  $R_E = 0.4k\Omega$ ,  $R_s = 0.1k\Omega$ , coupling capacitor  $C_C = 1\mu f$ .


2 4 1 2

27. a.i. Using small signal circuit of common gate amplifier, derive the voltage gain  $A_v$ .

5 3 2 3

- ii. Calculate the small signal voltage gain of the source follower circuit given below. The circuit parameters are  $V_{DD} = 12V$ ,  $R_1 = 162k\Omega$ ,  $R_2 = 463k\Omega$ ,  $R_s = 0.75k\Omega$ ,  $V_{Tn} = 1.5V$ ,  $K_n = 4mA/V^2$ ,  $\lambda = 0.01V^{-1}$  and  $R_{si} = 4k\Omega$ .

5 3 2 2

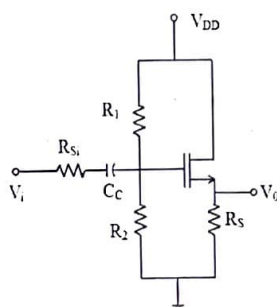

(OR)




b.i. Derive the voltage gain of a common source amplifier with source resistance.

6 3 2 3

ii. Determine the value of the coupling capacitor in the circuit given if  $f_L = 20\text{KHz}$

4 4 2 2

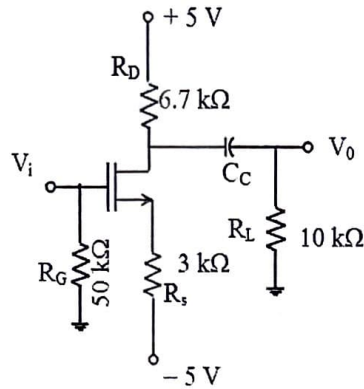

28. a.i. With necessary expressions, discuss the effect of negative feedback on gain, gain sensitivity, bandwidth and noise of an amplifier.

4 3 3 1

ii. A voltage series negative feedback amplifier has a voltage gain without feedback of  $A=500$ , input resistance  $R_i = 3\text{k}\Omega$ , output resistance  $R_o = 20\text{k}\Omega$  and feedback ratio  $\beta = 0.01$ . Calculate the voltage gain  $A_f$ , input resistance  $R_{if}$ , and output resistance  $R_{of}$  of the amplifier with feedback.

6 3 3 2

(OR)

b.i. Define Barkhausen criteria and explain the operation of a wein bridge oscillator and derive its frequency of oscillation.

8 3 3 3

ii. Determine the frequency of oscillation of BJT RC phase shift oscillator if  $R_1 = 25\text{k}\Omega$ ,  $R_2 = 60\text{k}\Omega$ ,  $R_c = 40\text{k}\Omega$ ,  $R = 7.1\text{k}\Omega$ ,  $h_{ie} = 1.8\text{k}\Omega$  and  $C = 0.41\text{nf}$ .


2 3 3 2

29. a.i. Compare the operating characteristics of Class A, Class B, Class AB and Class C power amplifier.

4 3 4 1

ii. Calculate the input power, output power and efficiency of the Class -A power amplifier given below.

6 3 4 2

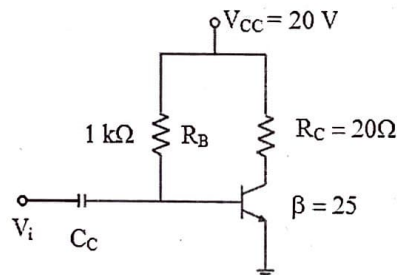

(OR)

b.i. Discuss briefly on the operation of class C power amplifier and write its efficiency expression.

3 3 4 3

ii. Derive the efficiency of class B power amplifier and explain its push-pull configuration.

7 3 4 3

30. a.i. Write short notes on BJT multi transistor current mirror and give its output current expression.

4 3 5 3

ii. Discuss the operation of FET two transistor current source and derive its output current.

6 3 5 3

(OR)

b.i. With neat diagrams and necessary expressions, explain the operation of basic BJT differential amplifier and its small signal equivalent circuit.

8 3 5 3

ii. Draw the circuit diagram of BJT differential amplifier with active load and write its differential gain expression.

2 3 5 3

\* \* \* \* \*