
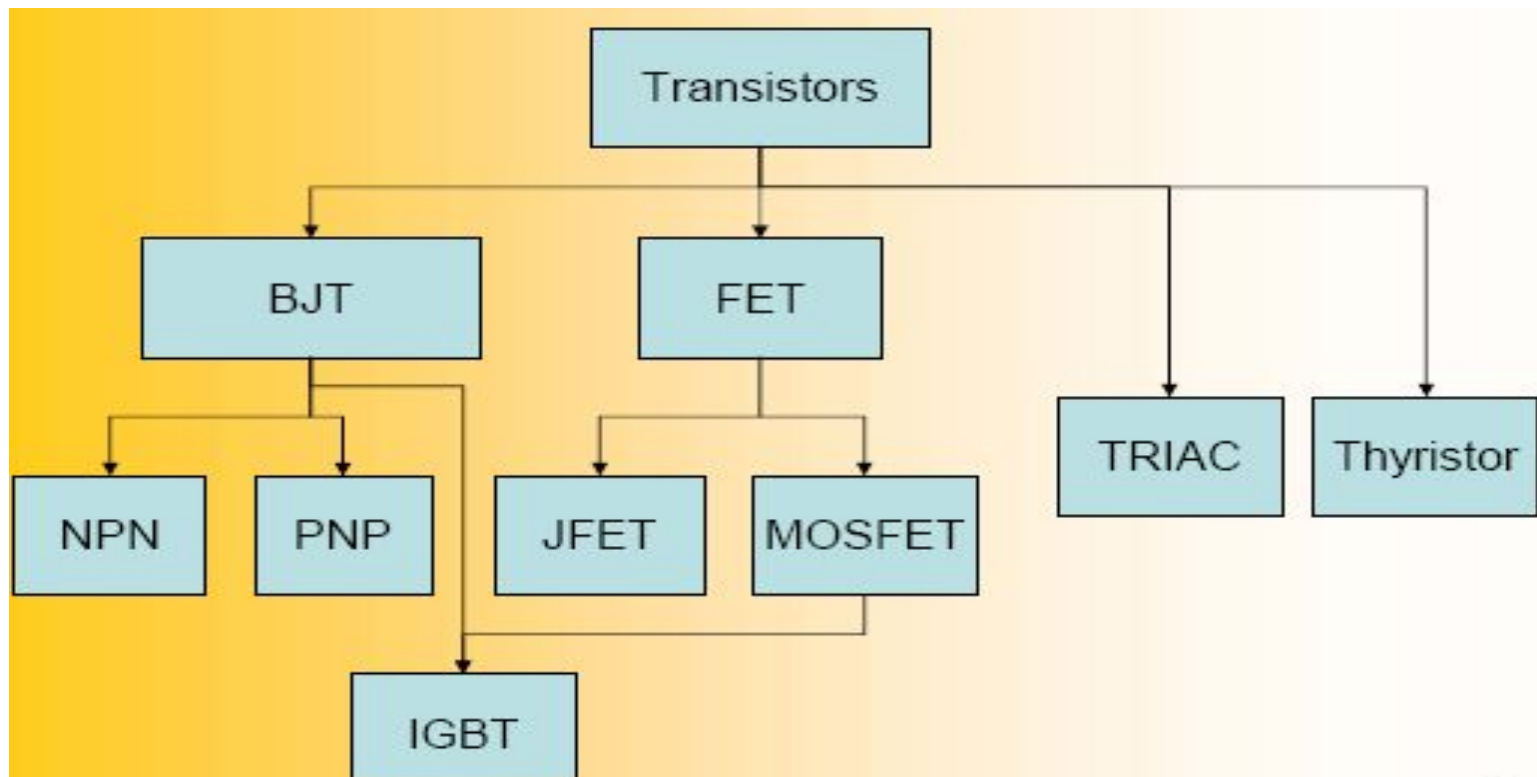


Introduction

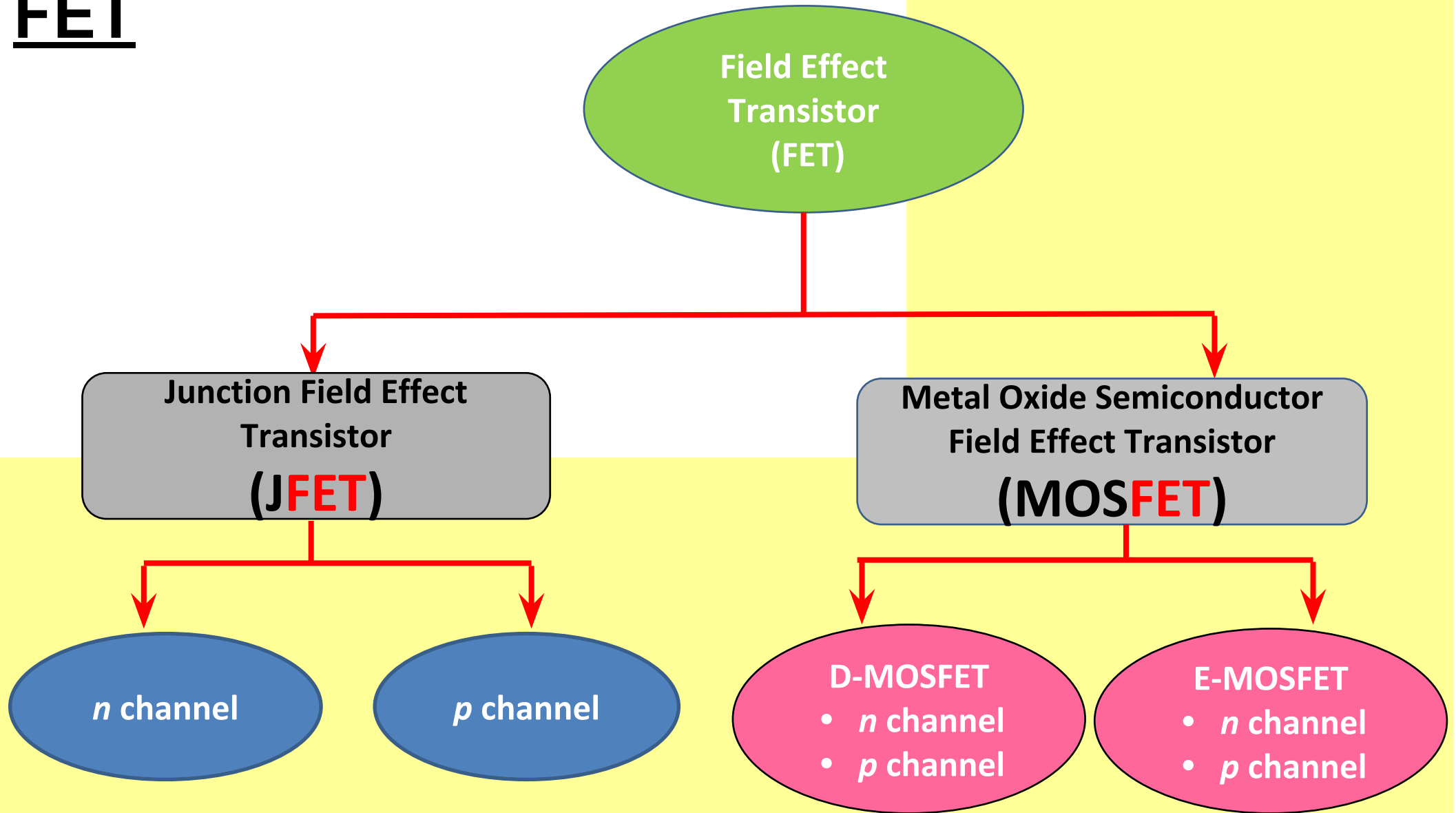- ❑ Field-effect transistors (FETs) are probably the simplest form of transistor
- ❑ Widely used in both analogue and digital applications
- ❑ Are characterized by a very high input resistance and small physical size, and they can be used to form circuits with a low power consumption
- ❑ Are widely used in very large-scale integration



FET



MOSFET (Types)

- Four types:



- n-channel enhancement mode

- Most common since it is cheapest to manufacture


- p-channel enhancement mode

- n-channel depletion mode

- p-channel depletion mode

  



Depletion type

 

Enhancement type


An Overview of Field-Effect Transistors

  - ❑ Many forms, but basic operation is the same
- ❑ A voltage on a control input produces an electric field that affects the current between two other terminals
- ❑ when considering amplifiers we looked at a circuit using a ‘control device’
- ❑ FET is a suitable control device



Notation

 - ❑ FETs are 3 terminal devices
- ❑ drain (d)
- ❑ source (s)
- ❑ gate(g)
- ❑ the gate is the control input





Insulated-Gate Field-Effect Transistors

- ❑ Such devices are sometimes called IGFETs (insulated-gate field-effect transistors) or sometimes MOSFETs (metal oxide semiconductor field-effect transistors)
- ❑ Digital circuits constructed using these devices are usually described as using MOS technology
- ❑ Here we will describe them as MOSFETs


Device Structure and Physical Operation

Device structure of MOSFET

  

- ❑ “MOS” \equiv metal-oxide-semiconductor structure
- ❑ MOSFET is a four-terminal device: gate (G), source (S), drain (D) and body (B)
- ❑ The device size (channel region) is specified by channel width (W) and channel length (L)
- ❑ Two kinds of MOSFETs: n -channel (NMOS) and p -channel (PMOS) devices
- ❑ The device structure is basically symmetric in terms of drain and source
- ❑ Source and drain terminals are specified by the operation voltage

Structure: *n*-channel MOSFET (NMOS)

 


Operation with zero gate voltage

- ❑ The MOS structure form a parallel-plate capacitor with gate oxide layer in the middle
- ❑ Two pn junctions (S-B and D-B) are connected as back to back diodes
- ❑ The source and drain terminals are isolated by two depletion regions without conducting current
- ❑ The operating principles will be introduced by using the n -channel MOSFET as an example



Creating a channel for current flow

- ❑ Positive charges accumulate in gate as a positive voltage applies to gate electrode
- ❑ Electric field forms a depletion region by pushing holes in p -type substrate away from the surface
- ❑ Electrons accumulate on the substrate surface as gate voltage exceeds a **threshold voltage** V_t
- ❑ The induced n region thus forms a **channel** for current flow from drain to source
- ❑ The channel is created by inverting the substrate surface from p -type to n -type → **inversion layer**
- ❑ The field controls the amount of charge in the channel and determines the channel conductivity

 



Applying a small drain voltage

- ❑ A positive $v_{GS} > V_t$ is used to induce the channel \rightarrow n -channel **enhancement-type** MOSFET
- ❑ Free electrons travel from source to drain through the induced n -channel due to a small v_{DS}
- ❑ The current i_D flows from drain to source (opposite to the direction of the flow of negative charge)
- ❑ The current is proportional to the number of carriers in the induced channel
- ❑ The channel is controlled by the **effective voltage** or **overdrive voltage**: $v_{OV} \equiv v_{GS} - V_t$
- ❑ The electron charge in the channel due to the overdrive voltage: $|Q| = C_{ox} W L v_{OV}$
- ❑ **Gate oxide capacitance** C_{ox} is defined as capacitance per unit area
- ❑ MOSFET can be approximated as a linear resistor in this region with a resistance value inversely proportional to the excess gate voltage

  

Operation as increasing drain voltage

- ❑ As v_{DS} increases, the voltage along the channel increases from 0 to v_{DS}
- ❑ The voltage between the gate and the points along the channel decreases from v_{GS} at the source end to $(v_{GS} - v_{DS})$ at the drain end
- ❑ Since the inversion layer depends on the voltage difference across the MOS structure, increasing v_{DS} will result in a tapered channel
- ❑ The resistance increases due to tapered channel and the $i_D - v_{DS}$ curve is no longer a straight line
- ❑ At the point $v_{DSsat} = v_{GS} - V_t$, the channel is **pinched off** at the drain side
- ❑ Increasing v_{DS} beyond this value has little effect on the channel shape and i_D saturates at this value
- ❑ **Triode region:** $v_{DS} < v_{DSsat}$
- ❑ **Saturation region:** $v_{DS} \geq v_{DSsat}$

  

□ Induced charge in the channel due to MOS capacitor:

$$Q_I(x) = -C_{ox} [v_{GS} - V_t - v(x)]$$

□ Equivalent resistance dR along the channel:

$$dR = \frac{dx}{qn(x)\mu_n h(x)W} = \frac{dx}{\mu_n W Q_I(x)}$$

□ I-V derivations: (more detail in next slide)

$$dv = i_D dR = \frac{i_D dx}{\mu_n W Q_I(x)} = \frac{i_D dx}{\mu_n C_{ox} W [v_{GS} - V_t - v(x)]}$$

$$\int_0^{v_{DS}} \mu_n C_{ox} W [v_{GS} - V_t - v(x)] dv = \int_0^{i_D} i_D dx$$

$$i_D = \mu_n C_{ox} \frac{W}{L} \left[(v_{GS} - V_t) v_{DS} - \frac{1}{2} v_{DS}^2 \right]$$

■ Process transconductance parameter

■ Aspect ratio: W/L

■ Transconductance parameter ($\mu A/V^2$): $k_n = \mu_n C_{ox} (W/L)$



□ Drain current of MOSFETs:

■ Triode region:


■ Saturation region

□ On-resistance (channel resistance for small v_{DS}):

$$r_{DS} = 1/k_n (v_{GS} - V_t)$$

 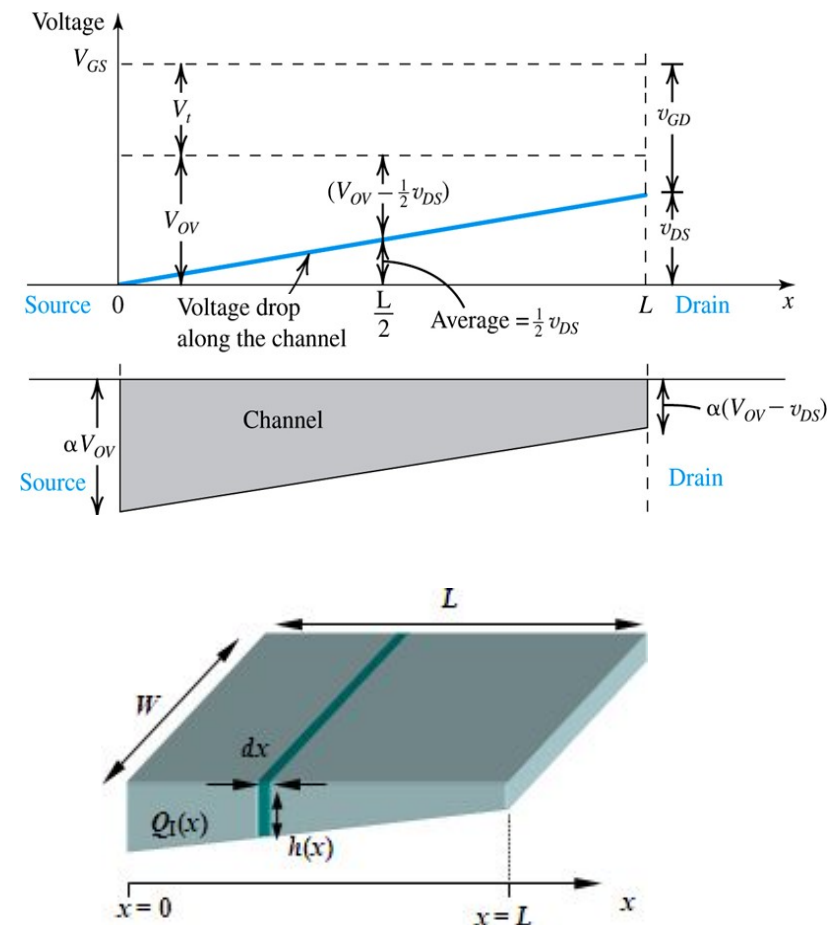

 Derivation of the i_D - v_{DS} Relationship



$$i = \frac{dq}{dt} = \frac{dq}{dx} \frac{dx}{dt}$$

$$Q = CV \quad C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} \quad (4.2)$$

$$\epsilon_{ox} = 3.9\epsilon_0 = 3.9 \times 8.854 \times 10^{-12} = 3.45 \times 10^{-11} \text{ F/m}$$

$$dq = -C_{ox}(Wdx)[v_{GS} - v(x) - V_t] \quad (4.3)$$

$$E(x) = -\frac{dv(x)}{dx} \quad (\because E = -\nabla V)$$

$$\frac{dx}{dt} = -\mu_n E(x) = \mu_n \frac{dv(x)}{dx} \quad (4.4)$$

$$i = -\mu_n C_{ox} W [v_{GS} - v(x) - V_t] \frac{dv(x)}{dx}$$

$$i_D = -i = \mu_n C_{ox} W [v_{GS} - v(x) - V_t] \frac{dv(x)}{dx}$$

$$i_D dx = \mu_n C_{ox} W [v_{GS} - V_t - v(x)] dv(x)$$

$$\int_0^L i_D dx = \int_0^{v_{DS}} \mu_n C_{ox} W [v_{GS} - V_t - v(x)] dv(x)$$

$$i_D = (\mu_n C_{ox}) \left(\frac{W}{L} \right) \left[(v_{GS} - V_t) v_{DS} - \frac{1}{2} v_{DS}^2 \right] \quad (4.5)$$

At the beginning of saturation region, $v_{DS} = v_{GS} - V_t$

$$i_D = \frac{1}{2} (\mu_n C_{ox}) \left(\frac{W}{L} \right) (v_{GS} - V_t)^2 \quad (4.6)$$

$$k'_n = \mu_n C_{ox} \quad (4.7) \quad C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} \quad (4.2)$$

$$i_D = k'_n \left(\frac{W}{L} \right) \left[(v_{GS} - V_t) v_{DS} - \frac{1}{2} v_{DS}^2 \right] \quad (\text{Triode region}) \quad (4.5a)$$

$$i_D = \frac{1}{2} k'_n \left(\frac{W}{L} \right) (v_{GS} - V_t)^2 \quad (\text{saturation region}) \quad (4.6a)$$


$\left(\frac{W}{L} \right)$: Aspect ratio of the MOSFET

The p -channel enhancement-type MOSFET

- ❑ p -channel enhanced-type MOSFETs are fabricated on n -type substrate with p^+ source and p^+ drain
- ❑ Normally, source is connected to high voltage and drain is connected to low voltage
- ❑ As a negative voltage applies to the gate, the resulting field pushes electrons in n -type substrate away from the surface, leaving behind a carrier-depletion region
- ❑ As gate voltage exceeds a negative **threshold voltage** V_t , holes accumulate on the substrate surface
- ❑ A p -type channel (**inversion layer**) is induced for current flow from source to drain
- ❑ Negative gate voltage is required to induce the channel → **enhancement-type** MOSFET

Complementary MOS (CMOS)

 
- ❑ CMOS technology employs both PMOS and NMOS devices
- ❑ If substrate is p -type, PMOS transistors are formed in n well (n -type body needed)
- ❑ If substrate is n -type, NMOS transistors are formed in p well (p -type body needed)
- ❑ The substrate and well are



Current-Voltage Characteristics

Circuit symbol

□ n -channel enhancement-mode MOSFET

 

The current-voltage characteristics




□ Cut-off region: ($v_{GS} \leq V_t$)

$$i_D = 0$$


□ Triode region: ($v_{GS} > V_t$ and $v_{DS} < v_{GS} - V_t$)

□ Saturation: ($v_{GS} > V_t$ and $v_{DS} \geq v_{GS} - V_t$)


□ large-signal model (saturation)

   



n-MOSFET Characteristics

 

 Plots V-I characteristics of the device for various Gate voltages (V_{GS})



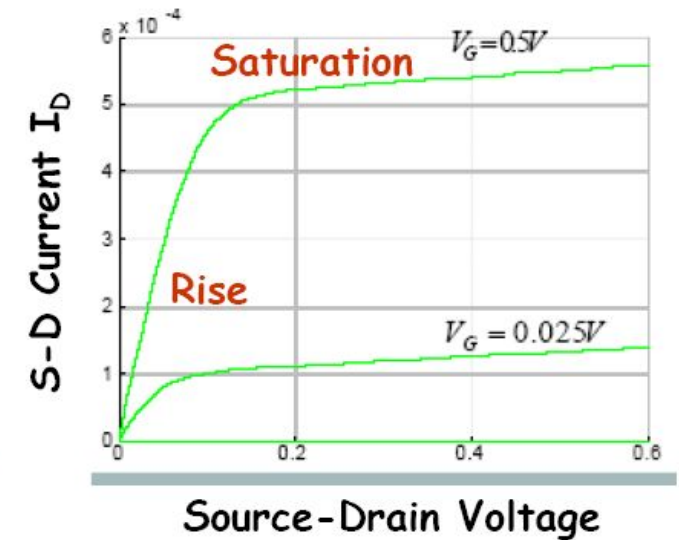 At a constant value of V_{DS} , we can also see that I_{DS} is a function of the Gate voltage, V_{GS} . The transistor begins to conduct when the Gate voltage, V_{GS} , reaches the Threshold voltage: V_T .



Current-Voltage Characteristics

Cut-off: $V_{GS} < V_T$
 $I_D = I_S = 0$

Triode: $V_{GS} > V_T$ and $V_{DS} < V_{GS} - V_T$
 $I_D = k_n' (W/L) [(V_{GS} - V_T)V_{DS} - \frac{1}{2}V_{DS}^2]$

Saturation: $V_{GS} > V_T$ and $V_{DS} > V_{GS} - V_T$
 $I_D = \frac{1}{2}k_n' (W/L)(V_{GS} - V_T)^2$

where $k_n' = (\text{electron mobility}) \times (\text{gate capacitance})$
 $= \mu_n (\epsilon_{ox} / t_{ox}) \quad \dots \text{electron velocity} = \mu_n E$

and V_T depends on the doping concentration and gate material used
(...more details later)


Channel length modulation

- ❑ The channel pinch-off point moves slightly away from drain as $v_{DS} > v_{DSsat}$
- ❑ The effective channel length (L_{eff}) reduces with v_{DS}
- ❑ Electrons travel to pinch-off point will be swept to drain by electric field
- ❑ The length accounted for conductance in the channel is replaced by L_{eff} :

$$\int_0^{v_{GS}-V_t} k_n' \frac{W}{L} [v_{GS} - V_t - v(x)] dv = i_D$$


$$i_D = \frac{1}{2} k_n' \frac{W}{L_{eff}} (v_{GS} - V_t)^2 \left(1 + \lambda v_{DS} \right)$$

 assuming that $\frac{\Delta L}{L} \propto v_{DS} \rightarrow i_D = \frac{1}{2} k_n' \frac{W}{L} (v_{GS} - V_t)^2 (1 + \lambda v_{DS})$



Finite output resistance

 
$$r_o \equiv \left[\frac{\partial i_D}{\partial v_{DS}} \right]_{v_{GS} \text{ constant}} = \left[\frac{\partial}{\partial v_{DS}} \left(\frac{1}{2} k_n' \frac{W}{L} (v_{GS} - V_t)^2 (1 + \lambda v_{DS}) \right) \right] = \frac{1}{\lambda V_A}$$



- ❑ V_A (**Early voltage**) = $1/\lambda$ is proportional to channel length: $V_A = V'_A L$
- ❑ V'_A is process-technology dependent with a typical value from 5 ~ 50 V/ μm
- ❑ Due to the dependence of i_D on v_{DS} , MOSFET shows **finite output resistance** in saturation region

The body effect

- ❑ The BS and BD junction should be reverse biased for the device to function properly
- ❑ Normally, the body of a n -channel MOSFET is connected to the most negative voltage
- ❑ The depletion region widens in BS and BD junctions and under the channel as V_{SB} increases
- ❑ **Body effect:** V_t increases due to the excess charge in the depletion region under the channel
- ❑ The body effect can cause considerable degradation in circuit performance

 

Temperature effect

- ❑ V_t decreases by $\sim 2\text{mV}$ for every 1°C rise $\rightarrow i_D$ increases with temperature
- ❑ k'_n decreases with temperature $\rightarrow i_D$ decreases with increasing temperature
- ❑ For a given bias voltage, the overall observed effect of a temperature increase is a decrease in i_D

Breakdown and input protection

❑ Weak avalanche

- *pn* junction between the drain and substrate suffers avalanche breakdown as V_{DS} increases
- Large drain current is observed
- Typical breakdown voltage 20 ~ 150 V

❑ Punch-through

- Occurs at lower voltage (~20 V) for short channel devices
- Drain current increases rapidly as the drain depletion region extends through the channel
- Does not result in permanent damage to the device


❑ Gate-oxide breakdown

- Gate-oxide breakdown occurs when gate-to-source voltage exceeds 30 V
- Permanent damage to the device

❑ Input Protection

- Protection circuit is needed for the input terminals of MOS integrated circuits
- Using clamping diode for the input protection


The *p*-channel enhancement-type MOSFET

 

- ❑ For a PMOS, the source is connected to high voltage and the drain is connected to low voltage
- ❑ To induce the *p*-channel for the MOSFET, a negative v_{GS} is required $\rightarrow V_t$ (threshold voltage) $< 0V$
- ❑ The body is normally connected to the most positive voltage

The current-voltage characteristics

 - ❑ Cut-off region: ($v_{GS} \geq V_{tp}$)
 $i_D = 0$
- ❑ Triode region: ($v_{GS} < V_{tp}$ and $v_{DS} > v_{GS} - V_{tp}$)
- ❑ Saturation: ($v_{GS} < V_{tp}$ and $v_{DS} \leq v_{GS} - V_{tp}$)




- ❑ Transconductance parameter $k'_p = \mu_p C_{ox} \approx 0.4 k'_n$
- ❑ The values of v_{GS} , v_{DS} , V_t and λ for *p*-channel MOSFET operation are all negative
- ❑ Drain current i_D is still defined as a positive current

MOSFET Circuits at DC

DC analysis for MOSFET circuits

- ❑ Assume the operation mode and solve the dc bias utilizing the corresponding current equation
- ❑ Verify the assumption with terminal voltages (cutoff, triode and saturation)
- ❑ If the solution is invalid, change the assumption of operation mode and analyze again

DC analysis example

 


Assuming MOSFET in saturation

$$-V_{SS} = V_{GS} + I_D R_S = V_{GS} + \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2 R_S$$

$$\rightarrow V_{GS} = 3V \text{ or } 1V \text{ (not a valid solution)}$$

 
$$(V_{DS} = 4V) \geq (V_{GS} - V_t = 1V) \rightarrow \text{saturation}$$



Assuming MOSFET in saturation

$$\rightarrow V_{GS} = 3V \text{ and } V_{DS} = -1.696V$$
 
$$V_{DS} < V_{GS} - V_t \rightarrow \text{not in saturation!}$$



Assuming MOSFET in triode

$$I_D = \frac{W}{L} \mu_n C_{ox} \left[(V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

$$V_{GS} + I_D R_S = -V_{SS}$$

$$V_{DS} + I_D (R_D + R_S) = V_{DD} - V_{SS}$$

$$\rightarrow V_{GS} = 3.35V, V_{DS} = 0.35V \text{ and } I_D = 0.33mA$$

$$V_{DS} < V_{GS} - V_t \rightarrow \text{in triode}$$

Applying the MOSFET in Amplifier Design

MOSFET voltage amplifier

□ MOSFET with a resistive load R_D can be used as a voltage amplifier

□ The voltage transfer characteristic (VTC)

- The plot of v_I (v_{GS}) versus v_O (v_{DS})
- DC analysis as v_{GS} increases from 0 to V_{DD}

■ Cutoff mode: ($0 \text{ V} \leq v_{GS} < V_t$)

$$\square i_D = 0$$

$$\square v_O = v_{DS} = V_{DD}$$

■ Saturation mode: ($v_{GS} > V_t$)



$$\square i_D \approx \frac{1}{2} \bar{k} (v_{GS} - V_t)^2$$

$$\square v_{DS} = V_{DD} - i_D R_D = V_{DD} - \frac{1}{2} \bar{k} (v_{GS} - V_t)^2 R_D$$

■ Triode mode: (v_{GS} further increases)

$$\square i_D \approx k [(v_{GS} - V_t) v_{DS} - \frac{1}{2} v_{DS}^2]$$
  
$$\square v_{DS} = \frac{1}{R_D} [V_{DD} - k (v_{GS} - V_t) v_{DS} + \frac{1}{2} k v_{DS}^2]$$



Biasing the MOSFET to obtain linear amplification

- ❑ The slope in the VTC indicates voltage gain
- ❑ MOSFET in saturation can be used as voltage amplification
- ❑ Point Q is known as **bias point** or **dc operating point**



- ❑ $V_{DS} \approx V_{DD} - \frac{1}{2}k_n(V_{GS} - V_t)^2 R_D$
- ❑ The signal to be amplified is superimposed on V_{GS}
 - ❑ $v_{GS}(t) = V_{GS} + v_{gs}(t)$
- ❑ The time-varying part in $v_{GS}(t)$ is the amplified signal
- ❑ The circuit can be used as a linear amplifier if:
 - A proper bias point is chosen for gain
 - The input signal is small in amplitude

The small-signal voltage gain

- ❑ The amplifier gain is the slope at Q :

$$A_v \equiv \left. \frac{dv_{DS}}{dv_{GS}} \right|_{v_{GS}=V_{GS}} = -k_n(V_{GS} - V_t)R_D = -k_n V_{OV} R_D$$
- ❑ Maximum voltage gain of the amplifier

$$|A_v| = \left| -\frac{I_{DD}}{V_{OV}} \right| \leq \frac{V_{DD}}{V_{OV}/2} = |A_{v \max}|$$

  

Determining the VTC by graphical analysis



- ❑ Provides more insight into the circuit operation
- ❑ **Load line:** the straight line represents in effect the load

$$i_D = (V_{DD} - v_{DS})/R_D$$

- ❑ The operating point is the intersection point

Locating the bias point Q

  - ❑ The bias point (intersection) is determined by properly choosing the load line
- ❑ The output voltage is bounded by V_{DD} (upper bound) and V_{OV} (lower bound)
- ❑ The load line determines the voltage gain
- ❑ The bias point determines the maximum upper/lower voltage swing of the amplifier



The MOSFET as an Amplifier and as Switch

The MOSFET acts as a Voltage-Controlled Current Source !

$$v_{GS}$$

$$i_D$$


Transconductance Amplifier !

Saturation Region !!!

$$i_D = \frac{1}{2} k'_n \frac{W}{L} (v_{GS} - V_t)^2 \quad (4.20) \text{ Saturation current} \quad \text{Nonlinear !}$$

For linear amplification, we need dc-bias voltage V_{GS} and require small input signal v_{gs} .

 4.4.1 Large-Signal Operation-The Transfer Characteristics



Basic structure of the **Common-Source (CS)** (ground-source) amplifier.

$$v_O = v_{DS} = V_{DD} - R_D i_D \quad (4.35)$$


4.4.2 Graphical Derivation of The Transfer Characteristics

$$v_{DS} = V_{DD} - R_D i_D \quad (4.36)$$

$$i_D = \frac{V_{DD}}{R_D} - \frac{1}{R_D} v_{DS} \quad (4.37)$$

Load-line equation

 For a given input $v_I (v_{GS})$,
We can find output $v_O (v_{DS})$.



Small-Signal Operation and Models

The DC bias point

□ MOSFET in saturation

■ Drain current: $I_D = \frac{1}{2} k_n' \left(\frac{W}{L} \right) (V_{GS} - V_{th})^2$

■ Drain voltage: $V_{DS} = V_{DD} - I_D R_D > V_{OV}$

□ The small-signal circuit parameters are determined by the bias point

The small-signal operation

□ The small-signal drain current:

$$v_{GS} = V_{GS} + v_{gs}$$

$$i_D = \frac{1}{2} k_n' \left(\frac{W}{L} \right) (V_{GS} + v_{gs} - V_{th})^2 = \frac{1}{2} k_n' \left(\frac{W}{L} \right) (V_{GS} - V_{th})^2 + k_n' \left(\frac{W}{L} \right) (V_{GS} - V_{th}) v_{gs} + \frac{1}{2} k_n' \left(\frac{W}{L} \right) v_{gs}^2$$

$$\approx \frac{1}{2} k_n' \left(\frac{W}{L} \right) (V_{GS} - V_{th})^2 + k_n' \left(\frac{W}{L} \right) (V_{GS} - V_{th}) v_{gs} = I_D + g_m v_{gs}$$



$$\rightarrow i_d = g_m v_{gs}$$

□ The small-signal voltage gain:

$$v_D = V_{DD} - i_D R_D = V_{DD} - (I_D + i_d) R_D = V_D - i_d R_D = V_D + v_d$$

$$\rightarrow v_d = -i_d R_D = -g_m v_{gs} R_D$$
  
$$\rightarrow A_v \equiv \frac{v_d}{v_{gs}} = -g_m R_D$$



The small-signal parameters

- Transconductance (g_m): describes how i_d change with v_{gs}

$$g_m \equiv \frac{i_d}{v_{gs}} = \left. \frac{\partial i_D}{\partial v_{gs}} \right|_{v_{gs}=V_{GS}} = k_n' \frac{W}{L} (V_{GS} - V_t) = \sqrt{2k_n' \frac{W}{L} I_D}$$

- Output resistance (r_o): describes how i_d change with v_{ds}

$$r_o \equiv \left[\frac{\partial i_D}{\partial v_{ds}} \right]_{v_{gs}=constant}^{-1} \approx \frac{1}{\lambda I_D}$$

- Drain current varies with v_{DS} due to channel length modulation
- Finite r_o to model the linear dependence of i_D on v_{DS}
- The effect can be neglected if r_o is sufficiently large

- Body transconductance (g_{mb}): describes how i_d changes with v_{bs}

$$i_D = \frac{1}{2} k_n' \frac{W}{L} (v_{gs} - V_t)^2$$



$$\rightarrow g_{mb} \equiv \left. \frac{\partial i_D}{\partial v_{bs}} \right|_{v_{gs}=constant, v_{ds}=constant} = \frac{\partial i_D}{\partial V_t} \frac{\partial V_t}{\partial v_{bs}} = - \frac{W}{L} (v_{gs} - V_t) \frac{\partial V_t}{\partial v_{bs}} = - g_m \frac{\partial V_t}{\partial v_{bs}}$$

$$V_t = V_{t0} + \gamma \sqrt{2\phi_F + v_{SB}} - \sqrt{2\phi_F} \quad \text{where } \gamma = \sqrt{\frac{2qN_A \epsilon_{Si}}{C_{ox}}}$$

$$\rightarrow \frac{\partial V_t}{\partial v_{bs}} \equiv \chi = \frac{\gamma}{2\sqrt{2\phi_F + v_{SB}}}$$


$$g_{mb} = g_m \chi$$

  - The body effect of the MOSFET is modeled by g_{mb}
- Can be neglected if body and source are connected together




The small-signal equivalent circuit models

□ Hybrid- π model

 

□ T-model

 

Small-Signal Parameters

NMOS transistors

■ Transconductance:


$$g_m = \mu_n C_{ox} \frac{W}{L} V_{OV} = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} = \frac{2I_D}{V_{OV}}$$

■ Output resistance:

$$r_o = V_A / I_D = 1 / \lambda I_D$$

Basic MOSFET Amplifier Configuration

Three basic configurations

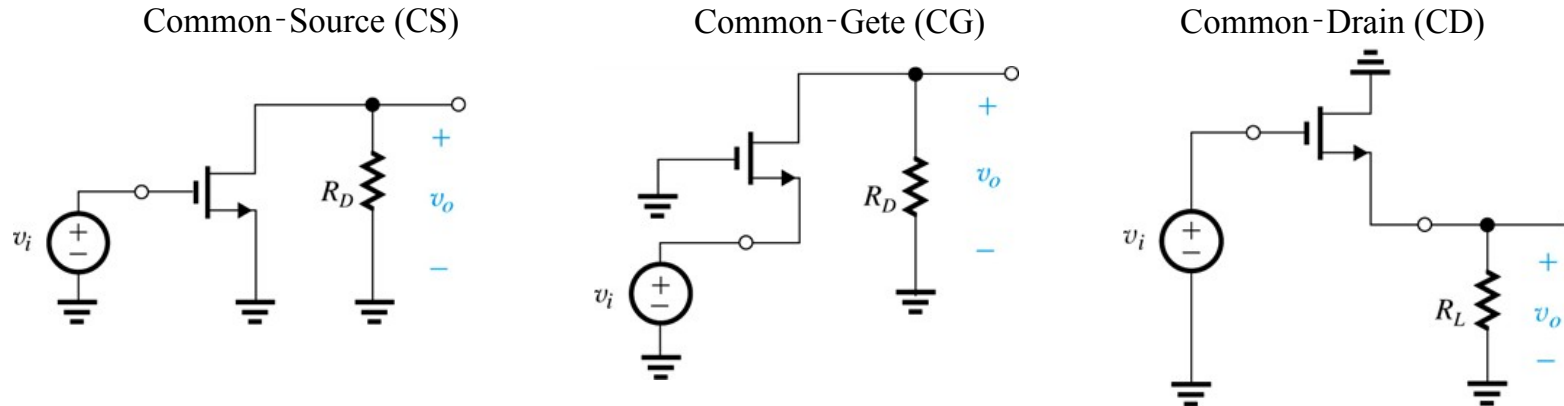


Characterizing amplifiers

- ❑ The MOSFET circuits can be characterized by a voltage amplifier model (unilateral model)
- ❑ The electrical properties of the amplifier is represented by R_{in} , R_o and A_{vo}
- ❑ The analysis is based on the small-signal or linear equivalent circuit (dc components not included)

❑ Voltage gain: $A \equiv \frac{v_o}{v_i} = \frac{R_L}{R + R_L} A_{vo}$

 ❑ Overall voltage gain: $G \equiv \frac{v_o}{v_{sig}} = \frac{R_{in}}{R_{in} + R_{sig}} A_v = \frac{R_{in}}{R_{in} + R_{sig}} \frac{R_L}{R_{in} + R_{sig} + R_L} A_{vo}$



Biasing in MOS Amplifier Circuits

DC bias for MOSFET amplifier


- ☐ The amplifiers are operating at a proper dc bias point
- ☐ Linear signal amplification is provided based on small-signal circuit operation
- ☐ The DC bias circuit is to ensure the MOSFET in **saturation** with a proper collector current I_D

Biasing by fixing gate-to-source voltage

- ☐ Fix the dc voltage V_{GS} to specify the saturation current of the MOSFET: $I_D = \frac{1}{2} k_n (V_{GS} - V_t)^2$
- ☐ Bias current deviates from the desirable value due to variations in the device parameters V_t and μ_n


Biasing by fixing gate voltage and connecting a source resistance

 - ☐ The bias condition is specified by: $V_{GS} = V_G - I_D R_S$
- ☐ Drain current has better tolerance to variations in the device parameters



Biasing using a drain-to-gate feedback resistor

 - ❑ A single power supply is needed
- ❑ R_G ensures the MOSFET in saturation ($V_{GS} = V_{DS}$)
- ❑ MOSFET operating point: $\frac{V_{DD}}{1 + \sqrt{2} R_D} = - \frac{1}{2} \mu_n k (V_{GS} - V_t)^2$
- ❑ The value of the feedback resistor R_G affects the small-signal gain



Biasing using a constant-current source


- ❑ The MOSFET can be biased with a constant current source I
- ❑ The resistor R_D is chosen to operate the MOSFET in active mode
- ❑ The current source is typically a current mirror
- ❑ Current mirror circuit:

- MOSFETs Q_1 and Q_2 are in saturation
- The reference current $I_{REF} = I = I_D$

$$\frac{V_{DD}}{1 + \sqrt{2} R} = - \frac{1}{2} \mu_n k (V_{GS} - V_t)^2$$

$$I_{REF} = \frac{1}{2} \mu_n k (V_{GS} - V_t)^2$$

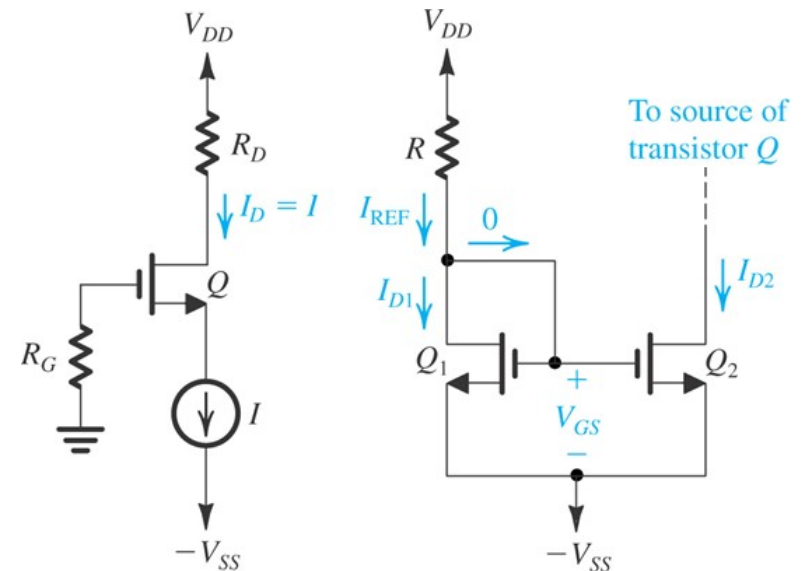- When applying to the amplifier circuit, the voltage V_{D2} has to be high enough to ensure Q_2 in saturation



NEW

BJT vs MOSFET

- RTL logic vs CMOS logic
- DC Input impedance of MOSFET (at gate end) is infinite
Thus, current output can drive many inputs □ **FANOUT**
- CMOS **static dissipation is low!!** $\sim I_{\text{OFF}} V_{\text{DD}}$
- Normally BJTs have higher transconductance/current (faster!)

$$I_C = (qn_i^2 D_n / W_B N_D) \exp(qV_{\text{BE}} / kT)$$


$$g_m = \partial I_C / \partial V_{\text{BE}} = I_C / (kT/q)$$

$$I_D = \mu C_{\text{ox}} W (V_G - V_T)^2 / L$$

$$g_m = \partial I_D / \partial V_G = I_D / [(V_G - V_T)/2]$$


- Today's MOSFET $I_D \gg I_C$ due to near ballistic operation

MOSFET Biasing

 


Basic Arrangement

$$V_{GS} = V_G - R_S I_D$$

 

Bias with one power supply

$$V_{GS} = V_G - R_S I_D$$

 


Bias with two power supplies

$$V_{GS} = V_{SS} - R_S I_D$$


$$(KVL: 0 + V_{GS} + R_S I_D - V_{SS} = 0)$$

➤ Resistor R_S provides negative feedback

Fixed Bias

 

6

 

Investigating the input loop

- $I_G = 0A$, therefore

$$V_{RG} = I_G R_G = 0V$$

- Applying KVL for the input loop,

$$-V_{GG} - V_{GS} = 0$$



$$V_{GG} = -V_{GS}$$

- It is called *fixed-bias configuration* due to V_{GG} is a fixed power supply so V_{GS} is fixed

- The resulting current, $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$

Self Bias

  - The self-bias configuration eliminates the need for two dc supplies.
- The controlling V_{GS} is now determined by the voltage across the resistor R_S



- For the indicated input loop:

$$V_{GS} = -I_D R_S$$

- Mathematical approach:

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$I_D = I_{DSS} \left(1 - \frac{I_D R_S}{V_P} \right)^2$$

- rearrange and solve.

- For output loop



- Apply KVL of output loop
- Use $I_D = I_S$

$$V_{DS} = V_{DD} - I_D (R_S + R_D)$$

$$V_S = I_D R_S$$

$$V_D = V_{DS} + V_S = V_{DD} - V_{RD}$$

Voltage Divider Bias

  

- V_G can be found using the voltage divider rule

$$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$$

- Using Kirchoff's Law on the input loop:

- Rearranging and using $I_D = I_S$:

$$V_G - V_{GS} - V_{RS} = 0$$

$$V_{GS} = V_G - I_D R_S$$

- Once the quiescent values of I_{DQ} and V_{GSQ} are determined, the remaining network analysis can be found.


$$I_{R1} = I_{R2} = \frac{V_{DD}}{R_1 + R_2}$$

- Output loop:

$$V_{DS} = V_{DD} - I_D (R_D + I_D R_S)$$

$$V_D = V_{DD} - I_D R_D$$

$$V_S = I_D R_S$$

 

Again plot the line and the transfer curve to find the Q-point.
Using the following equations:

$$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$$

Input loop : $V_{GS} = V_G - I_D R_S$

Output loop: $V_{DS} = V_{DD} - I_D (R_S + R_D)$